

Vol. 9 No. 7

OCTOBER  
1947

Registered at the G.P.O.,  
Sydney, for transmission  
by post as a periodical.

# RADIO

AND HOBBIES IN AUSTRALIA

6<sup>D</sup>



## Ken-Rad

THE FINE VALVES

OF RADIO

A TINY 5-VALVE PERSONAL SET



# Marconi School of Wireless

CONDUCTED BY  
AMALGAMATED WIRELESS (AUSTRALASIA) LTD.

FOR 33 YEARS THE LEADING RADIO COLLEGE IN AUSTRALIA

Backed by the resources of A.W.A. the Marconi School has always been in the position to provide the most up-to-date instruction in all modern Radio developments.

## SERVICE MECHANICS

New Course covering THEORY and PRACTICAL Instruction  
now available

## OTHER COURSES

### COMMERCIAL AND BROADCAST OPERATORS

Day or Night Classes	Next term commences 3rd November, 1947.
Correspondence	Course can be commenced at any time.

### AMATEUR RADIO OPERATORS

Night Classes	Next term commences 3rd October 1947.
Correspondence	Course can be commenced at any time.

### MATHEMATICS REFRESHER COURSE

Next term commences 3rd November, 1947.

### MORSE TELEGRAPHY

Classes in Oscillator and Sounder always available.

Call, 'phone or write for full particulars:—

## MARCONI SCHOOL OF WIRELESS

47 YORK STREET  
SYDNEY  
Tel. B0522

163 QUEEN STREET  
MELBOURNE  
Tel. MU9161

### POST THIS NOW

MARCONI SCHOOL OF WIRELESS

Box 2516, G.P.O., Sydney

Please send me without obligation  
full details of your courses.

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_





## Editorial

OUR baby portable, the Handie Talkie, described in this issue, is something of a landmark in receiver design.

In itself, it is the only five-valve set of its type we have yet seen, which probably makes it a "first", at least in Australia. It is as small or smaller than all the other four-valvers so far sighted, only one of which has been of Australian manufacture. This, despite the wooden cabinet we had to use, as against a thin-walled moulded type.

The problem of fitting everything into a small space, although the solution looks simple enough, is far more difficult than laying out a big set. For this reason, we are

permitting ourselves to be proud of our design, and I think you'll agree we really have something!

A further point we have to watch is that our original shall be capable of duplication by our readers. Chassis and parts have to be obtainable, and made to fit together. For this reason, a hand-made job using special bits and pieces might possibly have been fractionally smaller, but so little that it is doubtful whether the result would amount to much.

We are convinced that sets of this type will before long be well established sellers, simply because they fill a definite requirement. The value of anything is set by how much more one will pay to get it. If you want it badly enough, you will consider the money well spent. These sets won't be cheap because their total components are about the same as for bigger jobs.

For these reasons, we think our design is indicative of an entirely new type of set. It is the logical conclusion to all the portable sets of the past, which have really been standard chassis and speakers squeezed into cabinets which were really "in between." So much so that one manufacturer early in the piece actually supplied his portable with a large accumulator to run it!

Where torch-type batteries are easy to get, and cheap, replacements of the A battery isn't really a problem, any more than it is with a torch. Carrying it round is much the same as in the case of a camera, with little difference in size and weight.

Good luck to the personal portables. We think ours is good enough to set the pace. You'll think so too, when you first switch it on!

At last we have been able to set a publication date for our new Short-Wave Handbook, and you can look for it about the middle of October. It has grown considerably since we first thought of bringing out a call-sign list. It now covers, in addition, illustrated designs for dual-wavers, short-wavers, transmitters and modulators for amateurs, and other information with a particular application to short-wave listening. It will have about 100 pages with a heavyweight, colored cover, and for its price, 2/-, cannot be equalled for value by any other publication, local or overseas.

Sorry it has been a little longer appearing than we had hoped, but we wanted to get it right before you bought it.

Look for its blue cover soon, and then let us know what you think about it. Next year's edition is already being planned on a much bigger scale, and we'd like to include your ideas.

But that's a story for the future. We are printing plenty, but anticipate a sell-out in short order. Don't say we didn't warn you!

*John Moyle*

## INDEX

Page	Page
Mother Can Hear When Baby Cries . . . . . 3	A 166 MC Receiver . . . . . 54
Supersonic Washing Machine . . . . . 4	Trade News And Releases . . . . . 61
Technical Review . . . . . 7	New Folding Wing Aircraft . . . . . 65
Secrets Of White Light . . . . . 12	Studying The Shock Wave . . . . . 66
Push-Button Telegraph . . . . . 17	News Of The Skyrays . . . . . 68
A Flying Torpedo . . . . . 19	The Douglas Skystreak . . . . . 70
News And Views—Crossword . . . . . 21	A Three-Wheeled Scooter . . . . . 71
Handie Talkie Personal Set . . . . . 24	Short-Wave Notes . . . . . 76
A 20-Watt Amplifier . . . . . 37	Amateur Notes . . . . . 80
Home Recording . . . . . 46	Record Reviews . . . . . 82
Serviceman Who Tells . . . . . 51	Answers To Correspondents . . . . . 84
	Book Reviews . . . . . 87

## McGILL'S

Est. 1860

### TECHNICAL BOOKS ON ALL SUBJECTS

A Brief Selection from our Large Range of Publications.

#### RADIO

	Price	Postage
RCA Receiving Tube Manual	3/3	4d
Radiotron Designers' Handbook	6/-	6d
How To Make Good Recordings	8/9	4d
The Amateur Radio Handbook	8/-	5d
The Radio Amateur's Handbook, American Radio Relay League	12/6	1/-
The Log of Amateur Radio Station, American Radio Relay League	3/9	3d
All About Frequency Modulation, Radio Craft	4/-	2½d
Handbook for the Guidance of Operators of Experimental Wireless Stations	1/6	1½d
Techniques of Recording, Goldsmith and Geisel	8/-	2½d
Radio for the Millions—Popular Science	10/6	7d
Technical Topics Radio Handbook—Mingay	7/6	6d
Philips Manual of Radio Practice, Beard	22/6	1/3
Modern Radio and Home Recording	2/-	2½d

#### BOAT BUILDING, etc.

Model Boat for Juniors—Horst	14/-	8d
Handbook of Knots, Graumont	7/-	3d
Wooden Boat Ship Building, Gaasbeek	18/9	5d
Brown's Knots and Sollices	4/5	2½d
How To Build Boats, Hauber	7/6	2½d
Model Steamers and Motor Boats, How To Build and Run Them, Percival Marshall	5/6	3d
Model Sailing Yachts, Percival Marshall	4/9	3d
Building the Small Boat, Bradley	12/3	8d
Rowboats, Bicycle Boat, Small Dinghy, Popular Mechanics	1/9	1½d
How To Build Your Own 14-Foot Sailing Dinghy, Popular Mechanics	1/9	1½d
"Skipper" 14-Foot Outboard Runabout, Popular Mechanics	1/9	1½d
12 & 14ft. Outboard Runabouts, Popular Mechanics	1/9	1½d
How To Build Your Own Canoe, Kayak or Surfboard, Popular Mechanics	1/9	1½d
Small Sailboats, Popular Mechanics	1/9	1½d
Build a Boat for Pleasure or Profit, Popular Mechanics	10/6	6d
Plywood Boats, Rudder	7/6	3d

Mail Orders by Return Post.

### SUBSCRIPTION DEPARTMENT 1st Floor.

American and English Radio Magazines.	
Q.S.T. . . . . (A)	21 7 0
C.Q. . . . . (A)	1 5 0
Audio Engineering . . . . . (A)	1 5 0
Radio News . . . . . (A)	1 12 0
Radio Craft . . . . . (A)	1 2 0
Communications . . . . . (A)	1 2 0
Service . . . . . (A)	1 2 0
Wireless World . . . . . (E)	1 5 0
Electronic Engineering . . . . . (E)	1 12 6
Wireless Engineer . . . . . (E)	2 0 0

PLUS EXCHANGE.

### McGILL'S AGENCY

183 ELIZABETH STREET,  
MELBOURNE.

(The G.P.O. is opposite.)

Phone C.8113-4.



## *An AUSTRALIAN Organisation*



### *Working for AUSTRALASIA*

In these days, goods of all descriptions are in abnormal demand and the radio industry is no exception.

Under these conditions, it is inevitable that there are some people who cannot be fully satisfied. Some of these people start looking for a reason other than the most obvious one—that the industry cannot immediately supply the inflated and unstable demand.

All sorts of tales come to light—some true, some with a vestige of distorted truth and others entirely false. You may have heard some of these yourself. You may have heard for instance, that Rola is exporting a large proportion of their production to newly found overseas markets.

Such is far from the truth, and we say quite definitely that Rola products are not going

out of Australasia, which corner of the globe, it is our bounden duty to serve.

The new markets that are opening up are not for Rola until our customers in Australasia have been satisfied.

Rola Co. (Aust.) Pty. Ltd. is a completely independent Australian organisation working one hundred percent for Australasia.

# **ROLA**

**GEO. BROWN & CO. PTY. LTD.,**  
267 Clarence Street, Sydney.

## **ROLA CO. (AUST.) PTY. LTD.**

The Boulevard, RICHMOND, Victoria  
**JOHN MARTIN PTY. LTD.,**  
116-118 Clarence Street, Sydney.




# MOTHER CAN HEAR WHEN BABY CRIES



Wouldn't you like one of these? Just one more gadget from USA via which Mrs. Wayne Morris and her 3-year-old daughter say goodnight to daddy. If the baby cries in the night while in bed, she can be heard anywhere in the house. Yes, we heard—most children can get the same result with a good pair of lungs! Anyhow, it's a pretty picture.



# YOUR FAMILY WASHING A PROBLEM?

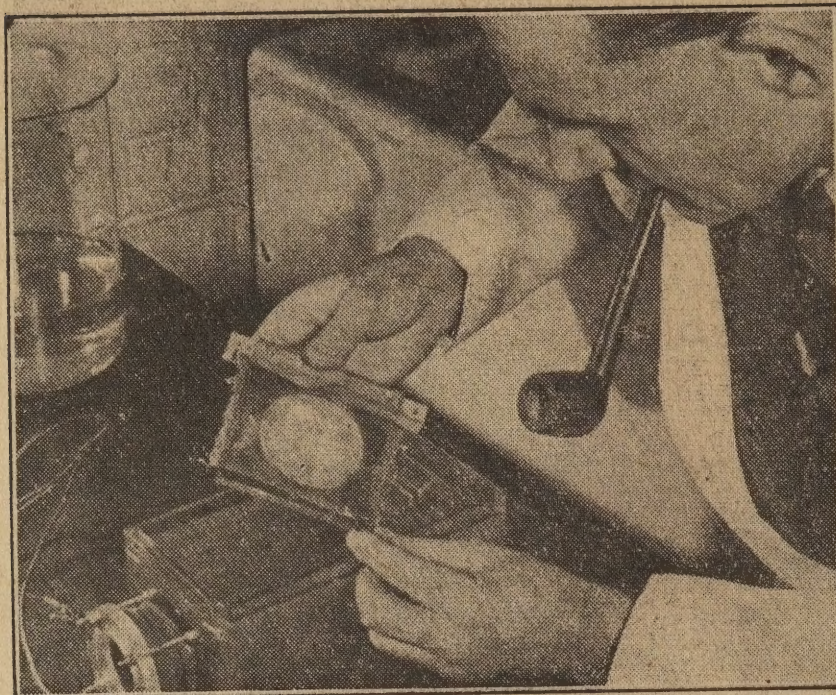

THE object of the association is to provide answers to scientific and technological problems that arise in practice in the industry concerned, and to carry out fundamental research which ultimately is the basis for real and lasting advances in technique.

The research director of the Launderers' Research Association is Mr. Courtney Harwood, himself a professional research chemist, and it was he who showed me round when I visited its laboratories recently.

The laundry industry in Britain is composed of many widely-scattered units, few of which, if any, are large

Mr. John Bold, Senior Electrical Technician at the British Launderers' Research Association Laboratories, Haddon, inserting a test-piece of soiled fabric into the "cleaning tank." The disc of quartz-reproducer from which the supersonic vibrations are propagated is in the circular fitting at the left-hand end of the tank. In this test transformer oil was used as the medium in the tank for certain technical reasons, but plain water is used normally.

The announcement of a promising, new method of cleaning soiled fabrics has been brought to the notice of the British Launderers' Research Association. Trade Research Associations now form an altogether characteristic feature of British industry. These organisations are staffed mainly by scientists and financed primarily by contributions from firms likely to be interested in their results; in many cases the annual income is augmented by Government grants.



enough to maintain a research staff. Its Research Association, therefore, is the only organisation able to carry out the fundamental and ad hoc research applicable to the industry. It also makes officers available to give advice to the people operating in the industry (as many of them do) with only a very limited technical training. It has, besides the director, a staff of 28 scientists, fully qualified in chemistry, physics, engineering and textile technology and bacteriology; in addition to these there are 50 assistants. As well as maintaining research laboratories, which at the moment are being considerably enlarged, the association runs a small laundry so that the laboratory results can immediately be put to a commercial test.


## WAVES SHAKE DIRT

The news I went specifically to investigate was that of promising results coming from an attempt to use supersonic waves to shake dirt particles off fabrics being laundered. The waves themselves are of the same nature as sound waves, but they are far higher than the ear can hear (hence the term "supersonic"); their use follows the principle employed for submarine detection during the war in the so-called asdic gear. Dust particles are held to fabrics by electrical attraction and it is this that is broken initially by the detergent solution (soaps, &c.) in

Adjusting the frequency of the amplifier. Tests have been carried out up to 300 kilocycles, and tests are to be carried out at frequencies up to a megacycle.



# THEN USE SUPERSONIC VIBRATIONS

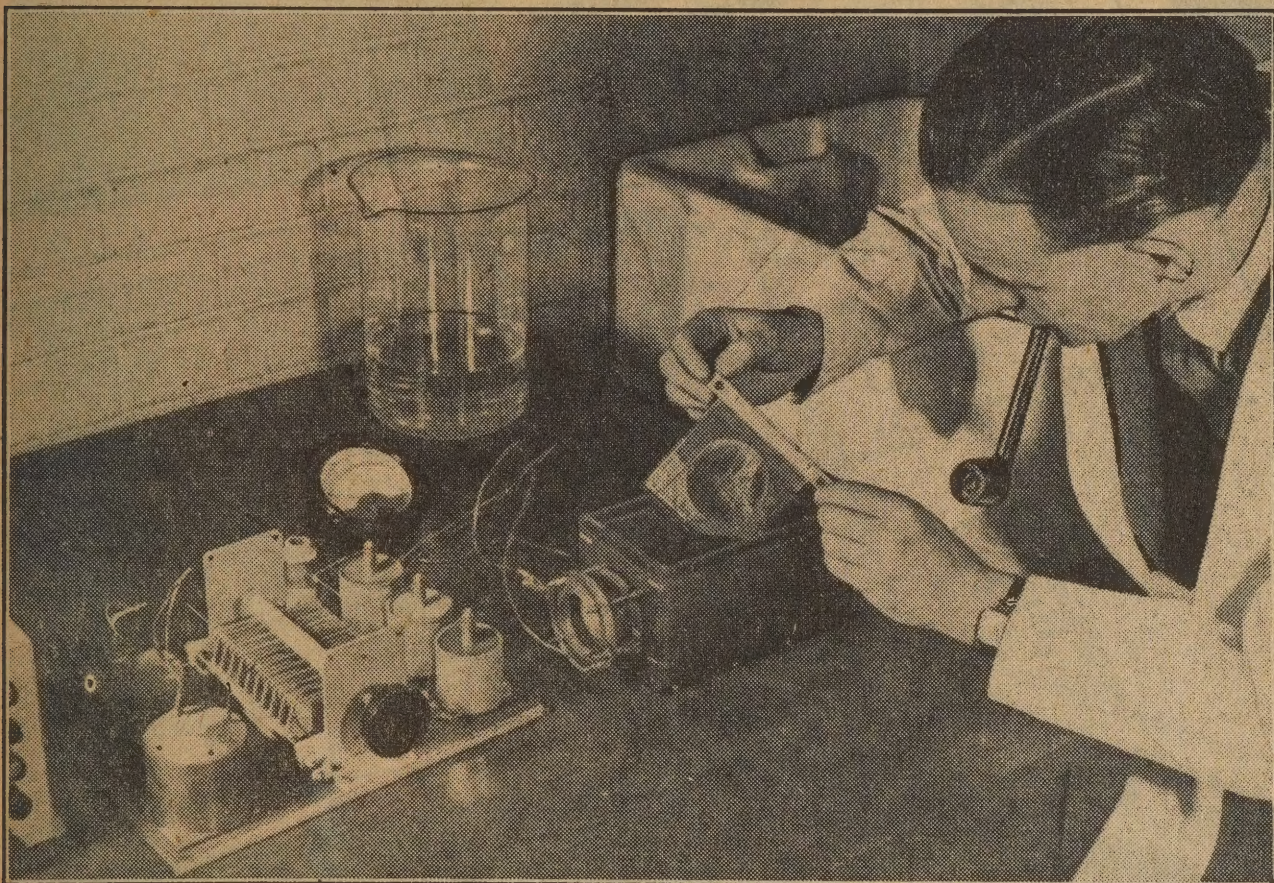

Mr. Bold holding the fabric test-piece just removed from the tank after a ten-minute "treatment." The fabric which was soiled black on immersion shows clear and clean in the centre area where it was subjected to the supersonic vibrations from the quartz-reproducer.

normal use in laundries. Supersonic waves are not intended to replace the detergents, but, after having shaken foreign particles clear of the fabric, to emulsify them in the solution, and thus keep them clean.

## EXPERIMENTAL ONLY

Mr. Harwood stressed that, although 12 months work has already gone into this research, and results are promising, a commercially practicable outcome is not to be expected for some long time—indeed, the apparatus I saw being used was only on a laboratory scale. Apart from the electrical gear originating and amplifying the waves, the actual container was no more than about 30 cm. long and 20 cm. deep. At one end of this bath was a quartz crystal cut to oscillate in sympathy with the frequency used and so placed that it could pass the oscillations on into the light oil with which the bath was filled. In the bath stood a beaker of detergent solution in which an 8 by 8 cm. sample of fabric of known "dirtiness" was suspended. The electrical generating apparatus is, of course, connected with the quartz crystal, which transmits the waves right through the bath.

The foregoing then is the scale on which experiments are being conducted

at present; a great deal more remains to be done before the new technique can be brought to a commercial scale. Even the most desirable frequency has not yet been determined; so far only those between 10 and 100 kilocycles per second have been tried at all extensively.

While it is too early to make predictions as to the effect such a method, if practicable, would have on the industry as a whole, it seems likely that it might enable commercial washing to be carried out at lower temperatures than are necessary with contemporary equipment. The supersonic method would certainly cut right across the normal revolving drum practice, because soiled articles would have to be extended during the process and not jumbled together as they are in the drum.

The method might also speed up handling of laundry, especially by


making unnecessary preliminary sorting of articles into different classes, which at present must be carried out before any washing can begin.

## NEW SOAPS

Supersonic waves, however, is only one of the subjects that are being pursued at the Launderers' Research Association. New soaps, new washing machines, and new thermostatically controlled irons are also being investigated, and, when necessary, prototypes of new plant can be built in the laboratory. During the war, fundamental research was held up there, as it was in most such institutions, so that urgent ad hoc investigations might be made as required. One great advance during this period was the development of a technique for lessening cross-infection from blankets used in hospital wards. Bed making in hospitals causes bacteria from the blankets to rise into the air, thus increasing the risk of cross-infection among the patients. The Launderers' Research Association's contribution to the solution of this trouble has been to devise an economic and effective process for oiling blankets during laundering so that the shaking of bacteria into the air during bed-making is materially lessened.

by *Ian Cox*



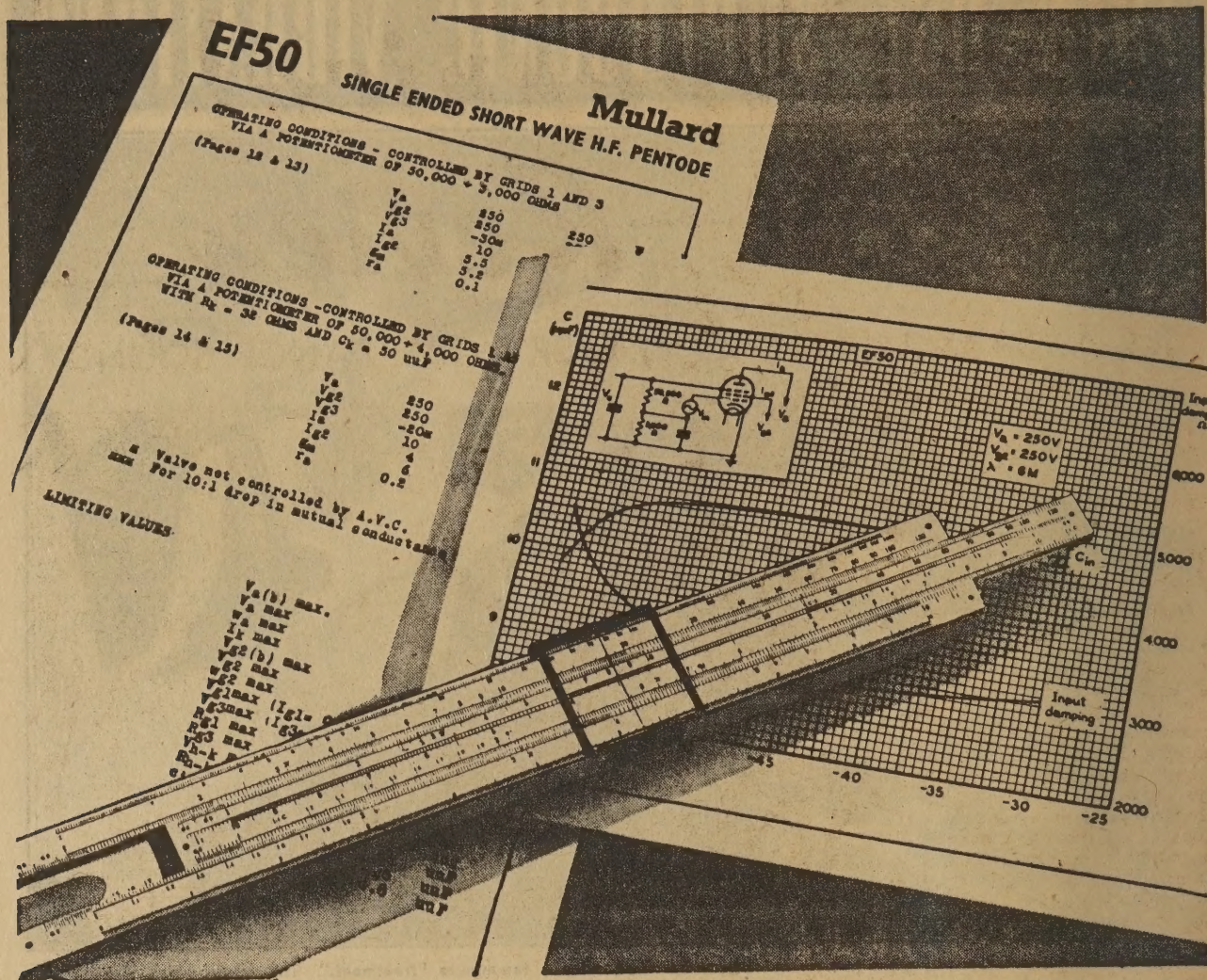

Whatever the application—known or potential—there is probably a Mullard valve or tube for the purpose.

# Mullard


*Engineers in Electronics*



MULLARD-AUSTRALIA PTY. LTD.

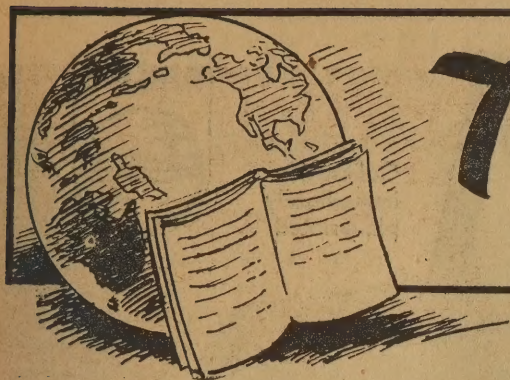35-43 CLARENCE ST., SYDNEY • DISTRIBUTORS IN ALL STATES





# Technical Review

## R.C.A. SAYS LISTENERS PREFER WIDE RANGE SOUND

Tests carried out on more than 1000 people by the RCA Acoustics Research Laboratory have thrown fresh light on public reaction to frequency response. Contrary to previous surveys, these tests indicated a preference for music with its full range of tones and overtones.

**C**ONDUCTED by Dr. Harry Olson, section head of the laboratory, the tests were conducted using a small orchestra instead of a loud-speaker as the sound source. The orchestra consisted of piano, trumpet, clarinet, violin, contrabass, drums and traps. It was placed in a room acoustically treated to simulate listening conditions in an average living-room.

A partition constructed of material that absorbed all tonal frequencies above 5000 cycles—the normal limiting range of radio reproduction — was placed between the musicians and the audience. By revolving movable panels in the partition, this limitation on tone quality could be removed, allowing the music to reach the audience unchanged.


### EFFECT OF AGE

Additional tests with subjects in various age groups, Dr. Olson added, showed that 75 per cent. of listeners between 30 and 40 preferred the full frequency range of popular music while only 59 per cent. of those between 14 and 20 expressed appreciation for the unrestricted tonal range in this classification of music.

"The listeners in the latter age group," Dr. Olson added, "are probably influenced by listening to radios, phonographs and juke boxes rather than orchestras and are, therefore, conditioned to a restricted frequency range."

Most of the tests were carried out using popular dance music. The small size of the room made it impossible to play symphonic numbers, but listener preference in this direction was checked with semi-classical selection. For all practical purposes, these results agreed closely with those obtained in the popular-music test.

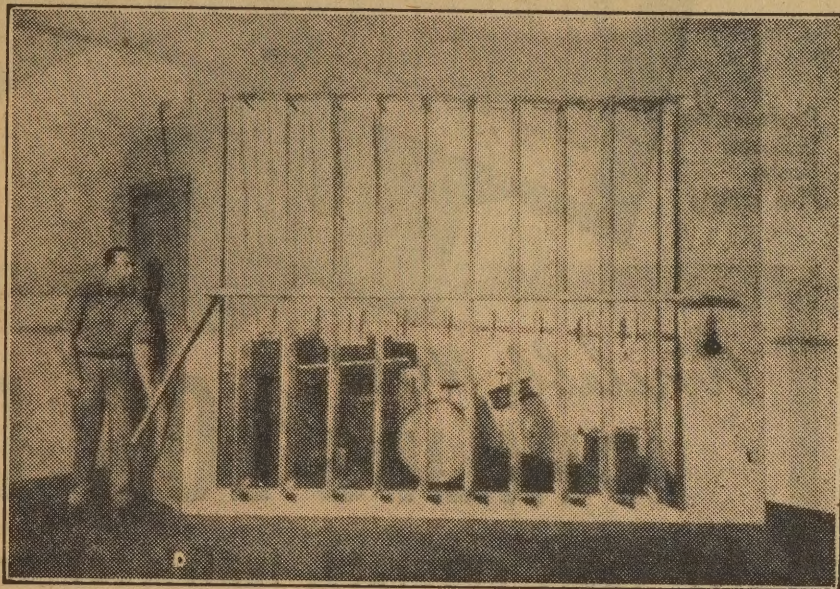When tests were carried out on speech, listeners preferred the full frequency range whether the audience was familiar with the speaker's voice or when the voice was being heard for




For the new tests by RCA, a small orchestra was housed in this special cubicle. The rotating partitions were made of a material absorbing all frequencies higher than about 5000 c/s. Use of an actual orchestra confined the audience reaction purely to frequency response.

the first time.

In discussing the preferences of listeners for mechanically reproduced music with restricted frequency range,

Dr. Olson said that this choice might be due to the distortions of sound which are inherent in common types of reproducing systems.

### SMALL TELEVISION CAMERA

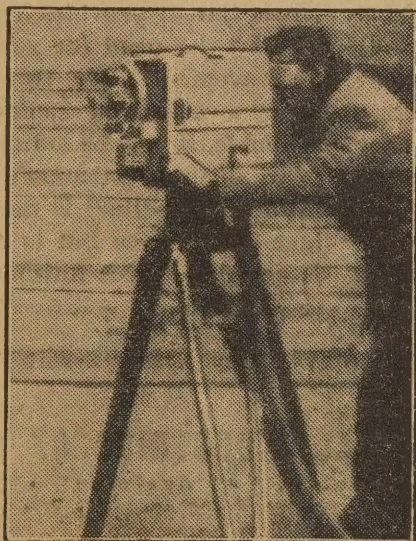

**S**MALL television cameras and high definition pictures are being developed in France. The equipment nearest application is the 819 line system of La Radio Industrie, featuring an incolescope with a primary image of only 1 cm. square. This camera, called the Eriscope, uses 16 mm. movie camera lenses and has a depth of field from 2 metres to infinity without focusing.

It can be used for normal outdoor work at intensities down to 500 lumens, but still further improvement is envisaged. The camera, which is comparable in size with a newsreel camera, contains the preamplifier and the final stages of the sweep circuits.


Transmission of the double interlaced picture at 50 half frames per second will be at 200 Mc. from a transmitter having a peak power of 1 Kw. Synchronising pulses are to be transmitted by A.M., and 10 Mc. picture band by F.M. and the sound on a separate 200 watt F.M. transmitter.





Calibration  
immediately  
pin-pointed

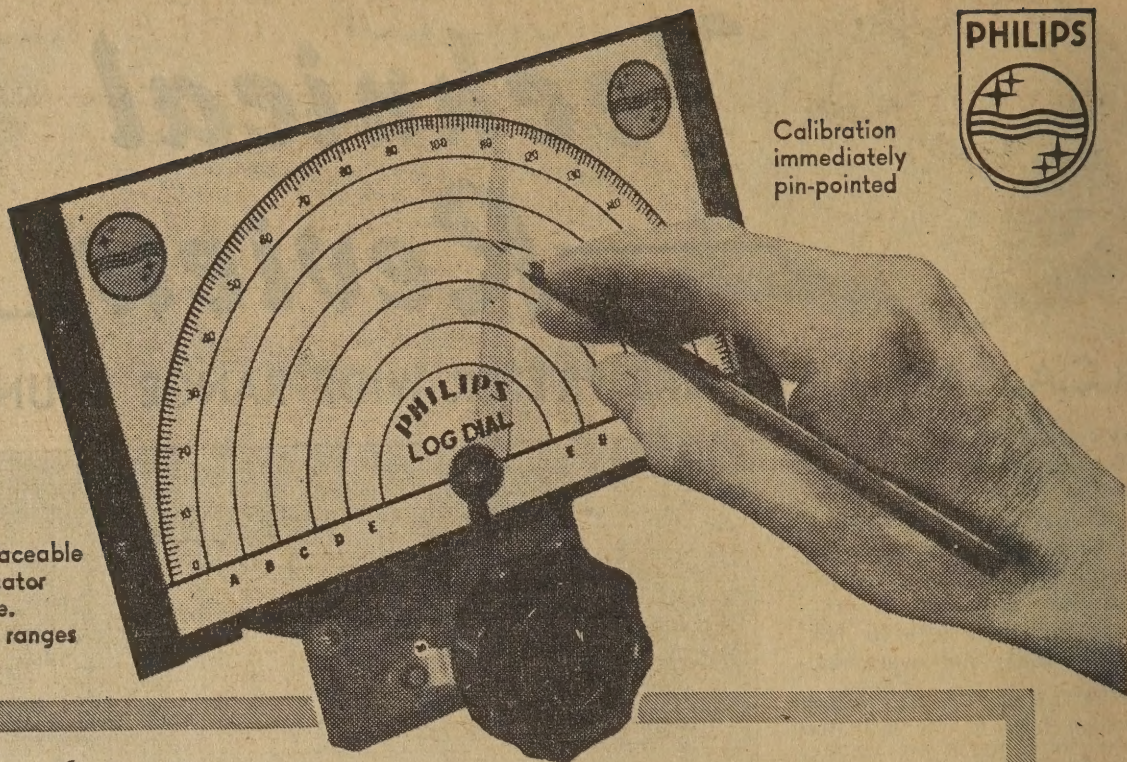Replaceable  
Indicator  
Scale.  
Five ranges



*Available NOW!*

## PHILIPS LOG DIAL

for easy, accurate, individual calibration

25/-

Specially designed for transmitting radio amateurs, short-wave listeners and equipment engineers, the new Philips "Log-Dial" is the ideal control and indicator mechanism for VFO (Variable Frequency Oscillator) Transmitter application, Amateur Band HF Receiver bandspreading, VHF Receiver tuning. Frequency Meters, Monitors and for many other radio and electrical applications.

The Philips "Log-Dial" mechanism provides positive, smooth running

with no slip or backlash. It has an ample reduction ratio for quick or slow tuning; calibration cannot be affected by mechanical troubles. The off-set Cursor provides instant logging without the need for scale reference or movement. The two-colour scale is removable and replacements are available. It may be mounted on front of or behind instrument panel. The Philips "Log-Dial" is designed for  $\frac{1}{4}$  inch shaft drive but is adaptable to larger sizes. It is finished in Florentine Bronze.

● The "Log-Dial" is available now from your nearest Philips branch; the price is only 25/- with special reduction for licensed amateur radio transmitters.



PHILIPS ELECTRICAL INDUSTRIES OF AUSTRALIA PTY. LTD.

Sydney • Melbourne • Adelaide • Perth • Brisbane

G23A



# COLOR TELEVISION FOR THEATRES

## IN DEVELOPMENT STAGE ONLY

Color television pictures on a  $7\frac{1}{2} \times 10$  feet theatre screen were shown publicly for the first time by Radio Corporation of America in a demonstration of its all-electronic color television system at The Franklin Institute, Philadelphia, on April 30. Color motion pictures, films and slides were projected with utmost realism.


**D**R. V. K. ZWORYKIN, who demonstrated the new system to illustrate his address on "All-Electronic Color Television," said that the large-screen system employs the all-electronic simultaneous method of color television developed at RCA Laboratories, Princeton, NJ.

However, it was emphasised that, remarkable as the advent of large-screen color television pictures appears, it must be regarded as still in the laboratory stage. Several years would be required for its development to the status of present black-and-white television.
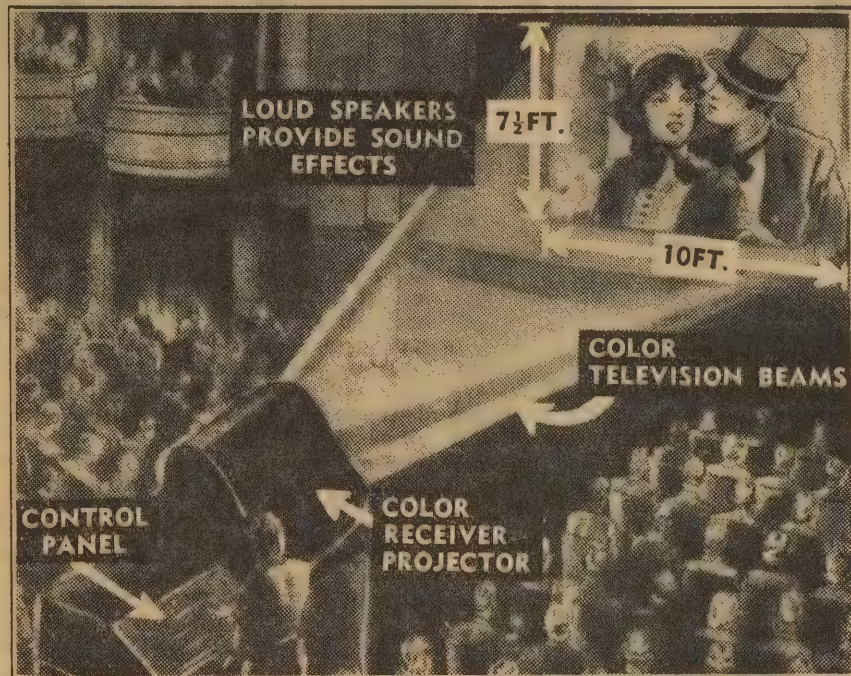
### SEPARATE IMAGES

In the electronic simultaneous color process, Dr. Zworykin explained, three separate images in red, green and blue are transmitted at the same instant over adjoining television channels of the same band-width as used in standard television.

Then at the all-electronic receiver, the three-color signals are applied to picture tubes, one with a red phosphor face, one blue and the other green. The flickerless pictures on the face



Large screen color television, as presented by the RCA electronic projector.

of each kinescope are projected by an optical system to the auditorium screen, where they are superimposed in perfect registration to form a single image blended in the same colors as the original.

Dr. Zworykin pointed out that color television is passing through a series of stages in its progression toward perfection. A great step was made when RCA developed the simultaneous all-electronic color system, which eliminated all mechanical parts and rotating discs.

"This system is completely compatible with existing monochrome television and has other important advantages,"

he continued. "The simultaneous color television can be made at a time in the future when color television is ready, without obsolescence of the monochrome receiving and transmitting equipment."

Dr. Zworykin disclosed that the pick-up unit used in the demonstration incorporated the electronic "flying spot" which has been under development for nearly ten years. In this system, the flying spot of light is created on the screen of the kinescope by the electron scanning beam.

The light from this spot is projected through color slides or films, scanning the entire surface of the scene or object, point by point. As the light beam, then tinted with color, emerges from the film or slide, it passes through a series of filters which separate respectively the red, green and blue portions of the color in the beam.


### PERFECT REGISTER

Each color then is reflected into photocells which change the light values into electrical signals for transmission to the receiver. The flying spot method, he added, assures perfect picture registration by permitting the transmission of the three color values of each picture element simultaneously.

Dr. Zworykin revealed that the special projection kinescopes used in this large screen color television system owed their brightness and effectiveness, in large part, to improvements achieved by RCA since development of the original kinescope.

"Some of these improvements such thing about the untidy little visitor as the design of electron guns to operate at higher voltages and to yield smaller, sharper dots, and the develop-

(Continued on Page 19)

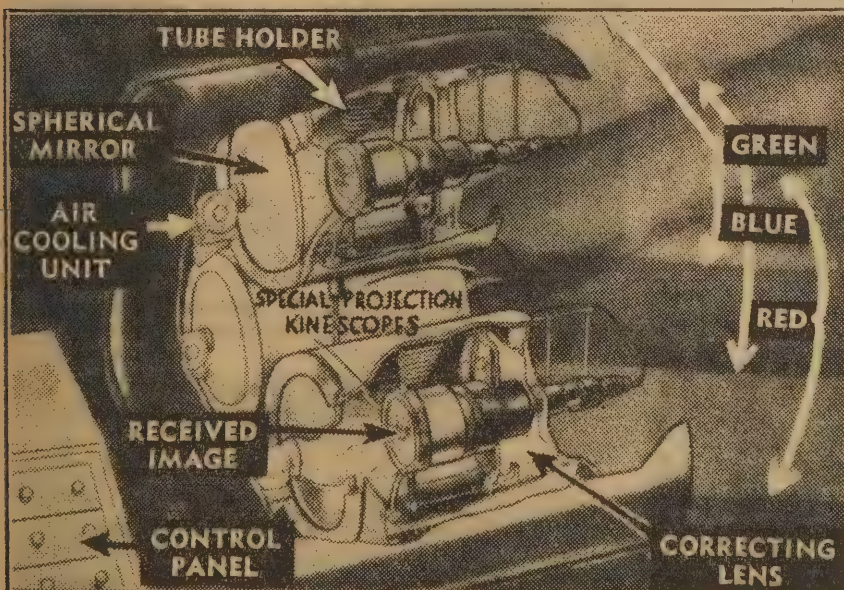

Showing how the three projection kinescopes are arranged within the large electronic color projector.





# REFRIGERATION

## *The Radio Serviceman's* BIG OPPORTUNITY!

Radio Servicemen throughout America and Great Britain have considerably increased their income and business by handling Refrigeration work as well as Radio. Here in Australia, Refrigeration is becoming more and more popular and even essential to business. Already it is a valuable source of income for those radio servicemen who have prepared themselves to handle Refrigeration service. Now is the time to study Refrigeration service and "Modern Electric and Gas Refrigeration" is undoubtedly one of the most outstanding and up-to-date text books on the subject.

## MODERN ELECTRIC AND GAS REFRIGERATION

By A. D. Althouse, B.S. Member of American Society of Refrigerating Engineers and C. H. Turnquist, B.S. Assoc. Member of American Society of Refrigerating Engineers. **OVER 60 EXTRA PAGES IN LATEST EDITION**

920 pages, over 400 illustrations (many in colour). This book is planned to serve as a text book in both domestic and commercial applications of modern refrigeration. All the common types of refrigerators, mechanism and their operation are covered and the relationship which exists between the types of systems and their construction and the parts within the system. Several coloured inserts are used to illustrate complete refrigeration cycles or portions of cycles of operations.

**CONTENTS:** Fundamentals of Refrigeration—the Compression System—the Absorption System—

Conventional Domestic Compression Cycle Refrigerators—Domestic Rotary and Hermetic Compression Cycle Refrigerators—Domestic Absorption Refrigerators—Domestic Automatic Controls—Domestic Refrigerator Electric Motors and Gas Supply—Domestic Refrigerator Cabinets—Domestic Refrigerator Installations—Domestic Refrigerator Servicing—Service Tools and the Refrigeration Service Shop—Commercial Refrigeration Cabinets and Mechanisms—Commercial Refrigeration Calculations and Heat Loads—Commercial Refrigeration Installation and Servicing—Refrigerants—Technical Characteristics—Air Conditioning—Domestic Refrigerator Specifications—Refrigeration Laboratory Projects—Answers to Review Questions—Index.



### FOUR BOOKS IN ONE

Covering: Basic Principles, Servicing, Operations, Repair of

1. Household Refrigeration,
2. Special Refrigeration Units,
3. Commercial and Industrial Refrigeration,
4. Air Conditioning Systems.

A gold mine of essential important facts for engineers, servicemen and users. Here you have at your fingers-end a complete library in one volume containing the necessary data you have been looking for on modern units, systems and machines, refrigerators including freon, lockers, water coolers, quick freezing and air conditioning systems.

### LIST OF CHAPTERS

Fundamentals of Refrigeration—Refrigerants—Compression Systems Compressors—Absorption Systems—Household Refrigerators—Refrigeration Control Devices—Service Tools and Their Use—Installation Methods—Household Unit Servicing—Cabinet Maintenance and Repairs—Electric Motors and Their Control—Refrigeration System Lubricants—Locker and Home Cold Storage Dairy Refrigeration—Grocer and Market Refrigeration—Ice Cream Cabinets and Soda Fountains—Drinking Water Coolers—Marine Refrigeration—Refrigeration Storage—Refrigeration Storage Operation—Commercial Refrigeration—Ammonia Plant Auxiliaries—Ammonia Booster Systems—Brine Systems—Circulating Pumps—Ammonia Plants, Erection and Operation—Ammonia Absorption Systems—Ice Making—Cooling Water—Standard Safety Code—Refrigeration and Air Conditioning Terms—Air and its Properties—Heat Transmission Through Walls—Development of Air Conditioning Ducts—Air Duct Design—Complete Air Conditioning System—Estimating Requirements for a Store—Est. Requirements for a Restaurant—Est. Requirements for a Home—Attic Fans—Railway Air Conditioning—Starting up a System—Servicing Air Conditioning Systems—Tables and Data.



- ★ 1280 PAGES
- ★ 46 CHAPTERS
- ★ 4 BOOKS IN ONE!
- ★ FULLY ILLUSTRATED
- ★ INDEXED FOR READY REFERENCE

CLIP AND POST TODAY

ORDER FORM

**ANGUS & ROBERTSON Ltd.**

89 Castlereagh Street, Sydney.

1. Please send me "Modern Electric and Gas Refrigeration," Price 38/6 (post 1/-).
2. Please send me Audel's "Refrigeration and Air Conditioning Guide," Price 26/- (post 9d.)

(a) for which I enclose payment (b) charge to my Account.

NAME .....

ADDRESS .....

(Tech.R.H. 10/47).



# REPORTER RADIOS NEWS PICTURE IN EIGHT MINUTES



Station wagon with mobile radio and picture-transmitting equipment installed.

Radio and wire circuits have already established themselves as a necessary means for conveying spot news photographs from the locale of an event to newspaper plants. Recently successful experiments were completed by the "New York Daily Mirror" in which prints produced in an automobile immediately after exposure were transmitted to the editor's desk in less time than the negatives could have been delivered by usual motor-cycle courier.

**T**HE picture equipment used at both terminals of the test radio circuit comprises a complete picture transmitter and receiver. Clear reproducible photographs up to 8 by 10 inches in size can be sent to any point in the network of stations.

In operation, the photo to be transmitted is wrapped around a cylindrical drum that is motor-driven and synchronised by means of a quartz-crystal oscillator with a comparable drum on the receiving unit. A phototube, scanning the picture in spiral

fashion at the rate of 90 rpm, translates the various shades of black, grey and white into electrical currents of varying character. These currents are processed and fed over the lines in the form of an 1800 cps. amplitude-modulated signal to the receiving unit, where they are inversely processed to produce the original picture. Transmission time for a 5in by 7in photograph is about six minutes.


The picture signal for the radio tests was fed to the output of a standard mobile f-m transmitter of the type used for police, taxi-cab, truck and similar service. Frequency of opera-

tion during the test was on 158.07 mc., with a total modulation swing of 40 kc., using the Armstrong phase system. The audio response of the equipment is essentially flat from 350 to 5000 cycles.

A thin flexible whip antenna, 18 inches long, mounted on the metal roof of the car served as the transmitting antenna.


At the fixed location conventional vhf. transmitter-receiver equipment was installed and connected to a temporary antenna with a power gain of three atop the building. This equipment was remotely controlled from the dark-room operating position several floors below.

Although the initial commercial installation will use a single fixed receiving location common to the talk-back transmitter, a much more extensive receiving system is considered necessary for eventual picture-transmission coverage of metropolitan New York. Probably as many as five separate locations at diverse points will be required to receive good pictures from outlying areas. At these points receivers will be in continuous operation and connected by telephone lines to the central operating post.

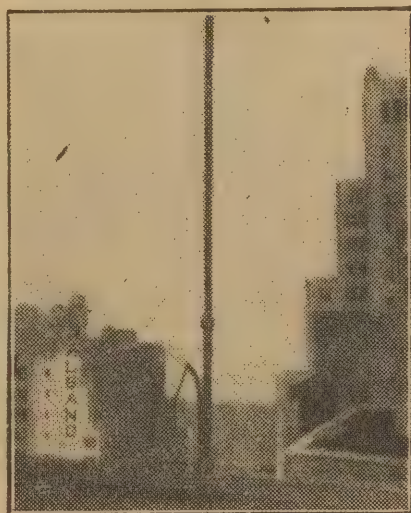

Temporary 152-162 megacycle antenna with a power gain of 3 erected on the building roof.


To further extend the system, portable receiving equipment can be parked near convenient telephone facilities and within receiving range of the mobile phototransmitter. The receiver will then serve as a relay point between the radio and wire links, making it possible to put news shots into the office of every subscriber in the continental network not more than fifteen minutes after the original picture is taken.

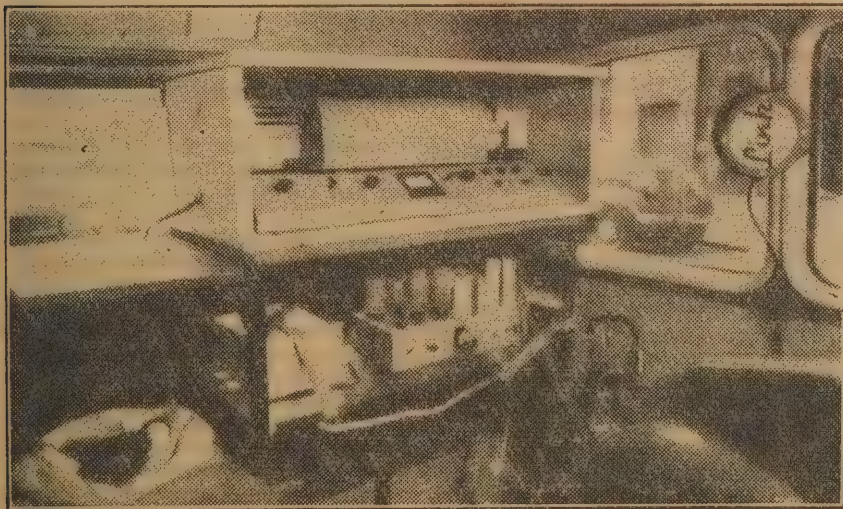

Interior of the Jeep station wagon. Standard mobile f-m communication equipment is on the floor. Immediately above are the dynamotor and picture frequency standard, with the sound-photo machine in a lead-lined box on the top of the table.



# PROBING SECRETS OF WHITE LIGHT

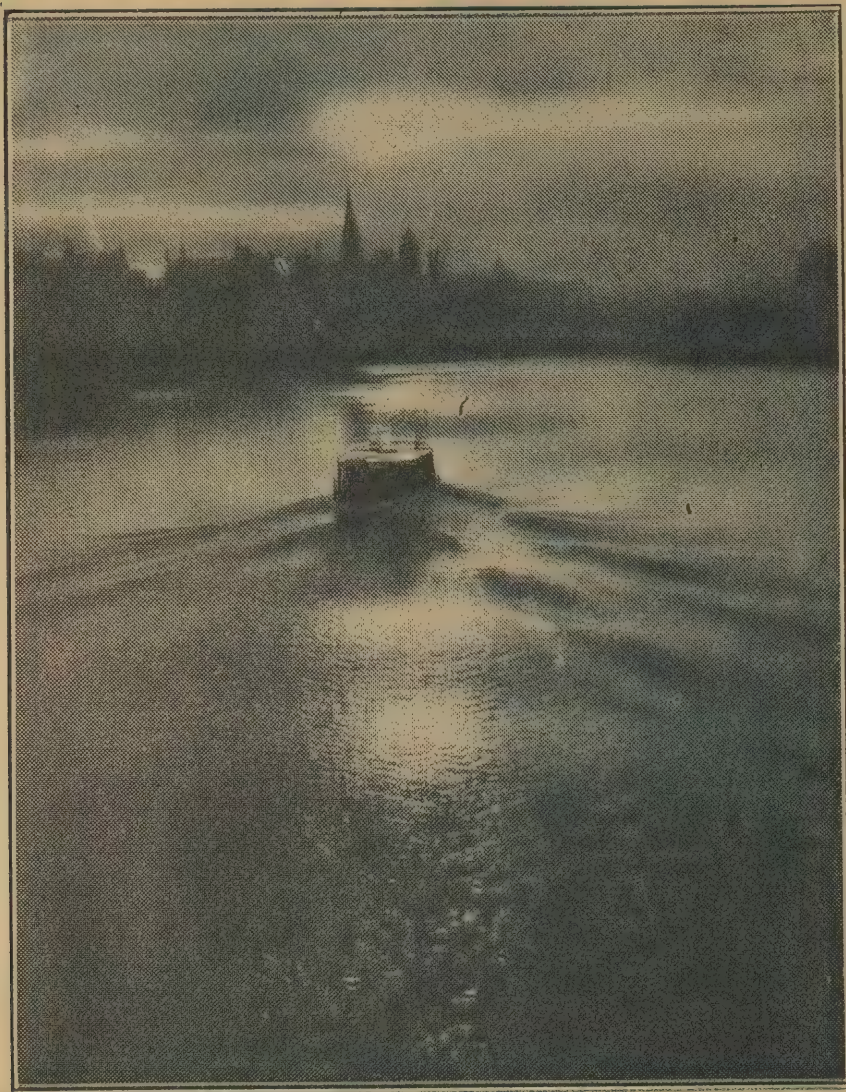

The increasing demand for color has brought into being a new profession called Color Engineering. During the last decade the practical use of color has gone beyond clothing, kitchens, furnishings and house painting, and entered the field of industry. The drab walls of factories have been replaced with pleasant colors, and the monotonous black of machinery has been superseded by gay greens, reds, blue and many other colors specially designed to relieve eye strain and fatigue.

The study of color is an interesting one. Of course this has hitherto been the domain of the decorator and the ladies. One sees in show windows and dressmakers' catalogues wonderful new names for colors.

## DOES NOT EXIST

Color is not actually a material thing. It does not really exist at all in nature as our eyes perceive it. This is hard, at first, to understand. To a lovelorn youth, the blue eyes of his lady love are very material things indeed, and to an irate wife, the glowing proboscis of her husband, who had lingered too long at the club, is real

enough. To tell either that the colors they see are only wave-lengths is to deprive them of one of their emotional outlets. It would certainly not be very romantic for a youth to announce: "Darling, your twenty thousand million wavelength eyes do such wonderful things to me," or the irate wife's anger would be somewhat dampened by having to say to hubby, "And look at your nose. It has so many million wavelengths it glows in the dark."

Yet that is exactly what color is. Red is not red until waves of a certain wavelength impinge on the retina of the eye, and the impulses set up in the optic nerves are translated

by the brain into what we see as red. The same holds for all other colors.

Light is due to waves set up in space. These waves are disturbances in the ether, and can be likened to the waves one sees in water. Just as the length of one of these waves is the distance from the crest of one to the crest of the next, so the wavelengths of ether waves are measured, as well as sound, which are waves set up in the atmosphere.

## VARIOUS WAVES

A distinction must be made between atmospheric waves and ether waves, the former giving rise to sound, and the latter to ether disturbances, such as light, heat, and electromagnetic waves, this last embracing radio waves. Ether waves are propagated without the necessity for atmosphere.

The number of waves which pass a given point in a unit of time determines the frequency of the wave train. The standard unit of time is one second, so that if a million waves pass a given point in one second, the wave is said to have a frequency of one million.

It has been experimentally demonstrated that waves exist of from a frequency of twenty million million to forty thousand million million, per second. As all these waves, except sound waves, travel at the same speed, namely, 186,000 miles per second, it follows that these waves must be extremely short from crest to crest.

Early sunrise on Melbourne's Yarra produces a wealth of color values which are really separated components of white light.

Within the range of ether wave frequencies given above, the eye is responsive to a comparatively narrow band, ranging from a frequency of 390 billion to 700 billion per second. But within this band there is an enormous number of frequencies, each of which has a specific effect on the eye in the production of color.

## LIGHT FREQUENCIES

White light consists of all frequencies in the visible range of 390 billion to 700 billion, impinging simultaneously on the retina of the eye. Thus, if white light is broken into its constituent frequencies by means of a prism or a spectroscope, we have a band of colors ranging from violet to indigo, blue, green, yellow, orange and red. These are the seven colors of the rainbow, which is also produced by white light being broken up by the prismatic effect of raindrops. The band of colors sometimes thrown on a wall by reflection of sunlight from a mirror is exactly the same seven colors.

In this band of seven colors we have the whole range of visible frequen-



# VALUE OF COLOUR IN OUR LIVES

cies, of which the extreme red is of a frequency of 390 billion, and the extreme violet is approximately 790 billion.

When we look at a rainbow we see before us the whole range of colors with which we are familiar. Combinations of these colors produce many more colors, and indeed closer examination of a rainbow will show that the seven main bands of colors are separated by many more shades, which merge from one band to another.

It was Newton who first opened the door to a knowledge of the behavior of white light, for it was he who discovered the spectroscope, and from whose researches our present knowledge is derived. When Newton discovered that a sunbeam consists roughly of seven varieties of visible light, he also discovered the fundamental basis underlying the phenomena of color.

## SELECTIVE ABSORPTION

What, then, causes various substances to appear in different colors? What is responsible for the gorgeous colors of flowers and fruits? The answer lies in what is known as the doctrine of "selective absorption." Simply put, this means that a substance possesses the property of being able to absorb entirely all but certain light rays lying within the visible spectrum, the other rays being reflected.

Observe a blue flower on which the sunlight is shining, or any other white light, for that matter. Since it appears blue, it is apparent that all the light rays corresponding to violet, indigo, green, yellow, orange and red have been somehow absorbed by the surface of the flower. The blue rays have been reflected to the eye with the consequent translation by the brain into a sensation of blue. The same principle applies to all other colors, no matter what the substance is which possesses the color. It may be a flower, a dye, a paint, or other substance.

The paper upon which this article is printed is white because ALL rays are reflected from its surface and none absorbed, the eye thus receiving an admixture of ALL rays. On the other hand, the ink with which the article is printed is black because it ABSORBS all the rays, and none are reflected from the surface to the eye. Simple, isn't it? (Or is it?)

This property of white of reflecting all rays is made use of in the painting of roofs in hot climates. White also reflects heat rays, and therefore roofs are painted white to gain the maximum of reflection. Black is rejected for the reverse reason.

## HUES AND VALUES

The color grey is produced when part of all rays are reflected and part absorbed. Colors differ not only in "hue," which is the difference between

red and blue, or green and yellow, and so on. They also differ in "value." This is the difference in two colors of the same "hue." It can also be called "intensity," such as red, carmine, vermillion and the multitude of other reds and the wide variety of greens, blues, and so on. This is due to the differences in the amount of light reflected. There is also the difference in "purity" of colors. This depends on the amount of greyness in the colors. Thus, adding white to any "hue" gives us tints, because it alters the amount of light reflected from the surface. In other words, the white, reflecting as it does ALL the rays, tends to overpower the rays coming from the "hue" and dilutes them, as it were. Adding black forms "shades" by increasing the absorption powers of the "hues."

## SUBJECTIVE COLORS

We have so far dealt with colors which have an objective reality because they result from the breaking up of white light by external objects. There are, however, certain "subjective" colors which are really tricks performed on us by a particular condition of the eye.

These tricks are caused by the eyes becoming color-weary owing to certain strains. For instance, there is the well-known optical illusion of gazing steadily at a red object for some time and then suddenly transferring the gaze to a white wall or paper. The image of the object will be seen upon the wall, but in a bluish-green color. This is caused by the eye becoming tired of the red rays emitted by the object, and thus is only able to see well those rays emitted from the white wall which are not like the red rays of the object. The bluish-green of the image on the white wall is said to be complimentary to the red.

If the original image had been any of the other colors of the spectrum, the complimentary colors seen would be as follows (the complimentary colors follow the spectrum colors):

by Calvin  
Walters

Violet and yellow, indigo and orange-yellow, blue and orange-red, green and reddish-violet, yellow and indigo, orange and blue, red and bluish-green.

One writer has reported that on gazing for a full half-hour at the flames of a house on fire he transferred his gaze at the moon, which appeared blue. It appears, therefore, that a "blue moon" can be a "subjective" reality. Probably "pink elephants" and "purple snakes" may be

explained in the same way. The practical application of the phenomenon of "subjective colors" in industry will be dealt with presently.

Transparent objects appear to be a certain color because of their ability to allow certain rays to pass through whilst rejecting others, so that a glass is red only when it allows red rays to pass through, and so with all other colors. By projecting light through glasses of various colors, various mixtures can be obtained with a great variety of colors, just as mixing pigments of various colors can produce other colors.

How does the eye see only one color from an admixture of several? The eye responds to any mixture of single colors which impinges on a single spot on the retina. The result is a sensation of a single color which may not necessarily resemble any of the colors in the original mixture. The retina of the eye contains nerves each of which has the property of being able to perceive one of the three primary colors red, blue or green.

## COLOR REACTION

Should the nerves sensitive to red and those sensitive to green be acted upon simultaneously, there will be produced, according to the degree and intensity of the "irritation," any color of the spectrum from red to green (through yellow and orange). Green and violet lights which are blended in different proportions will produce the intermediate blues. When all the three sets of nerves are acted upon simultaneously there is still a sensation of a single color or perhaps of white only.



Practically every instance of a single colored light is really an admixture of several single colors. This can be proved by passing white light through a green glass. Analysing this light with a spectroscope will reveal that what we really see as green light consists of not only green but also blue and yellow and may be red and violet. The resultant sensation is, however, one of green.

The writer has produced some wonderful effects for stage work by the use of different colored glasses. These project colored light on to a white background upon which is thrown shadows. The resultant effect is a wonderful display of kaleidoscopic colors of many hues. With three colored glasses many different colored shadows are produced. It is possible with red, green and blue glasses to produce shadows ranging through all the colors of the spectrum when the glasses are used simultaneously.
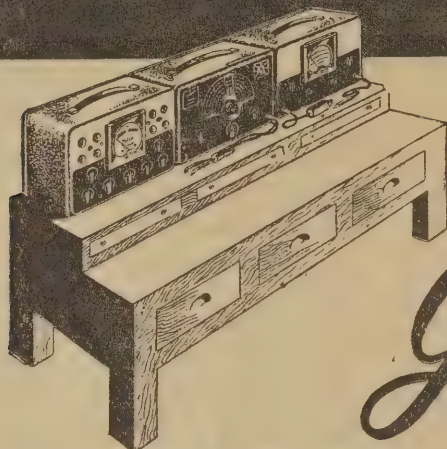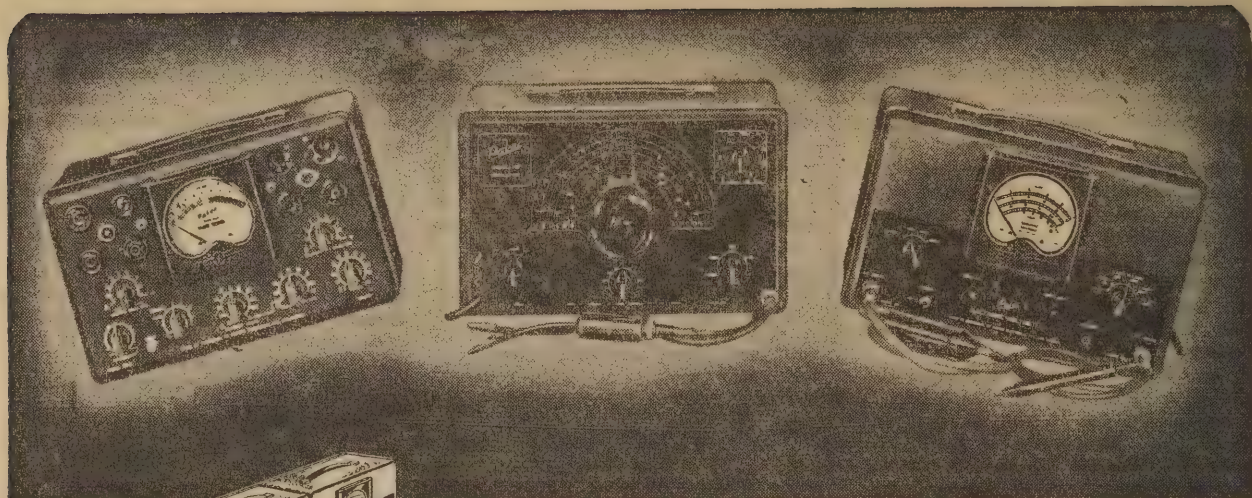
## IN INDUSTRY

The use of color in industry has its foundation partly in the phenomenon of "color tiredness" as mentioned previously. It has also been found that color of surroundings has a distinct effect on the apparent temperature of





THESE three essential units make an impressive showing and supply complete coverage for the quick and effective diagnosis of all radio problems. They also have the advantage of being individually self-contained and readily portable for outside service. Do more and better service in the competitive days ahead. Do it quicker, more profitably!

## Goodbye TO GUESSWORK!

### THE PALEC VALVE TESTER, MODEL ET-3

This compact, efficient valve tester, the latest model in the new series of Palec test instruments, is eminently suited for workshop, counter or portable use.

#### FEATURES:

**Good for years to come.** Selection of filament pins, irrespective of position on base, with full floating element selector switch—only one socket for each valve type necessary. Takes standard American valves, 7-pin button base and P and V Continental.

**Wide Heater Voltage Range.** Inbuilt filament transformer covers all filament voltages from 0.6 (deaf aid series) to 117 volts, catering for all overseas and local valves.

**Neon Shorts Test.** To conform with valve manufacturers' recommendation, comparatively low voltage is employed (50 volts max.) for this test. This prevents danger of short developing between grid and filament due to electrostatic attraction where normal striking voltage of the neon is applied to valve elements. Particularly applies to testing of 1.4 volt range of valves and is an exclusive feature.

**General.** Complete valve data booklet supplied, listing over 800 valves. Price: £19/10/6, plus tax.

### MODEL M.O. MODULATED OSCILLATOR

Range, 15 K/cs—30 M/cs in six direct reading bands. Vernier Dial 54:1 ratio, calibration accuracy 1%.

Has cathode follower to prevent frequency modulation and attenuator reaction.

Signal generator pattern attenuator of five steps: impedance 11 ohms on lower settings.

Triples shielding and adequate filtering ensures a leakage of less than 1 micro-volt at all frequencies.

Supplied complete with detachable dummy antenna, co-axial leads and 24-page instruction book.

Price: £32/17/6, plus tax.

**Note: Each of these instruments is A.C. operated, 200-260 volts, 50 C.P.S., and can be operated from a battery by using external vibrator unit.**

Price: £4/17/6, plus tax.

**All prices are nett trade and plus tax. Subject to alteration without notice.**

**Available at leading wholesalers in all States.**

### PALEC Model V.T.M. (Probe) MULTIMETER

Ranks as most versatile and valuable single piece of test apparatus.

Checks and tests all circuits, R.F., A.F., A.V.C., under operating conditions without disturbance.

Capable of quickly locating most obscure and elusive of intermittent, noisy, open or short circuits.

Checks all component parts and tests for high resistance insulation leaks.

Used with Model M.O. oscillator or equivalent, traces signal and determines stage gain in every channel from mixer to speaker.

**Note: Oscillator employed must have good attenuator characteristics. Ranges:**

(1) R.F.-A.F. six-range voltmeter: 0-2.5-10-25-100-250-1,000 volts A.C. Fitted with polystyrene bushed probe operating on frequencies up to 300 M.C. accuracy  $\pm 0.5$  db. to 100 M.C. Input cap., 10 uuf., loading equal to 6 megohms.

(2) High resistance D.C. six-range voltmeter: 0-2.5-10-25-100-250-1,000 volts D.C. Total load 11 megohms—giving over 4 megohms per volt on lowest range.

(3) Ohmmeter, six-range—from 0.5 ohms to 1,000 megohms.

Detachable co-axial leads, 20-page instruction book supplied. Employs 4 valves. Price: £29/10/6, plus tax.

**Palec Paton Electrical**  
PTY. LTD.  
Manufacturers of all types of Radio & Electrical Test Equipment & Meters

90, VICTORIA STREET, ASHFIELD, SYDNEY.  
Tele: GUA 1923-1980-1982. Telegrams: "Paton".

P.18.FP



rooms. In one factory the temperature was kept at 72 degrees, yet girls complained of cold. The walls were repainted a warm, coral color and the complaints ceased. Color also has an effect on apparent weight of objects. Boxes painted black were too heavy to lift, some operators complained. The foreman, on the advice of a color engineer, had the boxes painted a pale green over one weekend. On Monday, general approval was given the new "lightweight" boxes.

### STIMULATING RED

It is generally accepted that colors bordering around the red end of the spectrum are stimulating and those around the blue and green are cooler and relaxing. Telephone boxes when painted red have proved to be less tempting for long conversations than those painted sombre colors. Restaurants have had their turnover increased because their blue-green interior was repainted in red and yellow. The blue-green tended to cause customers to linger too long over their meals, thus limiting turnover.

In London, Blackfriars Bridge was painted black. The bridge was noted for its large number of suicides. The authorities, on advice, changed the paintwork to bright green and suicides decreased by over one-third.

It has been proved that red is the prime stimulator to action in sales requiring quick decisions. Thus an American petrol company increased the sales of its first grade petrol by painting the particular pump bright red. Sales increased by 50 per cent. All the other pumps were painted bright green and these also had increased sales, but only 15 per cent. greater.

### FOR FACTORIES

During the war color engineers in America developed complete color schemes for factories designed to decrease eye strain and increase production. Bodies of machines were painted light grey. Working areas cream. Ceilings are white and some walls are grey-green. Floors are sometimes buff or grey. Fire fighting equipment is of course red, while dangerous spots, such as low beams, edges of platforms and the like, are yellow striped with black. Electrical switch-boxes are blue.

This scheme has proved to increase lighting sometimes by as much as 100 per cent, increase production by over 15 per cent, accuracy by 40 per cent, and reduction of absenteeism by 60 per cent. One firm maintains that in 60 days it saved the cost of the painting in the recovery of small parts that were previously overlooked on the drab floor.

### SPECIAL PROBLEM

In textile factories where girls gaze at one-colored fabric for hours on end the painting of the walls white may have a detrimental effect. One American factory reported that after gazing at blue fabric and then raising their eyes to the white wall a peach color appeared before their eyes and it was several seconds before the girls could

## SCIENCE NOTES — BY PROF. A. M. LOW

### FAMOUS ENGLISH WRITER ON POPULAR SCIENCE

Not so long ago I happened to witness a number of fires all round me. It is interesting to think that by touring London at such a time with an instrument consisting of little more than a prism made from an old-fashioned chandelier or a cheap lens, one could estimate the nature of all the materials on fire.

**A**TMOSPHERE also contains minute quantities of other gases such as neon—you see its effect in modern lighting—and argon, a valuable gas used to prevent electric light bulb filaments from wastage at high temperature. All these materials are made from air by apparatus which, in itself, is a romantic story. Queerly enough, the microscopic quantities of rare gases in air help to keep us healthy!

### THINKING UP A POT OF JAM

You will have noticed from the Press, and therefore you will have known that it is true, that the energy in atoms must have been "put there," as it were, by the sun in its heat and, at its birth. Star dust is made more romantic by a little knowledge, and not less so, as has been said by people who do not grasp, fortunately, that scientists are as ignorant as anyone else.

We know, it seems, that matter can be converted into energy by a bomb, and we also know that in the preparation of the uranium family we can seemingly create a new element from "bricks," of which it is basically constructed. Call them electric particles if you prefer.

Now, if matter is energy at partial rest, and if energy can go through the ether, why not, in the vastly distant future, transfer material things by radio? The Betatron may be a beginning. An Atlantic flight was represented by a two-yard hop only yesterday in the realms of time.

More exciting still is it that thought also is energy. It even produces ether waves. I remarked long ago that I felt very small indeed beside the man of the few million, million years hence, who might look positively frightful with atrophied legs, artificial aids to everything, no hair and no teeth. But supposing he could think, a pot of raspberry jam across the Atlantic, that would be far more interesting than the best of bodies. As far as I am concerned at the moment it would be an extraordinarily desirable accomplishment.

I was amazed, as the headlines say, to find that every fire had a distinctive color. Due in some cases to dust or moisture in the atmosphere, but

usually, I think, to the materials concerned. Perhaps they were of interest to another world where peculiar people are saying, "They are lucky to have so much carbon in such convenient form."

I feel that the early savages who made fires by rubbing sticks together, a most trying business which seems to warm the person concerned more than the sticks, must have noticed the many colors achieved by their fires. Built on sand, these fires may have shown the yellow of sodium; built on rock, perhaps the green of copper. Every district must have had its own local characteristics.

### NO WONDER WE BREATHE

Breathing is a habit. A very good one, I imagine, but here is a very interesting thing, and this is about air. Of course it makes the green fields, we breathe it, and it is pleasant. But it is so much more than just "air." Aeroplanes fly in it, but without some of the queer substances it contains their manufacture might be slowed down by 30 per cent.

Air is mainly a mixture of 21 parts oxygen and 79 nitrogen. It was this nitrogen that saved Germany from a nitrate shortage in 1914, that might have slowed up production of explosives and fertilisers. Today, the separation of air into its various component gases has enabled almost every form of industrial and manufacturing process to be vastly speeded up.

Oxygen is a great "speeder up." There was a time when it was just used occasionally in hospitals to help sick lungs and hearts and to heal wounds. Now oxygen is one of the most vital tools known to the engineer. It welds, it cuts, builds gun mountings and salvages ships in a miraculous fashion.

Nitrogen, too, is almost as important. Unlike oxygen, it is a very lazy gas which never wants to join with anything else. So it can be used for preserving food. Just think what would happen in tinned foodstuffs if they were sealed up with air—rust, fermentation and waste. Not so when nitrogen is all around. Nitrogen, in a sense feeds the world in more ways than one, for, given good canning and dehydration, famines can be abolished.

regain their normal vision when again looking at the fabric. Color engineers solved the problem by painting the walls a peach color.


Much more could be said, if space permitted, about the effects of color on insects. How blue repels flies but

encourages mosquitoes. How barnacles in the sea are repelled by light green or white. However, enough has been said to encourage a greater study of color in our everyday existence so that our work will be not only more pleasant but safer and more efficient.



# YOU LITTLE BEAUTY!

## POLAR ENGLISH MIDGET CONDENSERS

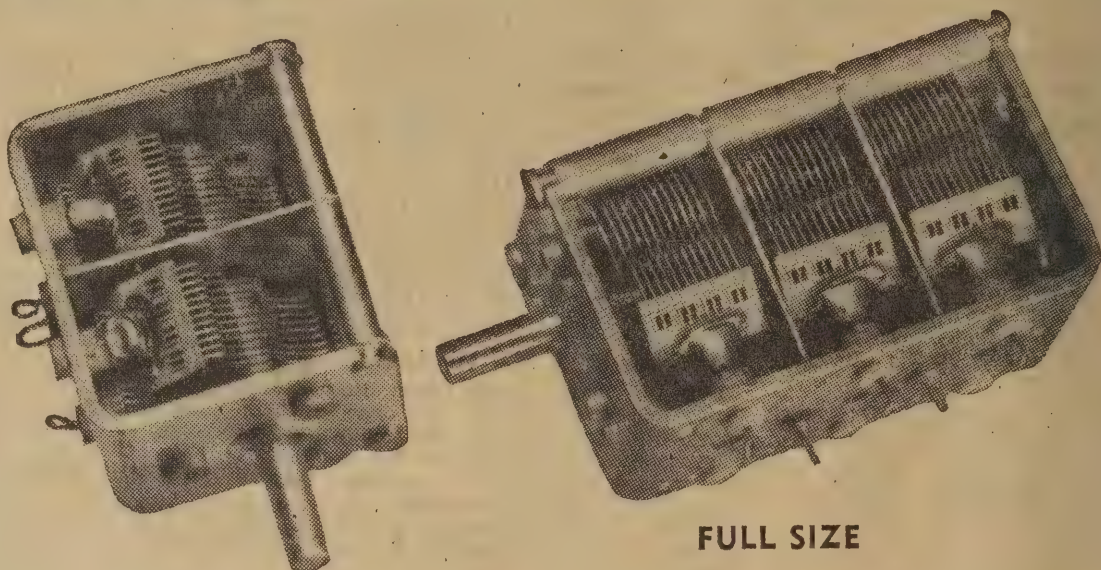


FULL SIZE

A REVELATION IN ENGINEERING DESIGN—2 GANG SIZE,  $1\frac{1}{2}'' \times 1\frac{1}{2}'' \times 2''$  DEEP—CERAMIC INSULATED—AIR DIELECTRIC BROAD CAST GANG—CAPACITY 363mmfd.

(3 GANG AVAILABLE THREE MONTHS)

## WEARITE MIDGET IFS

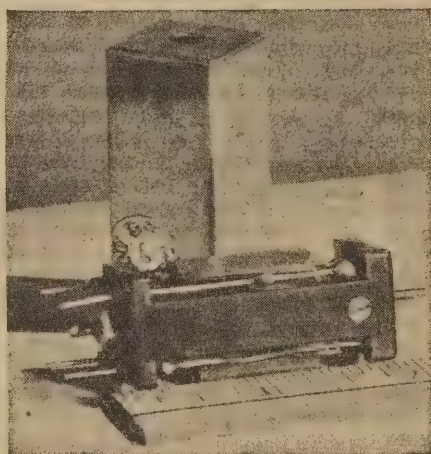

FULL SIZE


Designed for maximum gain and selectivity in smallest dimensions

TOTALLY  
ENCLOSED  
IRON  
DUST  
CORES  
SIZE

•  
 $13/16'' \times$   
 $13/16'' \times 1''$

•  
TROPIC  
PROOFED

•  
460 kc

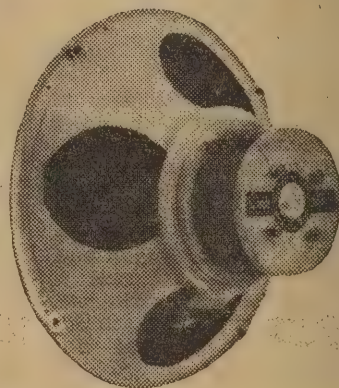

GOODMAN'S SPEAKERS

12 inch — 15 inch — PERMAGS

Goodman's speakers are the ideal reproducers for small cinemas, public address or high power radiograms. Anywhere quality, wide frequency response is required, use a Goodman's speaker.

## UNITED RADIO DISTRIBUTORS PTY. LTD.

RADIO-ELECTRIC

SHOWROOMS: 175 PHILLIP STREET, SYDNEY.

TELEGRAMS & CABLES: URD SYDNEY.



WHOLESALE

OFFICES: 183 PITT STREET, SYDNEY.

TELEPHONES: MA9251, MA1563.



# ERA OF PUSH-BUTTON TELEGRAPHY



**PUSH-BUTTON TELEGRAPHY.**—In the field of telegraphy, it is only natural that electrical devices should gradually replace other methods of doing jobs with a consequent saving of time and labor. An example of this process on a large scale is seen in the Philadelphia offices of Western Union when a new system costing about £750,000 was introduced by which push-button control takes the place of old-fashioned routing of messages.

Tripling the capacity of present wire systems, the new method relays messages to any of 270 points with the pushing of a button. Now in partial operation, push-button telegraphy will operate fully this month. It is the first of a series of such systems to be set up across the country. Under the old system, outgoing messages are sorted by routing clerks and carried by roller-skated girls to operators, who send the telegrams from their typewriters—like keyboards. The new system eliminates these steps. Each message is typed just once, at the point of origin. A printer perforator simultaneously prints the message and punches holes in a paper tape. A button is pushed, the tape runs through an electrical transmitter, and the message comes out in printed form at its destination, ready for delivery.

Picture shows operators at work at the new push-button boards in the Philadelphia Centre.





## *The Perfect Employee*

AVO measuring Instruments give you just the qualities you would like in your employees. Precision perfect and famed the world over for accuracy and ability to withstand rough usage, AVO gives the widest range of precision application possible and therefore represents the economical instrument buy to mechanic and engineer alike. Compact and portable AVO is worthy of your fullest investigation.

### WRITE FOR DETAILS OF FULL AVO RANGE

- MODEL 7 AVOMETER—50 RANGES
- MODEL 40 AVOMETER—40 RANGES
- AVO TEST BRIDGE—50 CYCLES
- ALL WAVE AVO OSCILLATOR
- AVO VALVE TESTER
- AVO MINOR-POCKET METER

### INTERSTATE REPRESENTATIVES

Q'LAND: C. F. WILLERS, 36 EAGLE ST., BRISBANE. S.A.:  
 NEWTON, MCLAREN LTD., LEIGH ST., ADELAIDE. VIC.:  
 E. R. CORNISH, 408 COLLINS ST., MELBOURNE; A. E. SUPPLIES  
 LTD., 486 COLLINS ST. TAS.: ELECTRONIC SUPPLIES LTD.,  
 94 LIVERPOOL ST., HOBART. W.A.: CARLYLE AND COM-  
 PANY, 915 HAY ST., PERTH

# AC-ELEC PTY LTD

INCORPORATED




Harbert St., St. Leonards, N.S.W.

P.O. Box 29, Crow's Nest, Tel. XF1042.



# BRITAIN HAS THIS FLYING TORPEDO

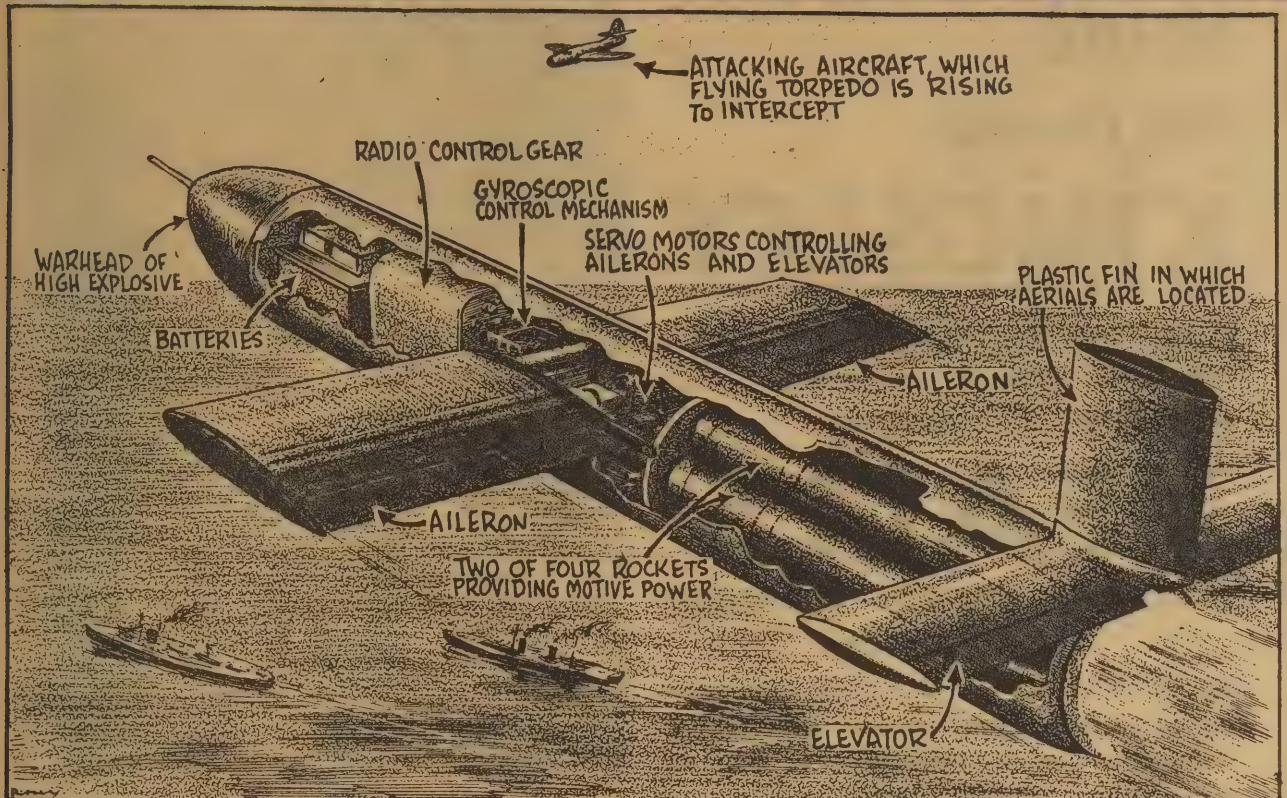

A pilotless rocket-powered "flying torpedo" that can be directed by radio control to intercept an attacking aircraft has been developed in Britain. Some details of the device were revealed recently when it was announced that the "flying torpedo" had successfully completed a full range of flight trials.

**T**HIS missile, the first British device of its type, is in many ways a development of the German V-1 flying bomb. It is, however, operated under direct radio control, and not by predetermined gyroscopic control.

Designed and developed by the Fairey Aviation Company, the "flying torpedo" is of orthodox monoplane design. The stub wings are placed almost half-way back along the length of the circular fuselage, which contains warhead, batteries for power for radio and gyroscope, motors that operate control surfaces, and rocket tubes.

For take-off, the missile is mounted on the rails of a ramp of light metal structure. The 10ft. launching cradle can be assembled by four men in less than a minute and a half.

To assist in giving the maximum initial speed, four booster rockets are fitted externally, mounted in pairs on each side of the fuselage.

After a second and a half of flight, the boosters are jettisoned by small explosive charges and the projectile continues on its way under its own rocket power. The four rocket tubes are each five inches in diameter. They feed their exhaust gases through a venturi tube to the rear nozzle.

Remote flight control is exercised by moving a "joystick" mounted in a control box on the ground or aboard

ship. A radio transmitter linked to the box relays "messages" as signals on set frequencies, and these are picked up by the radio equipment in the missile, where they activate servomotors operating the control surfaces.

The control surfaces of the "flying torpedo" consist of ailerons on the wings and elevators on the tailplane. Full flight control is maintained by these surfaces and the fin has no rudder attached.

The projectile is 7ft. 6in. long and its wingspan is just under 7ft.

This "flying torpedo" is a variant of

the "Butterfly" experimental rocket developed by the Germans in the latter stages of World War II. It was designed to trail down aircraft by means of its acoustic "ear" and "radio eye."

It was to be fired into the area of attacking planes. Radio waves were emitted and their echoes from any object within range were picked up by the sensitive mechanism. Control surfaces operated in accordance with wave echoes received, so that the 600-miles-an-hour missile might follow its quarry and strike it down, despite any evading action the plane might take.

## COLOR TELEVISION IN THE U.S.A.

(Continued from Page 9)

ment of efficient phosphors, with a wide range of color, have been practically continuous," Dr. Zworykin said. "Other important contributions of relatively recent date, are the use of metal backing for the fluorescent face of the tube and the utilisation of an improved optical system.

Television of theatre-screen size in life-like colors represents "a spectacular advance in the art of sight-and-sound broadcasting, and holds fascinating prospects for the future," declared E. W. Engstrom, who co-operated

with Dr. Zworykin in the Philadelphia demonstration.

Revealing the next big step to be expected in the evolution of color television, Mr. Engstrom said that cameras and other necessary apparatus are being developed at the laboratories, which will enable a demonstration of color television featuring outdoor scenes in motion.

In looking to the future, Mr. Engstrom said that it is the plan of Radio Corporation of America to perfect color television in such a manner that ultimately it will take its place alongside the RCA all-electronic black-and-white television system.



# BUILD YOUR OWN RADIO RECEIVER USING

THE FAMOUS

# KINGSLEY

FERROTUNE FOUNDATION KIT

AND WITH THE HELP OF

# VEALLS'


TECHNICAL EXPERTS TO SOLVE  
YOUR PROBLEMS

- VEALLS can supply all the necessary components to build famous KINGSLEY Kits, from the Speaker down to the last nut and bolt.


VEALLS Technical experts are gladly at your disposal to solve any of your personal perplexities in building up a Kingsley Kit.
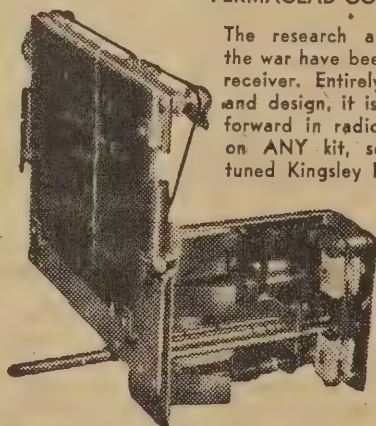
## "KINGSLEY" KITS

FERROTUNE GANGLESS FOUNDATION KITS.  
PERMACLAD COMPONENTS.



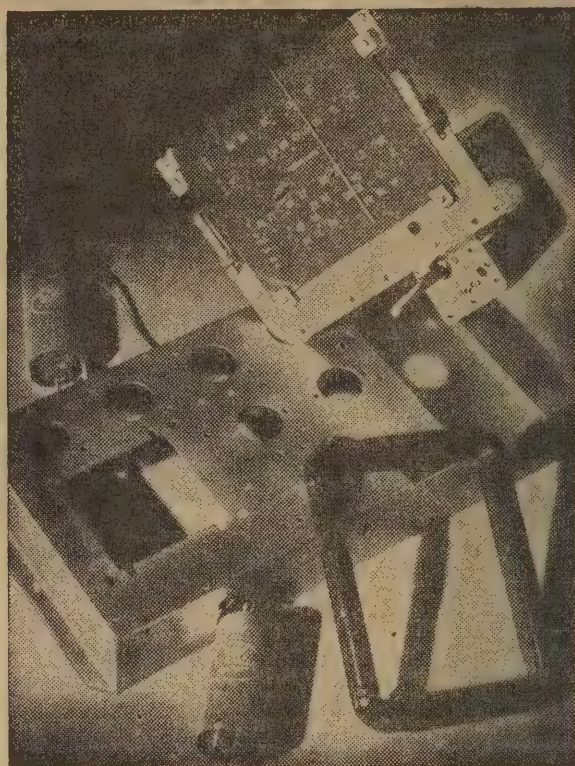The research and developments of the war have been applied to this new receiver. Entirely new in conception and design, it is a revolutionary step forward in radio. Before you decide on ANY kit, see the permeability-tuned Kingsley Kit.



## Kits Available For Immediate Delivery . . .

- ★ **MODEL K.F.T.1. COMPLETE**  
5 VALVE B/C SUPER HET. REC.  
PRICE . . . . . £12'8'1  
(Valves and Mantel Cabinet extra).
- ★ **MODEL K.F.T.2. COMPLETE**  
3 VALVE REINARTZ REC.  
PRICE . . . . . £8'9'5  
(Valves and Mantel Cabinet extra).
- ★ **MODEL K.F.T.3. COMPLETE**  
3/4 VALVE MANTEL REC.  
PRICE . . . . . £10'15'9  
(Valves and Mantel Cabinet extra).

**For Anything in Amateur Radio . . .  
It Pays To Consult VEALLS First !**

# VEALLS

ELECTRICAL & RADIO PTY. LTD.  
TEL. FJ3145

Head Office: 490 ELIZABETH ST.  
MELBOURNE

Telegrams  
"VELRADIO"

BRANCHES AT 243 SWANSTON STREET, MELBOURNE AND 299 CHAPEL STREET, PRAHRAN, VICTORIA.



# NEWS AND VIEWS OF THE MONTH

THE results of the Atlantic Convention which decides what frequencies shall be used for the world's services during the next five years are slowly seeing the light of day. Most of the decisions are of indirect interest only to the general public. To our readers, the decisions concerning amateur bands are probably the most important, for although the entire amateur fraternity represents only a small fraction of our total readers, many of the remainder listen to amateur activity at one time or another.

So far, the only change which seems definite is the lopping of 50kc from the end of the 20 metre band, making it 14mc., to 14.350mc., and the sharing of the section 14.250-14.350kc., with the Russians for their own internal or domestic use. Just what this latter provision amounts to is not clear, but there it is, and despite the worthy efforts of amateur organisations there it will probably remain.

## A NEW BAND

There may be a small curtailment on the 3.5mc. band which isn't likely to be serious, but there is a very definite prospect of an entirely new band 450kc. wide in the vicinity of 21mc. We don't like to see any of the recognised frequencies of the amateurs curtailed, and wish those who hope to restore the cuts every success. But even if they remain, we can't see that the final reshuffle is nearly as bad as many would imagine.

The 100 kc. allocated to Russia is an unknown quantity, although if the American high powered stations work

in that region, it's hard to see what use it would be to anyone else. It is almost certain that this will happen, as the Americans are very sore about this aspect of the business. But the new band is likely to prove more than a compensation, and no doubt this view was held very strongly when the cuts were allowed.

Listeners to 13 and 16 metre overseas' broadcasts are familiar with the fine signals which are to be heard when these bands do "open." It is likely that 21mc. will exhibit many more inconsistencies than the 14mc. band, but this in itself, will give an added interest to its use. It is near enough to 14mc. for much the same general techniques to apply, and receiver and transmitter efficiency should be quite easy to obtain. Also it is in harmonic relationship with the other bands lower in frequency.

## BE OPTIMISTIC

So although we are sympathetic with those, and regret the treatment they have received, we are by no means of the view, that our familiar DX, particularly on phone, has been ruined. On the contrary, we expect the new band to greatly relieve the congestion now apparent on 14mc. It may, when considered as "stations per kilocycles," actually leave us better off than before.

So don't be too gloomy, fellows, until you have a chance to try it out. It may prove to be a blessing in disguise.

Incidentally, there is also a rumor that the 50-54mc. band will give place to the older 56-60mc. band, as in pre-war days. This is relatively unimportant as a change, although it probably means that the UHF DX won't

## RADIO CROSS-WORD PUZZLE, No. 2.

### ACROSS

1. Perspire.
4. Code.
9. Units of capacity.
11. Unit of current.
12. Channel (Med.).
13. Small particles.
15. One million times the unit.
16. These step up voltage.
18. Transmitter component.
21. Type of frequency.
22. Type of armature winding.
23. Value.
25. Put in tune.
26. Good conductor.
27. Wire shielding.
28. Viper.

### DOWN

2. Collection of conductors.
3. Used for hearing.
5. Units of resistance.
6. Device for sowing seeds.
7. Attach.
8. Device for opening and closing circuits.
10. Arc denoting rise and fall of voltage.
11. . . . Volume control.
14. Bristle.
15. Electrical machine.
17. Attempt.
18. Be of importance.
19. Type of voltage.
20. Market place.
23. . . . Capacity switch.
24. Across a generator.

## BELOW:—LAST MONTH'S SOLUTION

R	E	V	E	R	B	E	R	A	T	I	O	N
E				O				M				E
C		C	A	B	L	E		P	U	P		G
T		O		O		L		L		U		A
I	N	E	R	T	I	A		I	N	P	U	T
F						N		F		I		I
I		A	R	E	A			A	Y	I	N	V
C		T		L		E						E
A	N	O	D	E				D	I	S	T	R
T		M		C				I		O		M
I		S	E	T				T	U	N	E	S
O				R				I				E
N	O	N	C	O	N	D	U	C	T	O	R	S

	1	2		3			4	5		6		
7												8
9						10		11				
					12							
13				14						15		
			16									
17		18								19		20
21										22		
						23			24			
25								26				
	27								28			



YOU WAITED FOR IT!  
HERE IT IS! THE NEW

# SIGNAL TRACER!



ANOTHER "FIRST" FROM *University*

## WHAT IT IS...

It's a Signal Tracer—the most versatile and fool proof instrument that has ever been designed for speedy and economical radio service work and general fault finding. It is built into an attractive brocaded steel case with a leather carrying handle and all necessary test leads and instructions are supplied. It embodies one of the famous "University" four inch square meters together with a new  $3\frac{1}{2}$ " permagnetic speaker. Standard type easily replaceable batteries are built internally and a book of instructions explains the uses and shows how signal tracing is the latest up-to-date method of service work. You hear the signal in the speaker—and you see the signal on the meter.

## WHAT IT DOES...

Spearhead of this most efficient instrument is the probe. This is a bakelite moulding into which is built one of the new bantam type valves. It actually traces the path of the signal RIGHT THROUGH the radio receiver from START TO FINISH. It can be used just as effectively on amplifiers or intercommunication systems and will give the same effectiveness and speedy service. When the probe strikes the faulty section, indications are given by the meter and speaker both. It will indicate clearly and easily faults in coils, condensers, intermediate frequency transformers, components, as the signal is traced.

This is the instrument you MUST have—a necessity in every place where radio work is being done. Quantities are limited, so place your order early. Ask for model S.T.B. "University" Signal Tracer.

## WHERE TO SEE IT...

N. S. W.: John Martin Pty. Ltd., George Brown & Co. Pty. Ltd., Fox & MacGillcuddy Ltd., Bloch & Gerber Ltd., Dominion Factors Pty. Ltd., Electronic Parts Pty. Ltd., VICTORIA: Veall's Electrical & Radio Pty. Ltd., Replacement Parts Pty. Ltd., Hartleys Ltd., John Martin Radio & Electrical, J. H. Magrath & Co., Arthur J. Veall Pty. Ltd., QUEENSLAND: Chandlers Pty. Ltd., Irvine Radio & Electrical Co., Trackson Bros. Pty. Ltd., A. E. Harrold. SOUTH AUSTRALIA: Gerard & Goodman Ltd., Radio Wholesalers Ltd., Unbehau & Johnstone Ltd., WESTERN AUSTRALIA: Atkins (W.A.) Ltd. TASMANIA: W. & G. Genders Ltd. NEW ZEALAND: Allum Electrical Co. Ltd.

Price  
**£14.0.0**  
Plus Tax

Made by

**RADIO EQUIPMENT PTY. LTD.**

5 NORTH YORK ST., SYDNEY  
Phones: B3678, B1960, M6391.



be as easy to achieve as formerly. Even this point, however, has yet to be demonstrated.

While on the matter of amateurs, there is a point we have felt strongly about for some time, in conjunction with many others who like to hear good operating.

It concerns the use, or rather the misuse of VFO's by many stations on 7 and 14mc.

It is a grand thing to have control of frequency in such a manner that one can move accurately to any spot in the bands. When working another station, it is economical in channels to move over to his frequency, thus in effect, doubling the number of channels which can be used.

But the practice of using the VFO to break in on another man's QSO, as we have heard so often in recent months, is, apart from being bad operating and against regulations, more often than not, sheer bad manners.

On one occasion recently, we were listening to a number of stations operating as a 'network, where this breaking in 'on each other' transmissions with snappy remarks was carried to such a pitch that at one time four stations were trying to talk at once, none of them being intelligible.

What possible good such bedlam can do, is hard to imagine. The effect on the general listener is far from happy. We must remember when we talk of the general public's reaction to amateur radio and its doings, that our transmissions are our best advertisement — our shop window. It's a mighty poor advertisement to fill the air with such twaddle, presented in such a manner as to create an almighty jumble and etheric chaos.

Use a little more thought, fellows, and clean up this poor operating. It isn't necessary, and it's illegal. You'll raise the prestige of your own station by so doing, and even guard against receiving the wrong kind of ticket when the authorities get fed-up with this state of affairs. The Atlantic Convention is surely sufficient reminder that we must be able to prove our worth and fitness to use the bands before what amounts to an International Tribune. Don't be one of those who bring amateur radio into disrepute.

#### F.M.—OFFICIAL

THERE are no immediate prospects of frequency modulation broadcasting being introduced into Australia to replace the existing system.

This statement was made officially by the Postmaster-General (Senator Cameron) who said that despite a forecast which had been made in a recent National news broadcast concerning FM broadcasting, several years would elapse before this system could supplement, much less replace, existing stations. The wireless sets at present used by listeners, of whom there were 1,700,000 in Australia, were incapable of receiving FM transmissions and, even if it were decided to introduce the FM system, a duplicate broadcasting service would have to be maintained over a very long period until virtually all listeners had obtained suitable receivers.




TYPE BT  
*Metallized*  
INSULATED
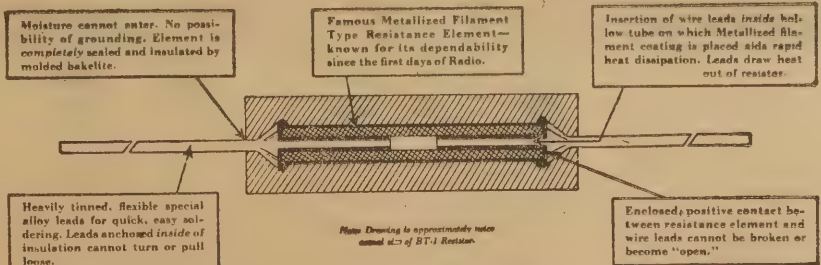
# RESISTORS



The Type BT Resistor, with its many superior features and special practical advantages, is the final result of more than twenty-three years of intense research and development work on the part of IRC engineers.

The time-tried Metallized filament principle is retained, but the ingenious construction, firmly based upon sound engineering principles, insures low operating temperatures with proportionately higher wattage dissipation in a conveniently small, sturdy, light weight, fully insulated unit with an exceptionally low noise level.



Available in  $\frac{1}{2}w.$ ,  $1w.$ ,  $2w.$  sizes

Sole Agents for Australia:

## Wm. J. McLELLAN & CO.

BRADBURY HOUSE, 55 YORK ST., SYDNEY • PHONE 5X7505






Here is the set you've been wanting for years—a real baby personal portable—a regular 5-valve superhet, loop aerial and all, not much bigger than our paste-pot! We have all spent many hours on its layout and production—we believe it is the only 5-valver of its kind available in Australia, and actually smaller than similar 4-valve sets. In the heart of our big city building, it will play all the locals at good strength. At night, particularly if you plug in an extra aerial, you'll hear all Australia. All the parts came from a regular radio store, and we have fixed the supply of chassis and cabinets. So you can build one just like it in time for your picnics, cricket matches, and summertime outings. Just push the battery switch and hear him go!



# A FIVE VALVE "PERSONAL" YOU CAN MAKE

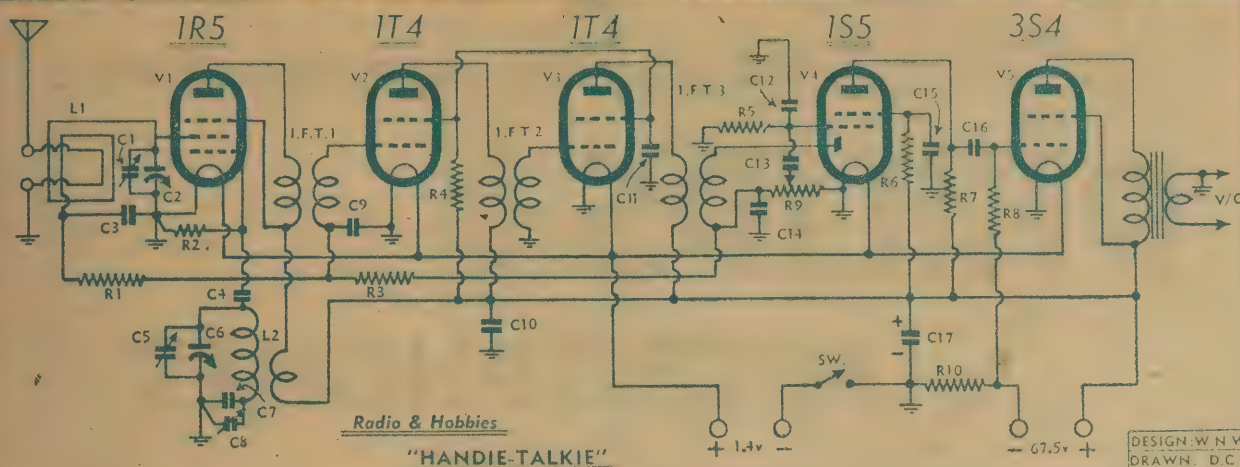

DESIGN: W.N.W.  
DRAWN: D.C.S.  
DATE: 9-9-47

AS with most of our sets, the 1947 "Handie Talkie," as we have chosen to call it, has quite a personal background. We have naturally been aware of the keen reader interest in miniature portables but had not been able to do much about it for lack of suitable components.

There was also some doubt in our mind as to whether miniature sets were really a proposition for home construction. One can tolerate a few liberties when there is a square foot of chassis to spare, but it is a very different matter when substantially the same number of components have to be fitted into a fraction of the space.

Our misgivings on this score were largely dispelled by the reception accorded "Tom Thumb" in the August issue. Not at all worried by the miniature parts and construction of this little regenerative set, many readers went right ahead and built it up exactly as we had described it.

The circuit as will be seen is particularly simple. There are no complexities—only a few points to watch in the layout when positioning the parts. The smaller the set, the more important it is to see that key components are mounted in the right place. The text will tell you all about it.

Then, to cap it all, limited stocks of the long-awaited button-based valves were released, with suitable sockets.

We could still see possible shortages, but the decision was inevitable. Shortages or no, we must have a new miniature portable.

## PROJECT COMPLETED

By the time you read this you should be able to buy a new chassis and cabinet specially made for the job, together with a dial plate and knobs to match. A fortnight's work, plus midnight oil and aspirins, turned the idea into a completed set, photographs, article and all.

The photographs don't show the set to full advantage. The prototype

little hint of the physical form it must take. You will note that it uses a 1R5 converter, two 1T4 IF amplifier valves, a 1S5 diode-pentode and a 3S4 output valve.

The omission or otherwise of an RF stage is dictated very largely by the supply position of three-gang miniature condensers and the simple truth is that there are very few available. A tuned RF stage in a portable receiver is a very good thing, both for gain and signal-to-noise ratio, but it obviously could not be considered in the light of the parts position. And an untuned RF stage is of doubtful value.

So our resonant loop aerial feeds straight into the grid circuit of the 1R5 converter. We thought carefully about the idea of a tuned loop in rela-

# Handie-Talkie

Then a few other things began to happen. August brought to light the heaviest mail we have ever had to cope with, and a big proportion of the letters had some reference to the need for a new miniature portable.

## SMALL PARTS

A local manufacturer came to light with a small two-gang condenser similar in dimensions to a couple we had seen from overseas. Small loop aerials made their appearance, and tiny oscillator coils. Imported miniature IF transformers were seen on dealers' shelves, and there was talk of them being produced locally.

cabinet was produced very hastily with hacksaw and file and photographed with the paint still "tacky." The dial plate is the right size and shape, but boasts only a few hand-painted figures instead of a properly printed scale. Even the knobs aren't the right shape, but the set has plenty of "oomph" just the same.

Quite a few trade identities have seen the set and their reaction has been the same. "It's a winner"—"Best thing you've ever turned out."

But enough of all that. Let's tell you about the works.

The circuit diagram is very much like any other battery set and gives

tion to other methods. One idea is to have an untuned low impedance loop comprising two or three turns around the outside of the case. A neat scheme, but it does require a specially tapped aerial coil, which we had no time to organise. Another difficulty is that of camouflaging the wires wound around the outside of an otherwise finished cabinet.

## STRAP AERIALS

Aerials in the carrying strap are another possibility. Here, again, special components are desirable and a long strap aerial is just as likely to be a nuisance as an asset. These schemes



The essential background  
to quality reproduction

# PHILIPS MICROPHONES

**DX** communication is the Radio Amateurs' most popular enjoyment, and for certainty of voice identification at extreme distance the type of microphone is important. Emphasis of the higher speech frequencies is required to "cut through" during interference and conditions of selective fading. Too much reproduction of lower audio frequencies can result in difficulty of reception by that DX station. Philips microphones are designed to suit the special requirements of the transmitting Radio Amateur.

The microphones illustrated, and also type 9535R (a general purpose crystal microphone), are available now from the Philips Office in your State.

**828.** A highly efficient, modern, streamlined, dynamic microphone, fitted with shielded plug and socket and supplied complete with 25 ft. of shield cable and stand . . . £8/11/6 (inc. tax) or without stand, £8.

**830.** A deskstand unit of modern, streamlined design, complete with "press to talk" switch, giving push button control of the microphone circuit and providing muting when required. Price, £8/10/- (inc. tax).

**9532T.** An excellent general purpose hand microphone with a wide range of applications, especially for mobile work. The diaphragm is of metal construction, extremely rugged and free from temperature variations. Price, £10/18/6 (inc. tax).



**PHILIPS ELECTRICAL  
INDUSTRIES OF AUSTRALIA PTY. LTD.**

SYDNEY • MELBOURNE • ADELAIDE • PERTH • BRISBANE  
S11-47.



were accordingly shelved for future reference and reliance placed on the well-proven tuned loop.

To ensure high gain in the set we elected to use two IF stages. These are operated with very low screen voltage, however, and actually draw only a fraction of the high tension current of a single stage operating under maximum conditions. There is an extra .05 amp of filament drain, of course, but this is not of vital importance.

A 1S5 operates as a diode detector and pentode audio amplifier, with a 3S4 as output valve.

In a circuit of this nature, the important thing is naturally to keep the number of components to an absolute minimum, since every additional part makes a call on the very restricted space under the chassis. Thus, the screen and oscillator plate of the 1R5 operates from the full high tension voltage, with a single 0.1 mfd high tension bypass. We tried a .01 mfd mica condenser in this position, but the effect was not quite adequate to suppress regeneration. Use a small 200-volt condenser or you will never fit it in beneath the chassis.

## BACK BIAS

Back-bias is provided for the output valve to obviate the need for a C battery, and an electrolytic condenser becomes necessary to prevent a degenerative effect. We chose to use an 8 mfd condenser between B-plus and chassis, where it is also useful under conditions when the B-battery is very run down. We found that the set operated quite satisfactorily with a 67½-volt battery delivering less than 45 volts.

Once again, it is absolutely essential to use one of the new midget 8 mfd condensers which are now available, and to avoid any condenser of doubtful quality. The condenser is connected right across the high tension supply and can impose a harmful bleed on the B-battery. In the original set no initial drain could be detected through a 1.0 milliamp meter, so we had no apprehensions, on that score.


Even so, it is good practice to disconnect the B-battery during long periods of idleness to avoid any possible bleed current and to avoid having the high tension voltage permanently in circuit. The ideal would be a double pole switch, but we had no hopes of finding one small enough for the job.

## THE CIRCUIT

A dropping resistor is necessary for the two IF amplifier screens, and an .01 mica condenser suffices for a bypass. AVC is applied to two stages only and the filter is cut to a minimum. A .05 mfd condenser is necessary in the loop aerial return, since a smaller value interferes with the tracking of the tuned circuit. Use a midget 200-volt tubular and it can be mounted above the chassis alongside the 1R5 converter valve.

A number of condensers and resistors is essential in the audio circuits, but these can all be midget types with the sole possible exception of the 10 meg-ohm grid resistor, R5. Use ½-watt resistors in all other positions and use

# THE SET INSIDE THE CABINET

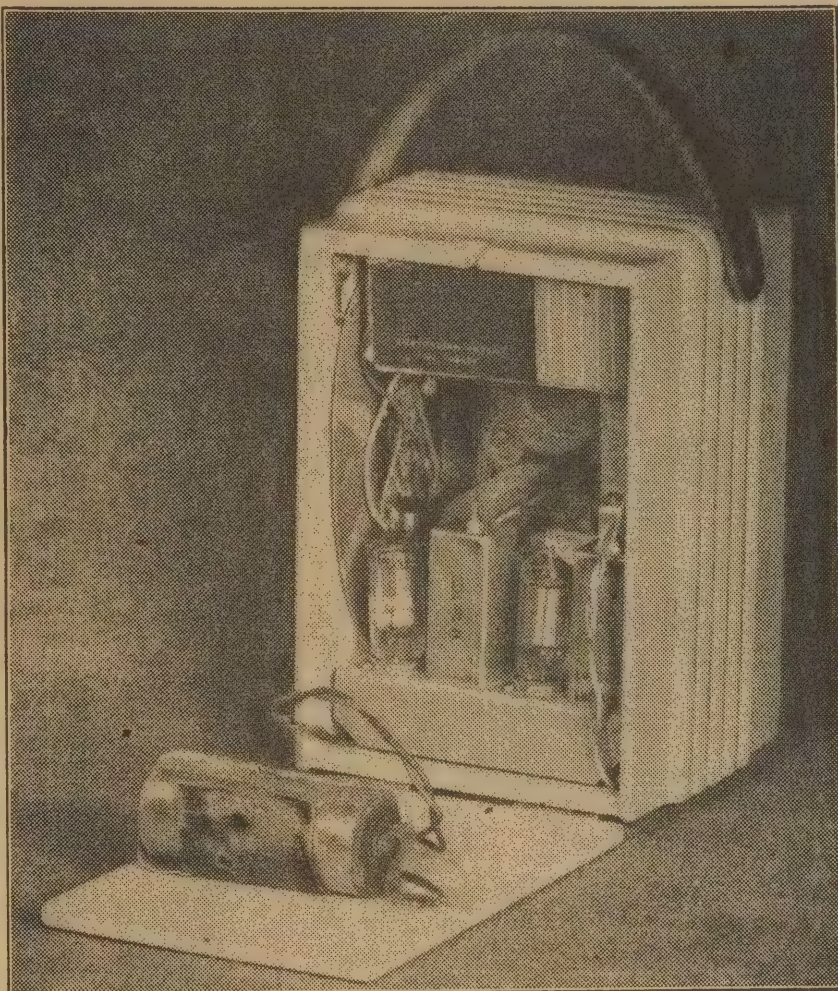

The picture shows how the set and batteries fit into the cabinet. The "B" battery is in place, and the "A" battery is shown in its clip on the hinged back. There is room for quite a large "A" cell.

## PARTS LIST

### AND KEY TO CIRCUIT

1 Chassis 3 15/16" x 3 1/4" wide x 7/8" deep.	C3 .05 mfd. 200 V. tubular.
1 Cabinet 4 3/16" wide x 4" deep x 6 3/16" high (inside dim).	C6 Section of gang, .0004 mfd. (approx.).
1 Loop aerial, 4" x 5" oval (approx.).	C7 .0004 mfd. mica.
1 Midget 2-gang condenser.	C8 2-plate mica trimmer.
3 Midget 455 kc. I.F. transformers.	C9 .01 mfd. mica.
1 Midget oscillator coil (wound on grid resistor).	C10 0.1 mfd. 200 V. tubular.
1 3" loudspeaker (or smaller) with 5000 ohm trans.	C11 .01 mfd. mica.
1 3S4, 1 1R5, 1 1S5, 2 1T4 valves.	C12 .00005 midget mica.
1 67½ volt miniature B battery.	C13 .005 mfd. mica.
1 1.5 volt cell (see text).	C14 .0001 mfd. midget mica.
1 Dial indicator plate.	C15 .01 mfd. mica.
2 knobs.	C16 .005 mfd. mica.
1 Midget off-on switch.	C17 8 mfd. midget electrolytic.
SUNDRIES	
Plastic hook-up wire. 1 & 2-mil. spaghetti, nuts, bolts, solder lugs, solder, scrap aluminium for brackets.	
CONDENSERS	
C1 2-plate mica trimmer.	R1 0.1 meg. 1/3rd. W.
C2 Section of gang, .0004 mfd. (approx.).	R2 0.1 meg. 1/3rd. W.
C4 .0001 mfd. midget mica.	R3 3.0 meg. 1/3rd. W.
	R4 .25 meg. 1/3rd. W.
	R5 10 meg.
	R6 3.0 meg. 1/3rd. W.
	R7 1.0 meg. 1/3rd. W.
	R8 3.0 meg. 1/3rd. W.
	R9 1.0 meg. potentiometer (small).
	R10 600 ohm midget.



# ARMY DISPOSALS EQUIPMENT

## WAVEMETERS

(Class C).

(Manufactured by A.W.A. For The Army)

These wavemeters are ideal for the amateur station. Regulations demand that every experimental station has, as a part of its equipment, a calibrated wavemeter.

Now is your chance to complete that station with a necessary instrument at a fraction of its original cost.

Each unit fully "tested" before being despatched to clients.

**£4-17-6** F.O.R.




**Internal View**

Range, 1470kc. to 10,260kc. In three bands as follows 1470 to 2870, 2800 to 5520 and 5280 to 10,260. Wavemeter operates on:—6 volts A.C. or D.C. L.T. for filament of valve and 90 volts H.T. (no batteries supplied). Valve used 1-6J8.

Jack provided for use with headphones when used for checking transmitter.

Circuit diagram, parts list, working instructions, headphones, etc. Supplied with each wavemeter.

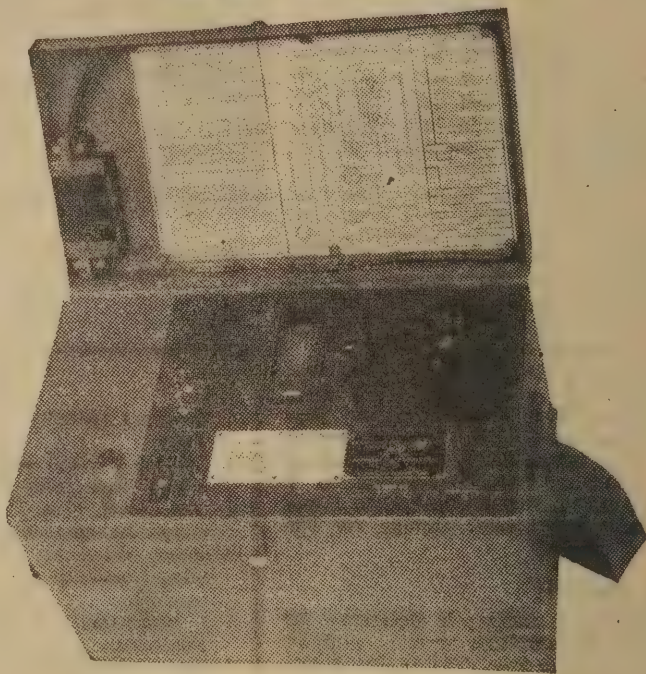Weight 23 lb. Size  $15\frac{1}{4}'' \times 10\frac{1}{4}'' \times 8\frac{1}{4}''$



**External View**

## PARAGON RADIO

245 PARRAMATTA RD.,  
HABERFIELD, N.S.W.

**Phone: UA2145**

ADDRESS ALL MAIL TO:—  
BOX 14 P.O., HABERFIELD,  
N.S.W.



as many of the midget "postage-stamp" mica condensers, as possible. Every saving in component size will help simplify layout and wiring.

As far as the constructor is concerned, more attention needs to be paid the actual job of assembling and wiring the set than to the details of the electrical circuit. Apart from its diminutive size, the chassis uses a more or less conventional layout—a point we considered worth while in this "pioneer" midget portable.


#### DIMENSIONS CRITICAL

The chassis is actually 3 15-16in. long, 3 3/4in. wide and 7-8in. deep. These dimensions are quite critical, and anything over a sixteenth inch tolerance may make the difference between the parts fitting together and into the cabinet or the reverse. Even assuming that you use a commercial chassis and cabinet, it is essential to plan ahead and make sure that everything will fit exactly as intended.

The original set used a "Kingsley" gang, being the smallest of the locally made air-gangs we knew of. As a rule we avoid direct mention of trade names, but there is no alternative in a set of this type, where parts must fit exactly together. Mounting the gang 3-8in. back from the front of the chassis and 1-32in. from the side brings the spindle 1 1-16in. above the top of the chassis and 1 5-16in. in from the right-hand edge. This sets the position of the tuning control on the front of the cabinet.

There are one or two excellent Eng-

## PARTS POSITION UNDER CHASSIS

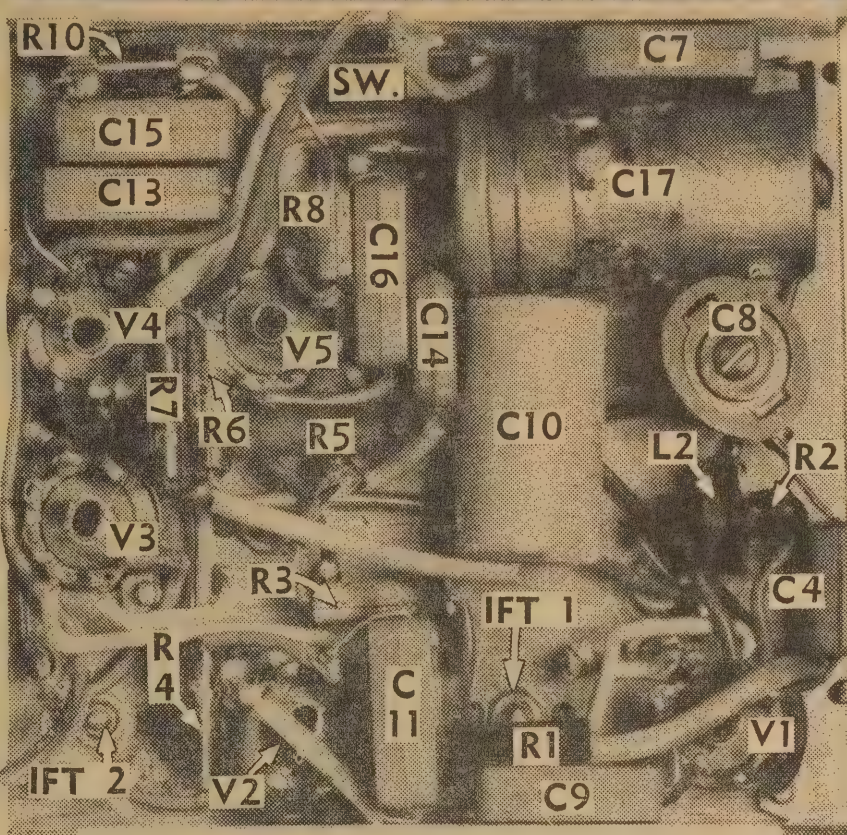

## ★ ☆ DISPOSAL ☆ BARGAINS ☆ ★

### NEW VIBRATOR POWER SUPPLIES

12 V. INPUT

375 V. 200 M.A.

Synchronous Rectifiers  
£7/-/-

Valve Rectifiers  
£8/10/-

6 V. INPUT

225 V. 200 M.A.

Synchronous Rectifiers  
£6/10/-

Valve Rectifiers  
£8/-/-

### NEWS

By the time this Edition goes to Press we will have a release of new Transceivers, Power Supplies, Amplifiers & P.A. Speakers including  
No. 11. Transceivers 9 Valves.  
No. 19. Transceivers. 15 Valves.  
No. 112. Transceivers.  
No. 113. Transceivers.  
This will be the best and possibly the last Release of these goods.

SEND FOR YOUR LIST.

Packing and delivery to rail —  
FREE — Please add Freight  
and Postage.

### Rotary Convertors

24 V. D.C. INPUT

230 V. A.C. 50 CYCLE OUT  
100 WATTS

Used But in Good Order

£6/10/-

New

£8/10/-

### GENEMOTORS

INPUT	OUTPUT		
6v.	240v. 50MA.	2	0
6v.	190v. 90MA.	3	10
12v.	180v. 60MA.	3	0
12v.	275v. 110		
	550v. 50	3	10
24v.	550v. 350	6	0

### CO-AX CABLE — 72 ohm

No. 11 Twin. 11mm Lead Covered Single. 9mm Single.  
Lengths to 500 yards. Minimum 10 yards.

1/- PER  
YARD

**EXCELAIR RADIO** 136 Victoria Road, Marrickville. Phone: LA1604



Available at all Leading Wholesalers

# RADOFONE KIT SET WITH SPEAKER



The latest in Kit Sets featuring four or five valve chassis broadcast, dual wave or including NEW TRI-WAVE BRACKET by Radio Frequency Products.

## RADOFONE KITSET Features:—

- Bakelite Cabinet Knobs.
- Cadmium Chassis 4 or 5 valve with  $\frac{1}{2}$  meg. Switch pot.
- Dial Glass calibrated for all States of Australia including Short Wave calibrations.
- Stromberg or Myba 2 Gang Condenser, rubber floating mount.
- 5" Amplion Dynamic or Rola Permagg. Speaker with choke.
- Kingsley Permaclad IF's and coils.
- Cabinet Colours: Walnut, Cream, Mahogany and Green, with Cream, Green or Gold Louvres.
- R.F.P. dual or Tri-wave Bracket supplied if required.

*Radio & Hobbies circuit and necessary parts list supplied with each kit.*


**SYDNEY DISTRIBUTORS:—**MARTIN DE LAUNAY—BLOCH & GERBER—GEO. BROWN—DAVIS RADIO—DOMINION FACTORS—FOX & MacGILLYCUDDY — LAWRENCE & HANSON—UNITED RADIO DISTRIBUTORS—RADIO DESPATCH.

*Now appointing Distributors in all States*

# RADOFONE INDUSTRIES

135 COOK ROAD, CENTENNIAL PARK, SYDNEY



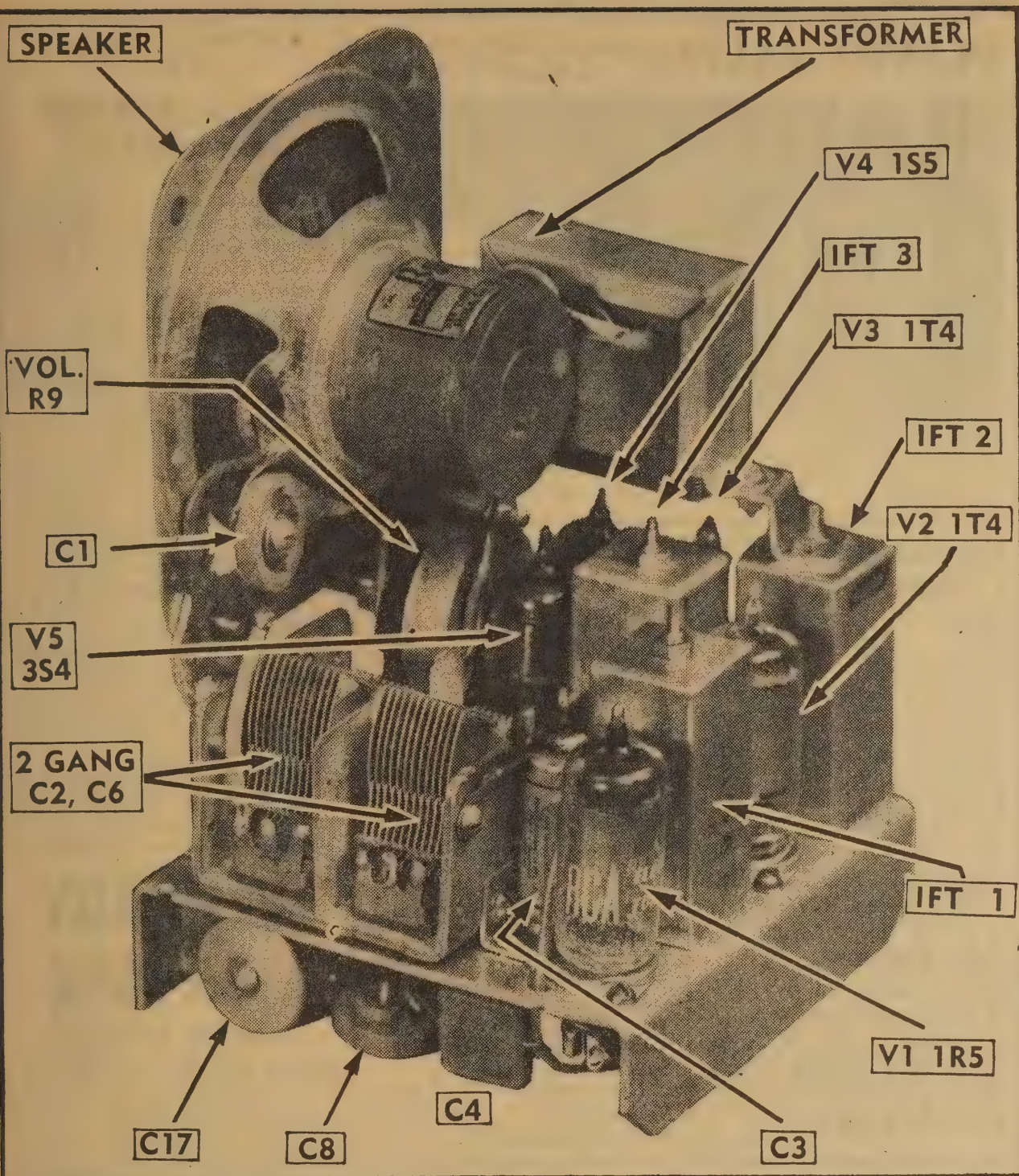

lish gangs on the market which can be used successfully in the set. These must be mounted on suitable brackets to bring the gang spindle in exactly the same relationship to the front and side of the chassis.

The brackets themselves will have to be cut and bent from a scrap of aluminium—not too difficult a task for anyone who proposes to build this set.

#### DIRECT DRIVE

We have made no attempt to provide for a vernier tuning drive because of the space factor. In practice, tuning with a direct knob control is quite satisfactory.

The volume control must be mounted on another bracket to bring the spindle

exactly in line horizontally with the gang spindle—that is 1 1-16in. above the top of the chassis. The distance between spindles must be 1 5-8in., bringing the volume control spindle 1 5-16in. from the left-hand edge of the chassis. The volume control and bracket should be mounted far enough back to allow just the 1/4in. spindle to protrude through the front of the cabinet — not the threaded bush as well.

It will pay to be fussy about these dimensions, since the spindles must coincide with the holes in the new escutcheon plate being produced for the set. If they are not exactly right the holes will not coincide and the plate may not mount in correct rela-

tionship to the sides of the cabinet or the speaker grille.

#### POSITION OF KNOBS


The knobs are not spaced symmetrically on the plate but a balanced appearance is lent by the plate itself and the numerical reference scale surrounding the tuning knob. Another point, of course, is that the positions are set to some extent by the natural location of the units on the chassis and the minimum clearance between them when the gang rotors are in the open position.

The "off-on" switch was not included with the volume control, since we could not locate a combined unit of suitable small dimensions. Rather


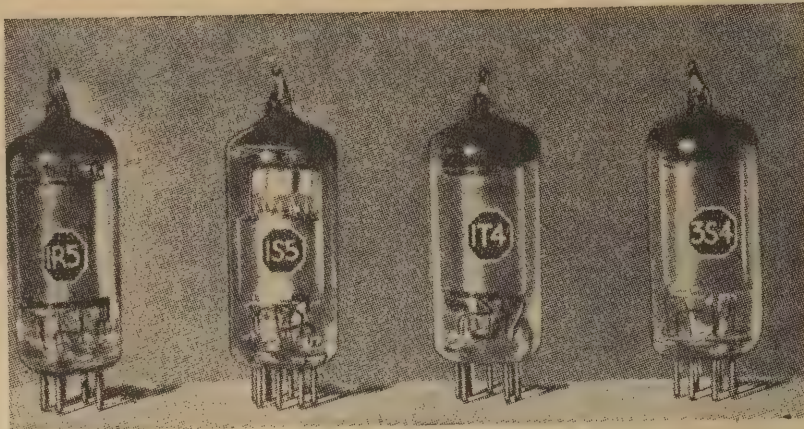
# PEANUT VALVES

STOCKS NOW AVAILABLE  
for Immediate Delivery



IR5 Converter  
22/10 ea.

IS5 Diode Pentode  
21/10 ea.

IT4 R.F. Pentode  
22/4 ea.

3S4 Power Pentode  
22/10 ea.

## SPRINGTIME PORTABLE PARTS PRICE LIST

Chassis . . . . . 7/6  
Cabinet . . . . . 52/6  
Loop Aerial . . . . . 7/6  
Osc. Coil . . . . . 8/6  
R.F. Coil . . . . . 8/6  
I.F. Transformers . . . . . 13/9  
3 Gang Condensers . . . . . 22/-  
DA7 Dial . . . . . 9/-  
Trimmers . . . . . 1/-  
Condensers: 10 mfd 2/6; .5 2/1;  
.1 1/-; .05 9d; .01 9d; .001 9d;  
.0001 9d; .00025 9d.  
Padders . . . . . 2/6  
.5 Potentiometer with switch 8/6  
½ watt Resistors, IRC . . . . . 9d  
3" Per. Mag. Speakers . . . . . 22/6  
Valves, see above  
Batteries, see column 3.

## LITTLE GENERAL PARTS PRICE LIST

Cabinets  
leatherette covered . . . . . 29/6  
Chassis . . . . . 4/11  
2 Gang Condensers . . . . . 17/-  
DA7 Tuning Dial . . . . . 9/-  
Power Transformer, 325v. 19/7  
Small Filter Choke . . . . . 5/9  
Aerial Coil . . . . . 8/6  
Oscill. Coil . . . . . 8/6  
Intermediates, 465 kc . . . . . 13/9  
Padder . . . . . 2/6  
Trimmers . . . . . 1/-  
Resistors: 1meg. 9d; .5meg. 9d;  
.05 9d; 20000 9d; 1000 9d; 400  
ohm 1/2; 150 ohm 1/2.  
Potentiometer, 5000 ohm . . . . . 5/-  
8mfd. Electrolytics . . . . . 3/9  
Condensers: .5 2/1; .1 1/-; .002  
9d; .0001 9d; .0005 9d.  
Octal Sockets . . . . . 1/-  
Speaker, 5" per. mag.,  
5000 ohms . . . . . 28/6  
Valves: 6J8 21/4; 6G8 19/10;  
6V6 18/10; 6X5 20/10.

## AUSTRALIA'S SMALLEST RADIO

### TOM THUMB

#### PARTS PRICE LIST

Front Panel, Chassis and Valve  
Bracket, set . . . . . 3/6  
Cabinet, Leatherette covered 9/6  
Reinartz Coil, RCS . . . . . 5/6  
Off-On Switch . . . . . 2/6  
Button Valve Sockets . . . . . 7d  
Midget Tuning Condensers  
.00036 . . . . . 12/6  
Resistors, ½ watt, IRC . . . . . 9d  
Condensers: 10 mfd. 2/6; .01 9d;  
.00025 9d; .0001 9d.  
Valves, see next column  
Headphones, 4000 ohm,  
English . . . . . 32/6  
Dial Plate . . . . . 1/3  
Knobs 9d, Pin Jacks 6d, Pointer  
Knob 1/-, Batteries, see below.

## CRYSTAL SET PARTS

PLANS SET 3 DIFFERENT . . . . . 6d.  
DUCET CRYSTALS . . . . . 1/-  
TERMINALS . . . . . 6d.  
CRYSTAL DETECTORS . . . . . 2/11  
" " Enclosed . . . . . 4/6  
" " Red Diamond . . . . . 7/6  
ALLIGATOR CLIPS . . . . . 5d.  
MICA CONDENSORS . . . . . 1/-  
COIL FORMERS (Cardboard) . . . . . 6d.  
COILS READY WOUND & TAPPED . . . . . 5/6  
HEADPHONES 4000 OHMS . . . . . 32/6  
TUNING CONDENSORS . . . . . 11/9

**EVEREADY**  
TRADE-MARK  
**MINI-MAX**  
TRADE-MARK

## PORTABLE BATTERIES

### Making Miniature Sets Possible

No. 745 A BATTERY 1.4 volt . . . . . 7/9  
No. 482 B BATTERY 45 volt . . . . . 11/6  
No. 467 B BATTERY 67½ volt . . . . . 17/1  
No. 471 A BATTERY 1. volt . . . . . 2/6

Please allow for postage. A cash refund will be made for any excess money forwarded. A deposit must accompany all C.O.D. orders.

Phone, Newcastle B3465; Address Telegrams "STANRADIO," NEWCASTLE.

**NEW  
STANDARD  
RADIO**

**102 HUNTER ST. NEWCASTLE.**



than compromise an otherwise nice layout on this account we used a particularly neat little push-button switch which happens to be available just now from distributors.

The 3in. loudspeaker mounts centrally above the tuning gang and potentiometer, the cone housing clearing the spindles by just 1-8in. This brings the magnet assembly to such a height that the "Minimax" battery just pushes in snugly between the magnet and the top of the cabinet. The front of the speaker should be lined up flush with the front edge of the chassis.

Yes, we know 3in. loudspeakers are as scarce as hen's teeth at the moment, but the position is bound to improve in the not-too-distant future!

You will have to manufacture a little bracket to attach the bottom right-hand edge of the speaker housing to the frame of the gang condenser. The other side of the speaker is attached to an extension of the same bracket which mounts the volume control.

OUTPUT TRANSFORMER

The midget output transformer must also be mounted by one lug to this bracket, at such a height that the top of the transformer is level with the magnet assembly. The B battery slides in on top of these two components and requires no other support. Careful control of vertical height is obviously essential.

Just how you bend the volume control bracket, or what fitments you em-

see still more compact designs requiring almost watchmaker's technique in the construction.

Once this part of the job is done, the rest of the assembly is quite simple. If the chassis is ready punched, it should be the work of a few minutes to mount the valve sockets and IF transformers.

The IF transformers in the original set are of English manufacture and employ single-hole mounting. The proposed locally-made units will be similar in size but have a modified mounting arrangement. It will simplify matters to use smaller nuts and screws than the usual 1-8in. Whitworth, and 8BA is suggested—if you can acquire them.

Be sure to mount the valve sockets and IF transformers in a way to ensure direct plate and grid leads. This is


important to ensure compact wiring and to avoid unwanted feedback.

Before beginning the job or wiring, file the bit of the soldering iron to a slender taper and then file the corners to reduce it to a slightly flattened diamond point. Tin it carefully and keep the tip clean as an absolute essential to neat soldering. You will be working on socket lugs which are less than an eighth-inch apart, and with midget condensers and resistors.

Excess heat or flux on any of these components may damage them, likewise unnecessary bending of the leads.

Begin by wiring up the filaments of the five valves, using preferably two colors of hook-up. The negative filament string must be connected to chassis, so that all A-minus pins become handy earth points. Remember, also, to connect the centre metal

(Continued on Page 75)

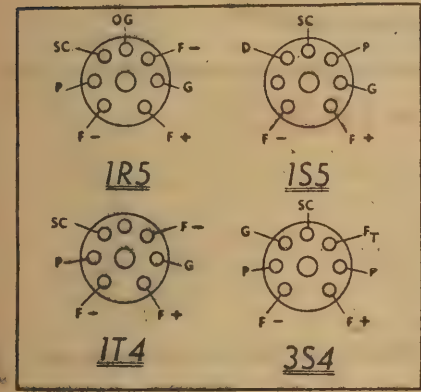

Here are the underneath socket connections for the valves used in the set. Note that three of them have two F- connections, both of which can be earthed. For the 3S4 connections see text.

play to mount the loudspeaker and transformer is not very important, provided they are in exactly the right positions. You will note, by the way, that there is just room for the transformer to mount alongside the speaker magnet without fouling the side of the cabinet. The rear of the transformer can be anchored by a bracket under a locknut of the second IF transformer.

WATCH DETAILS

All this detail may seem rather laborious, but precision is essential in a small job like this. And it is only the beginning. We can already for-

**\$100 GIVEN AWAY!**

**Suggestions wanted for listening to new personal portable radio!**

What is your suggestion for the best time and place to listen to the new Personal Portable radio? Eveready will pay £2 for every suggestion used. Simply address your entries to Eveready, Rosebery, Sydney.

**£2 from Eveready to Bruce Kyle, 21 Riverdale Ave., Marrickville who suggests taking a Personal Portable to the beach. "Then you can listen to the races and sun-bake too."**

**£2 from Eveready to Mrs. D. Laird, 66 Reed Street, Albert Park, Victoria who says she'd keep a Personal Portable in the laundry. Then she could do the washing and still follow her radio serial.**

**£2 from Eveready to Mr. Dave Williams, Nicholson Pde., Cronulla, N.S.W. who writes: "I'd take a Personal Portable along on week-end fishing trips. That's how to pass the time when fish aren't biting."**

They are as easy to carry as a girl's handbag. Their strong, clear tone, in such tiny space, is made possible by Eveready's miracle MINI-MAX battery... the same battery that was used in the "Walkie-Talkie".



**EVEREADY**  
TRADE-MARK  
**MINI-MAX**  
TRADE-MARK


Leading radio manufacturers are now making the new Personal Portable radios.



# COLLINS RADIO

409 LONSDALE STREET, MELBOURNE, C1. Phone MU1033


## ENGLISH 2-GANG TUNING CONDENSERS

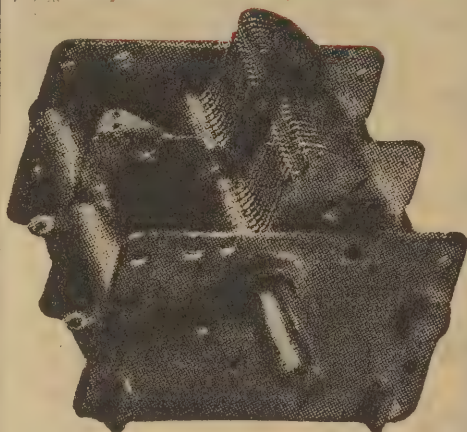

Expertly made. Midget Dimensions.  
Trimmers fitted.  
Ideal for your portable.

**17/3**

## ALUMINIUM CHASSIS

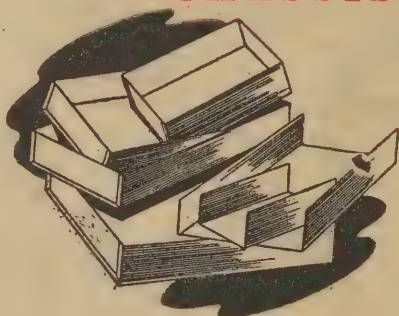

6" x 4" x 2"	Open Ends	3/6
12" x 7" x 2 1/2"	"	6/6
8" x 5" x 2 1/2"	Welded Ends	5/-
10" x 6" x 2 1/2"	"	6/6
13" x 7" x 2 1/2"	"	7/6
13" x 10" x 2 1/2"	"	9/-
17" x 10" x 3"	"	15/-

Standard 5-Valve Mantel Steel Chassis **8/6**  
Metal Cabinet to suit the above **20/-**  
Speaker Boxes, Will take 8" speaker **20/-**

**OTHER SIZES  
"MADE TO ORDER"**

## "COLRAD" BLUE PRINT SERVICE

1. Countryman's 4-Valve Battery Set. (1C7G, 1M5G, 1K7G, 1L5G.)
2. Economy 2-Valver, (1P5GT, 1Q5GT. Easy to make.)
3. Long Distance Crystal Set.
4. 5-Valve Dual Wave, 230 v. AC. (6A8G, 6U7G, 6B6G, 6V8G, 5Y3GT.)
5. 5-Valve B/Cast, 230 v. AC/DC. (6A8, 6U7, 6B6, 25L6, 25Z5, 302.)
6. 5-Valve Vibrator Receiver. (1C7, 1M5, 1M5, 1K7, 1L5.)
7. Midget 4-Valve Portable. Miniature Tubes and Special Battery saving feature.
8. 32-volt Farm Radio. No expensive Vibrator or power pack. Standard parts used.
9. Reinartz AC 3-Valve. A real winner, economical. (6J7, EL3NG, 5Y3.)
10. Portable 4-Valve. Uses (1A7GT, 1P5GT, 1H5GT, 1Q5GT.)
11. 15 watt Amplifier. (6SJ7, 6SC7, 6V6, PP, 5Y3.)
12. Selection of 14 Crystal Set Circuits, with guide to "Experimenters."
13. AC Economy 4. (6J8G, EBF2GT, 6V8GT, 5Y3GT.)
14. 10 watt Amplifier (6SN7GT, PP, 6V8GT, 5L3GT.)

**ALL ONE PRICE: 1/- each: POST FREE**

## FLEXIBLE COUPLINGS

7in. long .. **5/-**

5 3/4 in. long .. **4/6**

3 1/2 in. long .. **4/-**



As  
Illustrated

## VOLUME CONTROLS

- Aerostat. Popular Sizes .. **3/7**  
Stackpole. 1/4 meg. .... **3/6**  
Technico. Standard sizes .. **4/5**  
I.R.C. Popular sizes .. **6/2**  
Wire Wound. All types in stock



## VALVES

LARGE STOCKS  
AT LIST PRICES

Let us know your requirements  
All valves tested before despatch  
**PACKED SAFELY!**



## "Bright Star" HAM CRYSTALS

- 80 Metre AT Cut .. **52/6** each  
40 Metre BT Cut .. **52/6** each  
20 Metre Zero Drift .. **£5** each

Mounted in holder. Fits standard octal sockets.  
Regrinds **20/-** each. Customer must take risk of breakage. Every care taken.




**Any Article Listed Above Can be ORDERED with CONFIDENCE**



 **EGG INSULATOR**  
Polystyrene **6d** ea.

**BRASS WASHERS**  
1/8" Size Gross **1/9**  
5/32" Size Gross **1/6**

 **GRID CLIPS**  
Insulated 807 Type  
Don't Risk  
HI-VOLTAGE **1/9**

**CRYSTAL DETECTORS**  
"EBRO"  
As illustrated **2/6** ea.

 **NEEDLE CUPS**  
Brown Plastic **3/6** Pr.

**ROTARY SWITCHES**  
MIDGET SIZE **2/3** ea.

**TECHNICAL BOOKS**  
1947 ARRL Handbook . . . . . **12/6**  
1946 ARRL Handbook . . . . . **11/6**  
Radio Builders' Handbook . . . . . **1/-**  
Formula and Data Book . . . . . **1/-**  
Listener In Handbook. No. 16 . . . . . **2/-**  
Amateur Station Log Book . . . . . **3/6**  
A.R.R.L. Station Log Book . . . . . **3/9**  
Radiotron Designers' Handbook . . . . . **6/-**  
Handbook for Operators of Experimental Wireless Stations . . . . . **1/6**  
Practical Wireless Encyclopedia . . . . . **12/6**  
Modern Radio Service Technique . . . . . **4/-**  
RCA Transmitting Tube Manual . . . . . **2/4**  
Radio for the Millions . . . . . **10/6**  
Technical Topics. . . . .  
A "must" for the serviceman . . . . . **7/6**  
R.C.A. Receiving Tube Manual . . . . . **2/9**  
**MANY OTHERS IN STOCK.**  
**ENQUIRIES WELCOMED.**

Please include sufficient remittance for postage or freight when you order.

**CIRCLE CUTTERS**  
Adjustable.  
Cuts up to 3" Diam.  
**16/6** ea.

**BATTERY or SPEAKER 7 PIN PLUGS**  
OUR PRICE **6d** ea.

**AC/DC NEON TESTERS**  
"Hallmark"  
As illustrated **11/6** ea.

 **MIDGET I.F. TRANSFORMERS**  
English Made **14/3** ea.

**COIL FORMERS RIBBED**  
4, 5, 6 PIN. **2/3** ea.

**VALVE SOCKETS**  
All Types From **7d.** ea.

**SOCKET PUNCH**  
MAKES 1 1/8" Diam. **42/6** HOLE.

 **TOGGLE SWITCHES**  
From **3/1** EACH

**VALVE BASES**  
MICANOL 5 PIN **1/1 1/2** ea.  
For S/W Coils.

**TERMINAL STRIPS**  
"STEATITE" **1/10** ea.

**BEZELS**  
Ruby Prism . . . . . **3/-**  
2 Piece. Red or Green . . . . . **1/6**  
Front Loading Type **6/-**  
**SPECIAL!**  
Red or Green Bezels . . . . . **1/9**

**For FREE Technical Notes — CLIP THIS COUPON NOW!**

**TO COLLINS RADIO,**  
**409 Lonsdale Street, Melbourne, C.1.**  
Enclosed please find STAMPED, SELF-ADDRESSED ENVELOPE for **FREE CIRCUITS, TECHNICAL NOTES & CIRCULAR.**  
Include my name on your MAILING LIST for future issues.  
MR. \_\_\_\_\_

RH 1047. \_\_\_\_\_



# BARGAIN RELEASES



**P.M.G.**

## Adjustable Morse Keys

We have made another purchase of these brand new, genuine P.M.G. Adjustable Morse Keys and we are now able to sell them at the ridiculously low price of 10/- each.

P.M.G. MORSE KEY .. **10/- ea**  
(Without Headphones).

P.M.G. MORSE KEY. With brand new Stromberg-Carlson headphones .. **19/6**

PLEASE NOTE: These Morse Keys are brand new, ex-Army, and not military rejects.




## REFLECTOR GUNSIGHTS

Ex-Air Force. Containing best quality condenser lenses and adjustable reflector. Parts can be used for many purposes. **£2/10/- ea**

Postage 2/6 extra.

COMPONENTS INCLUDE THESE VALUABLE LENSES

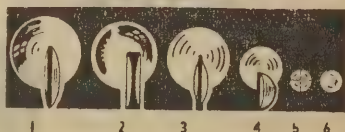

No. 1 Diam. 3 5-8 Foc. Len. 10in.  
No. 2. Diam. 3 1/4 Hollow Ground. No. 3  
Diam. 3 1/4 Foc. Length 4 1/2 in.+. No. 4  
Diam. 2 3-8 Foc. Length 6 1/2 in.+. No.  
5 Diam. 1 1-8. No. 6 Diam. 1 1-8  
Amber Coloured ordinary.

Gent's renovated  
Pocket watches, nickel  
and rolled gold—7 and  
15-jewels. Fully guar-  
anteed. **£2/10/-**  
PRICE & **£4/15/-**


Postage 1/- extra.



## GREASE GUN

Push-type grease guns, ex-Army. 5oz.  
Slightly used; perfect order. 12/6  
each. 10oz., slightly used; perfect  
order, 15/- each. 10oz. new, £1 each.

Postage 1/- extra.

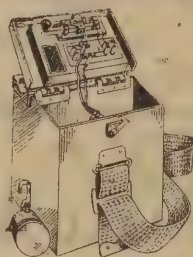

**Genuine P.M.G.  
Morse  
Key, with  
Light**

Complete with Steel  
Carrying Box, 8in.  
x 8 1/2 x 7. Worth  
at least £6/10/-.  
With carrying strap.

## Our Price . . . 11/6

The Carrying Case, which is complete  
with shoulder strap, alone is worth the  
money, or together with spotlight 29/-.  
Freight 4/- (NSW); Interstate F.O.R.



## Spot Light

Ideal for fishing,  
hunting, shooting.  
Brand new. Original  
cost £2/15/-  
each.

Our Price **17/6**

or together with  
Morse Key, Light  
and Case, 29/-.

Complete with Stand.  
Freight 3/-.



## METAL TOOL BOX,

**3/11 ea.**

3 1/2 wide, 7in. deep, 15in. long. Ideal  
for carrying spanners, pliers, hammers,  
etc. Opens at top and has leather  
grip handle. Cost the Army 15/- each.  
Brand new. Out they go for 3/11  
each. Post, N.S.W., 2/- extra; Inter-  
state 3/6 extra.

## THERMOMETERS

**300 degrees Fahrenheit**

Genuine mercury line Armour clad.  
The Thermometer with a 1001 uses.  
Brand New ex-Army.

**Price, 15/- ea.**

Postage 1/4



## Rubber One-Man Dinghies

Ex-RAF, brand new. Ideal for fishing,  
etc., original cost to RAF £15. Price  
now complete with sea anchor,  
paddles etc.

**Only £2/19/6 ea.**

Freight and Insurance, 4/6.

## SPECIAL TOOL OFFER


Our Offer this time includes Spanners  
that have been unprocurable for the  
past seven years.

**S.A.E. MAGNETO SET SPANNERS.**

One 9/32 x 5/16; One 11/32 x 3/8;  
One 13/16 x 15/64; One 1/4 x 7/32;  
One 11/32 x 3/8; One 0.B.A. x 1.B.A.;  
One 3.B.A. x 4.B.A.; One 4.B.A. x  
5.B.A.; One 6.B.A. x 7.B.A.; ONE  
RING AND OPEN END SPANNER—  
WHITWORTH.—One 1/2 ring and  
open end, one 9/16, ring and open  
end, one 5/8, ring and open end.  
1 2-lb. Ball Pein Hammer; 1 Tool Box  
3 1/2 in. x 7in. deep x 15in. long.

## The Lot for £2/13/6

Freight 4/6 extra.

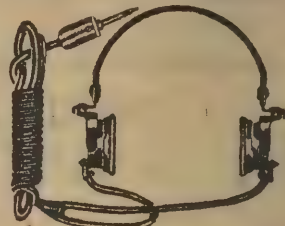

## HEADPHONES

Brand new, S.T.C. and Stromberg-  
Carlson. We have just made another  
purchase of the brand new 'phones,  
complete with cord and plug, and we  
are now able to sell them at the  
ridiculously low figure of—130 ohms  
impedance .. **9/6**

2000 ohms impedance .. **£1**

PLEASE NOTE: These 'phones are  
brand new, ex-Army, and not military  
rejects.

## BOMB- SIGHTS



Ex-Air Force. Useful component parts  
include 24v. motor. Best quality  
lenses, globes, sockets, etc. Cost £100.

Now .. **£2/17/6**

Postage 3/6 extra.


No C.O.D.

## DEITCH BROS

210a George Street, Sydney.



# A NEW 20-WATT AMPLIFIER DESIGN

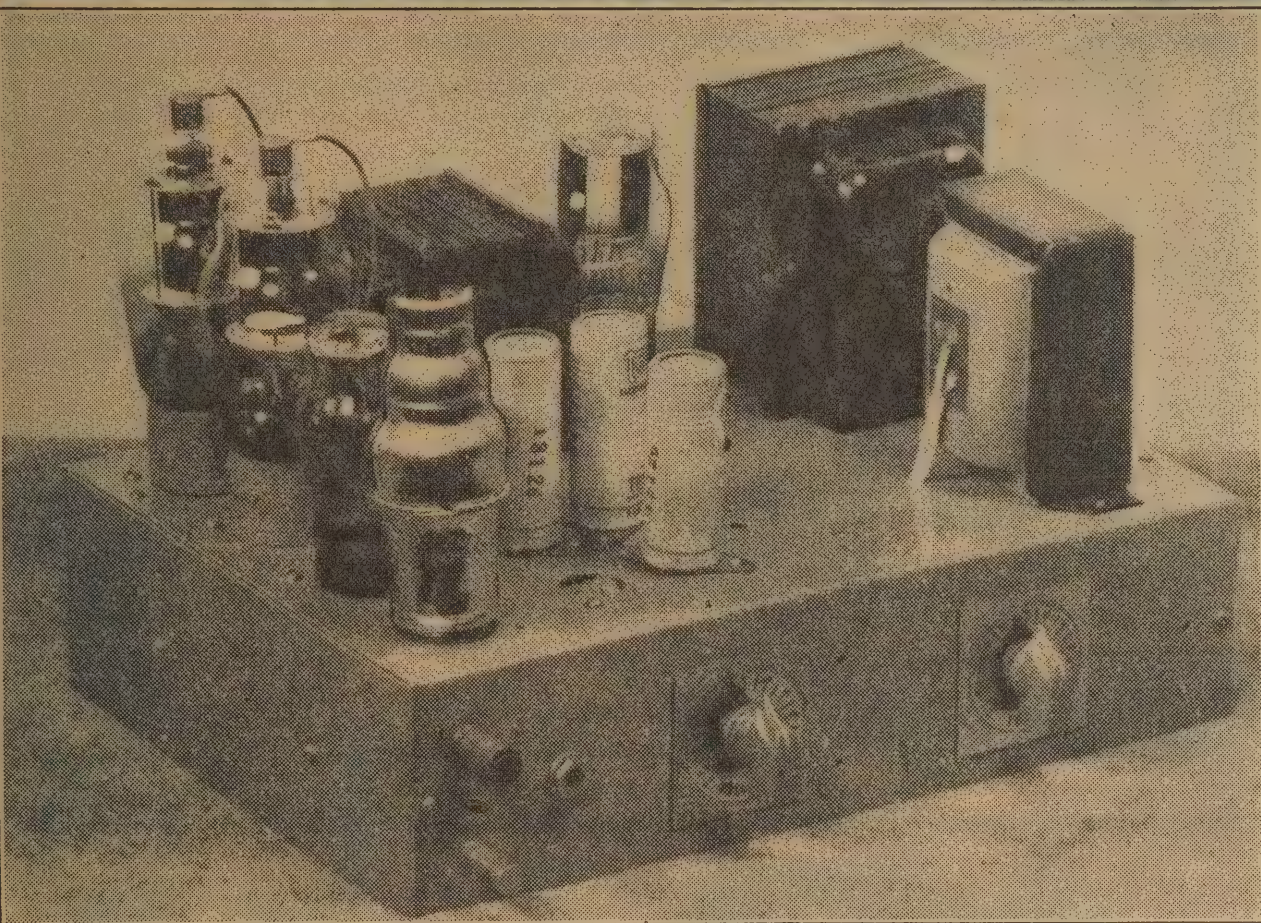

This general view of the amplifier will help you with the layout. It is not particularly critical.

The immediate success of our big 807 Radiogram prompted us to build up this amplifier for those who are interested mainly in quality reproduction or gramophone recordings. With an output of over 20 watts, you can regard this amplifier as the logical successor to the 13 watt 6V6 job, so popular over the past few years.

**T**HE original 13-watt amplifier proved popular because it offered excellent fidelity and good power output for a very moderate cost. Thousands of them were built in the original form, and as many others with tuners and preamplifier stages. Our new 807 job costs no more to build, but gives practically double the power output.

Behind this last sentence is the release of 807 transmitting valves at a fraction of their original price, so that they cost even less than the 6V6-G valves they replace. A much higher operating voltage is permissible, and this can be obtained from the same type of power supply without complication.

## PERMAG. SPEAKERS

Since the original 13-watt job was described, permagnetic speakers have come into general use in place of electrodynamics, which require a hundred volts or so across the field coil. In this new amplifier the full available

voltage is applied to the plates of the output valves instead of being partly absorbed by the field coil. Hence the higher output without much apparent change to the power supply.

The first valve in the circuit is a 6J7-G pentode voltage amplifier, connected in conventional fashion. Actually you can use a 57, 6C6, 6SJ7, or any similar sharp cut-off RF pentode without change to the electrical circuit. The 6AC7, VR65 or EF50 are other possibilities, although we have not actually tried them out in this circuit. You will note a rather strange collection of parts around the screen

of the valve, the purpose of which will be explained a little later.

We may mention in passing that the 6U7-G, 6K7-G, or other similar variable-mu pentodes are not a good choice for this position, where the stage is called upon to handle a substantial signal voltage. The tapering grid characteristic of a variable-mu valve can cause severe harmonic distortion.

## THE PHASE-CHANGER


The second valve in the amplifier is a triode-connected 6J7-G, which serves as a phase-splitter. Once again, almost any of the sharp cut-off pentodes will serve in this position, if connected as a triode.

We actually used an ordinary 6J5-G triode, which is seen in the photographs. Readers may have one of these or some other general purpose triode on hand, which will serve equally well with the same component values. A straight triode was not

by **W. N.  
Williams**



# Everyman's Guide to Radio

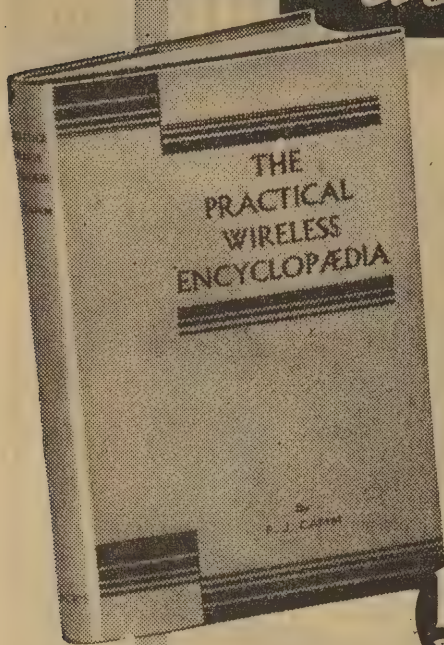

**12'6**  
POSTAGE  
**4D**

Compiled by an acknowledged expert, this volume forms a complete guide, in alphabetical order, to the construction, operation, repair and principles of every type of wireless receiver, including definitions, explanations, formulae and complete instructions on the making and testing of various wireless components.

A unique volume with every technical term, formula and fact explained in language which even the beginner will understand. A special feature of the work is the illustrations, which include a complete series of circuits for every type of modern receiver. The contents include every modern development. An invaluable volume which is a treasury of knowledge to the beginner, the expert, and the ordinary listener. Every fact may be rapidly consulted.

**400 pages — 484 illustrations.**

**CLIP AND POST TO-DAY**

DYMOCK'S BOOK ARCADE LTD., G.P.O., BOX 1521, SYDNEY.

Please supply me with Copy of "The Practical Wireless Encyclopaedia" by F. J. Camm.


1. Charge to my account.
2. I enclose 12/10, to cover price and postage.

Send to the following address:

**DYMOCK'S BOOK ARCADE LTD.**

424 GEORGE ST.

SYDNEY

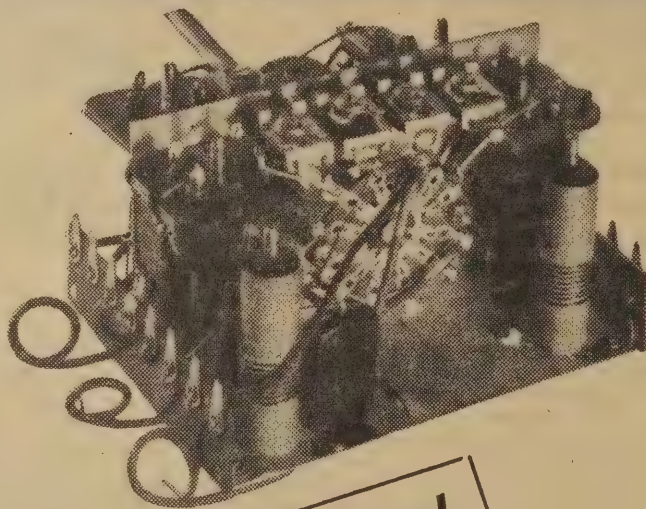

**To Be Released Shortly!**  
The "FECO" Series  
of new  
Miniature Coils  
and I/F Transformers

**Crown D.P. 3A.**

**TUNING UNIT**

**B/C & S/W 13 to 42 Meters**

This unit incorporates iron cored coils for both B/C and S/W bands. Each band consists of aerial R/F and oscillator coils.

Inbuilt fixed Padder condensers are incorporated, padder adjustment is by the iron core in the oscillator coils.

The use of iron cores in the S/W coils ensures better tracking as the inductance of each coil can be individually adjusted. This will give you more efficient overall performance.

**Price £4/17/-**

**Crown**  
**RADIO PRODUCTS LTD.**  
51-53 MURRAY STREET  
PYRMONT - SYDNEY  
Telephone NW 2628 (Lines)



stipulated in the circuit, mainly because there is no suitable type in the locally-made range.

Another point, of course, is that a 6J7-G is the better valve to buy if a new tube is necessary for the position. It makes an excellent triode, but has wider possible applications if the equipment is ever rebuilt at a later date.

In planning the amplifier, we were tempted to use the phase inverter arrangement adopted for the "Vibrogram" receiver a couple of months back. Perhaps it was just the urge to be different, for once.

However, there are a couple of points which make this circuit less desirable than the phase-splitter with 807 output valves. The first is that the grid resistors for the 807's should be as low as possible, consistent with circuit requirements, and we wanted to use 0.25 meg. at the most. This constitutes rather a severe a-c load on the plate circuit of the voltage amplifier, unless the plate load resistor be reduced to 0.1 megohm.

GRID CIRCUIT

This, in turn, would have a marked effect on the gain of the voltage amplifier, limiting the amount of feedback which can be applied or, alternatively, rendering the amplifier insensitive. As it is, the amplifier will give full output with any ordinary pickup or radio tuner. It is not intended for direct use with a microphone.

A further small point is that any grid current through either 807 would tend to bias the pentode phase inverter and have an adverse effect on its operation.


With the phase-splitter, the plate and cathode loads can conveniently be kept down to .05 megohm, so that the low grid circuit resistance is no embarrassment. And, furthermore, the circuit allows one to use any odd triode which may happen to be on hand, instead of demanding the use of a second pentode voltage amplifier.

As in the big radiogram receiver, the 807 valves are operated under class AB1 conditions with about 400 volts on the plates, 270 odd volts on the screens and cathode bias. Under ideal conditions, one could expect a power output of better than 25 watts, but some loss occurs due to poor voltage regulation and the imperfections of the output transformer. Even so, we measured better than 20 watts before overload point, which is more than enough for any domestic requirement. Hence, our reference to the job as a 20-watt amplifier.

SUPPRESSORS

Grid and screen suppressor resistors are included in the circuit as a precaution against instability, and these should be mounted as close as possible to the pins of the valve.

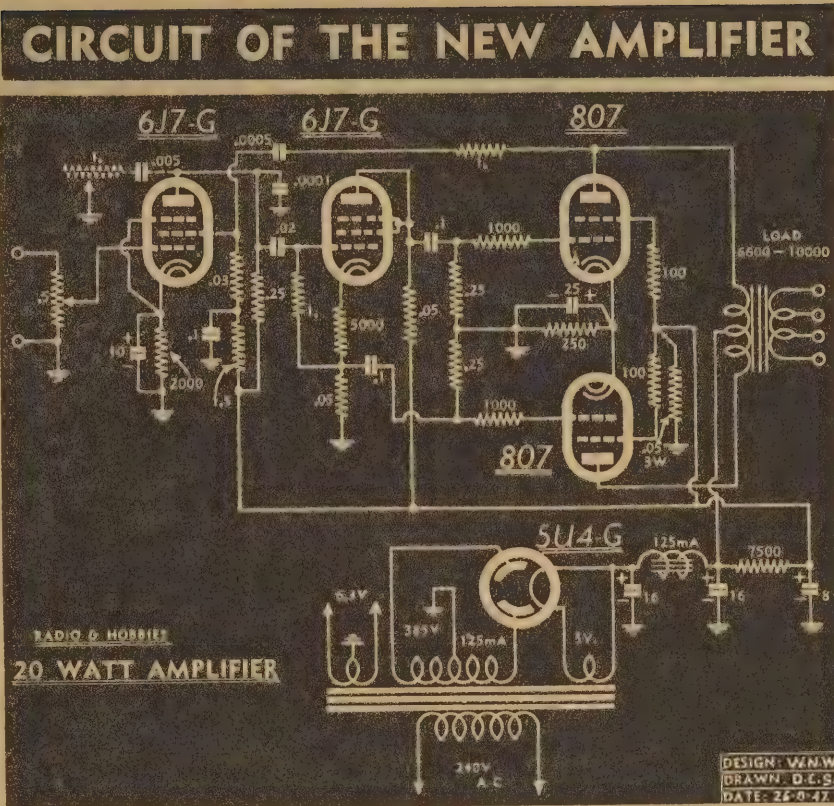The screens are supplied through a 7500 ohm dropping resistor and bypassed to earth by an 8 mfd. electrolytic. The 50,000 ohm 3-watt resistor and the drain of the two 6J7-G valves helps to stabilise the screen voltage to some extent. Naturally, the dropping resistor and the electrolytic condenser form a decoupling network, which adds to the filtering.



After considerable experiment, we have come back to the old phase-changer, always reliable.

Our experience with 807 valves under these general conditions is that the load is not particularly critical, provided it is between about 6500 and 10,000 ohms plate-to-plate. But do not use anything outside these limits. To handle the output it is very wise to use something larger than the transformers normally fitted to loudspeakers. Not only is the core inadequate, but the efficiency is generally well down.

We used a standard commercial output transformer, which is readily available. It is nominally rated at 15 watts and affords a choice of three secondary impedances for different

loudspeakers, namely 2.3, 8.0, and 12 ohms.

SCREEN FEED

Negative feedback is taken from the plate of the upper output valve, through a resistor and a small condenser to the screen of the 6J7-G voltage amplifier. The small condenser tends to reduce the feedback at the very low frequencies and thereby gives a small amount of bass boost. The effective degree of feedback is set by the .03 megohm resistor, which is in series with the normal 0.1 mfd. screen bypass.

The 1.5 megohm d-c supply resistor

PARTS LIST

- |   |   |
|---|---|
| 1 Chassis 12 x 8½ x 3in.  | 2 100 ohm, 1 1.0 meg. potentiometer, 1 0.5 meg. potentiometer.  |
| 1 Power Transformer 385/0/385V., 125mA, 5V 2A, 6.3V 3A.   | CONDENSERS  |
| 1 Filter Choke 125mA.   | 2 16 mfd. 600 P.V., 1 8 mfd. 525 P.V., 1 25 mfd. 40 P.V., 1 10 mfd., 40 P.V., 3 0.1 mfd. tub., 1 .02 mfd. tub., 1 .005 mfd. mica, 1 .0005 mfd. mica, 1 .0001 mfd. mica. |
| 1 Valve Shield.   | VALVES  |
| 3 Octal Sockets.  | 6J7-G, 6J7-G (or gen. purp. triode), 807, 807, 5U4-G.   |
| 3 5-pin Sockets.  | SPEAKER   |
| 2 Terminals.  | 12-inch permagnetic.  |
| 1 Output transformer 6600 to 10,000 ohm C.T. primary. Secondary to suit loudspeaker.  | SUNDRIES:   |
| 2 Indicator plates, "Volume" and "Tone."  | 2 insulated grid clips, 2 small grid clips, power flex, hook-up wire, shielded wire, spaghetti, nuts and bolts, solder lugs, 2 pointer knobs.                           |
| RESISTORS   |   |
| 1 1.5 meg., 1 1.0 meg., 3 .25 meg., 2 .05 meg., 1 .05 meg. (3W or substitute), 1 .03 meg., 1 7500 ohm 5W., 1 5000 ohm, 1 2000 ohm, 2 1000 ohm, 1 250 ohm 5W., |   |



# FERGUSON'S RADIO Pty., Ltd.

## Specialising in Audio Transformers

Manufacturers of the Output Transformer Type OP3 featured in the 20 Watt 807 Amplifier in this issue. This transformer was successfully used in the 807 Radiogram described in the June Issue. Type OP3 is a 15 Watt output transformer with a secondary suitably tapped so that it is possible to match any one of the popular makes of loudspeaker now available.

We have the pleasure of announcing two new transformers to our list of standard range types. Both transformers have been designed to operate in the anode circuit of an amplifier using a single 807 in the output.

The frequency response of both transformers is within 1 db. in the range 50 c/s. to 12,000 c/s. The primary impedance has been centred on 3250 ohms and the frequency response given is based on a D.C. unbalance of 85 m.a.

TYPE	PRIMARY	SECONDARY	FREQUENCY RESPONSE	RATING
OP22	Single 807. 3250 ohms.	500/125 ohms or 2.3 ohms.	1 db. 50 c/s-12,000 c/s.	10W.
OP23	85 m.a. D.C.	8.4/2.1 ohms or 12.5 ohms.	1 db. 50 c/s-12,000 c/s.	10W.

Type OP22 is ideally suited for the Recording Amplifier described in last month's issue.

Procurable from any wholesale house in all States including Tasmania. If you have any trouble obtaining supplies, write to us direct and we will forward a list of suppliers.

### FACTORY REPRESENTATIVES

N.S.W. ELECTRONIC INDUSTRIES IMPORTS.  
VIC. ELECTRONIC INDUSTRIES IMPORTS.

QLD. ELECTRONIC INDUSTRIES IMPORTS.  
STH. AUST. APEX AGENCIES.

## Available Now!

### English Goodmans High Fidelity Loudspeakers

#### 12 AND 15 INCH PERMANENT MAGNET TYPES

Both models have an outstanding frequency response and a power handling capacity of 20 watts and 30 watts respectively.

12 inch model voice coil impedance 15 ohms at 400 C.P.S.

15 inch model 3.5 ohms. Matching transformers also available.

**PRICES: 12 inch—£14/6/8. 15 inch—£35/13/9**

### English Taylor Model 65B All-Wave Signal Generators

Coverage from 100 Kc/s to 46 Mc/s. Operates from 110 or 200-250 volts A.C. mains, 40-100 cycles. 4 inch directly calibrated dial.

**PRICE: 29 Guineas Plus 10 Per Cent. Sales Tax.**

### English A.W.F. 8-in. Permanent Magnet Loudspeakers

Type U2T includes tapped transformer to suit 5000, 7000 or 15,000 ohm load. Voice coil impedance 2.3 ohms suits standard Australian made transformers.


**PRICE: £2/18/6**

*For further details apply to your local distributor or direct from the importers.*

**DENHAMS (M'bro) PTY. LTD.**  
MARYBOROUGH QUEENSLAND


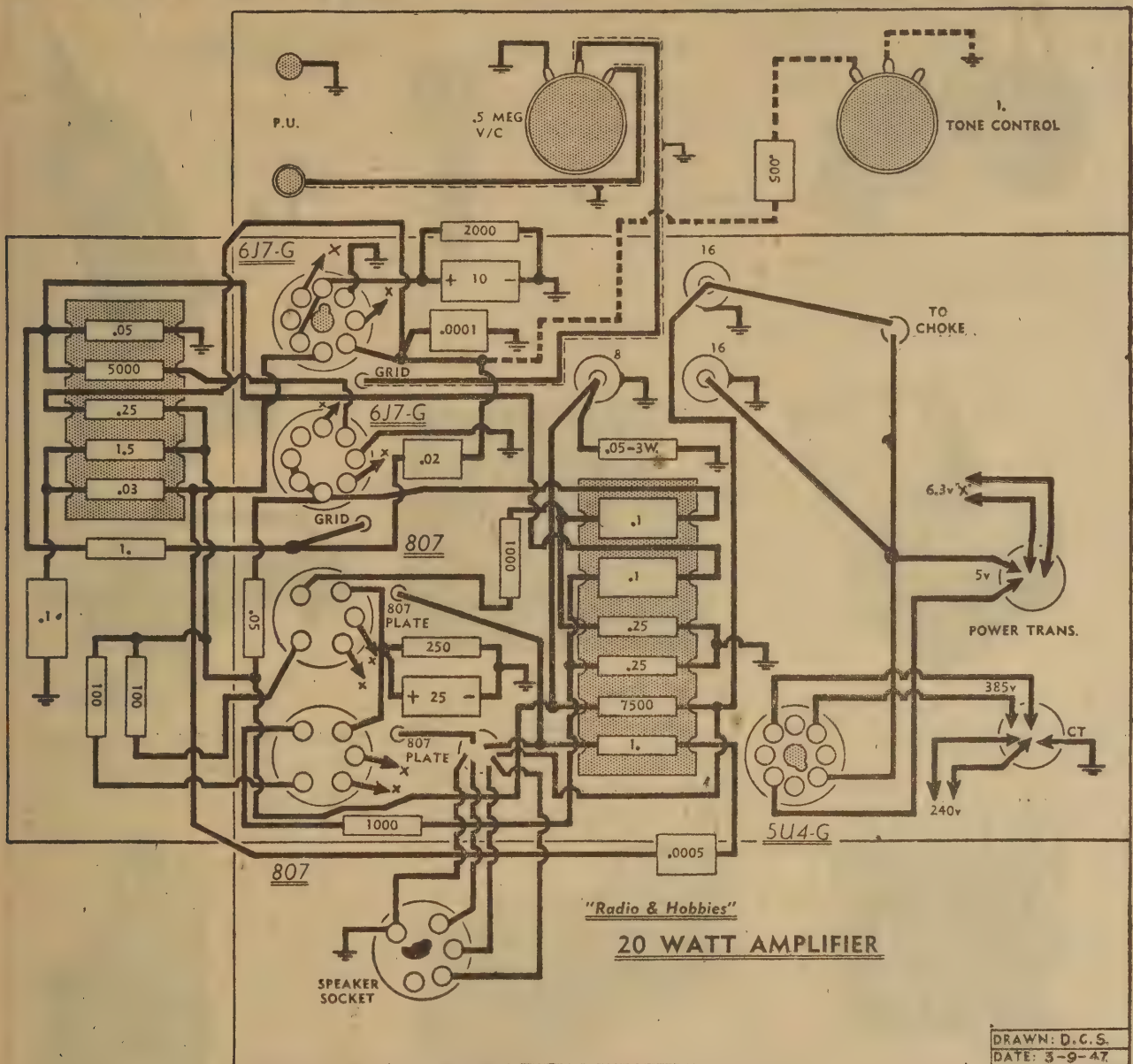
# WIRING DIAGRAM OF THE 20-WATT AMPLIFIER



This diagram shows how we laid out our chassis and wiring.

to the screen feeds into this point, since the series condenser prevents the d-c supply being derived from the negative feedback network. The arrangement may look a little involved, but the immediate reaction of everyone who has heard the original 807 radiogram is to comment on the full, throbbing quality of the bass response.

Incidentally, we have modified slightly the characteristics of the feedback and bass boost network, but the difference is only minor. In this amplifier, the emphasis is a little lower down the scale.

A final point is that we have shown dotted a conventional treble-cut tone control. This device should not be necessary, but readers frequently ask for it, as much as anything from habit. As far as we were concerned, its chief virtue was to balance the

layout of controls on the front of the chassis.

Coming to the power supply, it is a perfectly conventional affair using a 125 milliamp power transformer and choke, with three filter condensers. You could just get by with 100 milliamp equipment, but the 125 milliamp rating gives a margin of safety. A 150 milliamp rating throughout would be a good investment against possible additions to the amplifier, but there is not too much space to spare on the chassis.

Try and obtain 600 volt electrolyte condensers for use either side of the choke, as the 525 volt units would be operating right on the peak of their ratings. At least, make the one adjacent to the rectifier a 600-volt type. For the sake of low hum level, we have suggested 16 mfd condensers

rather than 8 mfd units. Of course, the actual working inductance of the filter choke is a governing factor in the hum level.

In building up the amplifier, we used the same universal chassis as designed for the "Vox Major" amplifier, described a few months back. In fact, the original "Vox Major" was partly stripped and the extra components added. You will notice a jack in series with the input circuit. Just forget this, as it has no connection with the operation of the amplifier.

The two normal input terminals are to the left of the chassis one being earthed and the other feeding through a shielded lead to the "hot" side of the potentiometer. The centre of the

(Continued on Page 43)



# DISPOSALS RELEASES



Hand Generator 6-8v output at 3 amps. at 100 R.P.M. Supplied with clamps, connecting leads, etc. in metal case.  
EACH . . . . . £3/10/-


DYNAMIC  
MICROPHONES  
supplied with  
matching transformer

15/-  
EACH




COPPER-OXIDE  
RECTIFIERS  
Full-wave  
bridge type,  
100 M/A O.P.

3/6  
EACH

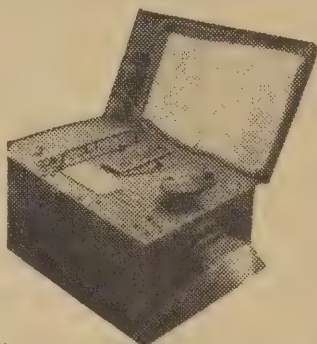

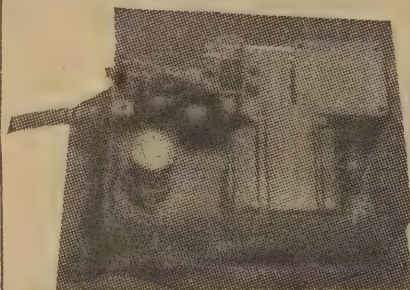
A.W.A. Class C. Heterodyne Wave-meters, new condition, supplied less Vibrator. Range 1.4-10 M/C's. Plus Harmonic output to 50 M/C.  
EACH . . . . . £4/10/-




Vibrator Power Supply complete with filter, 12v input, 300v output at 150 M.A.  
EACH . . . . . £3/10/-



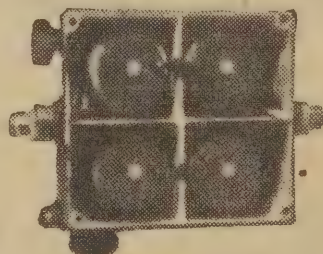Telephone Breast Set includes Microphone and Receiver, new in portable case.  
EACH . . . . . 10/-



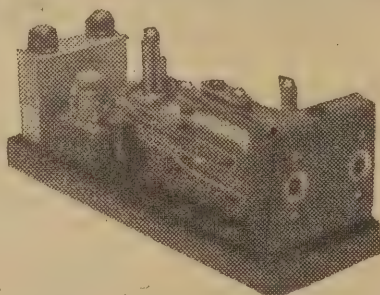240v A.C. Line Filter, 3 amps. as illustrated.  
EACH . . . . . 12/6



Telephone Jacks, mounted in dust-proof bakelite case.  
PAIR . . . . . 2/6

Receiver Noise  
Limiter, in-  
cludes EA50  
valve mounted  
and ready wired  
for your set.  
Supplied with  
full instructions.

8/6  
EACH



## PAPER CONDENSERS

6 uf. 1000 V.W.	10/-
4 uf. 1500 V.W.	15/-
4 uf. 2000 V.W.	20/-
30 uf. 500 V.W.	20/-
80 uf. 250 V.W.	20/-
5 uf. 400 V.W.	5/-
0.25 uf. 3000 V.W.	6/-

## FILTER CHOKES

100 M/A . . . . . 8/6

RELAYS. 150 ohm, 2 pair H.D. Contacts.

EACH . . . . . 5/6

## GENEMOTORS

12v input, 275v-110 M/A output. Plus 550v-50 M/A output. Complete with filter.  
EACH . . . . . £2/10/-

12v input 550v-350 M/A output £4/10/-  
24v input 340v-210 M/A output . . . £3

# ELECTRONIC EQUIPMENT CO.

LM3555

29B WEST ST., LEWISHAM.  
N.S.W.

LM3555



## POINTERS ON AERIAL SYSTEMS

**W**HILE the average urban dweller has come to think of an aerial simply as a length of wire tacked to the picture rail, there are plenty of instances where more attention has to be paid to the problem.

For general reception requirements, the conventional inverted "L" aerial is about the best all-round choice. This simply consists of a length of wire strung horizontally between poles and as high as possible, with a lead-in coming off one end, down to the receiver.

In remote areas, the horizontal portion of the aerial can be quite long, and constructors of small receivers frequently use as much as 100 feet of aerial wire, exclusive of the lead-in. However, such long aërials limit the apparent selectivity of small receivers and, in less remote areas, generally better results may often be obtained by keeping the aerial length down to about 50 feet.

The aerial should be as high as possible and erected clear of buildings. The directional properties of the inverted "L" are seldom very marked, so that it can be erected in any convenient position and direction.

Battery powered receivers should always be provided with an earth connection, made by clamping a wire round a pipe driven deeply into moist ground. An earth is less important with mains-operated receivers, mainly because a partial earth is provided by the power mains. However, where interference is experienced, the use of an effective earth may give quieter reception conditions, even though not adding materially to the loudness of the incoming signal.

Dipole aërials or special arrays are

widely used for short-wave communication purposes, being cut and erected to give definite directional properties and high-gain at their natural resonant frequency.

But, these very properties render them less suitable for general reception, where desired signals may arrive from all directions and at frequencies anywhere within the tuning range of the receiver.

However, the dipole aerial has another property which sometimes makes it useful in areas where electrical interference is high — notably close to power lines or industrial machines. Whereas the ordinary aerial and lead-in picks up signal over its entire length, the twin leads from a dipole are insensitive to incoming signals and merely convey the signal picked up in the top section to the aerial coil of the set.

Hence an improvement in signal-to-noise can sometimes be achieved by erecting the aerial proper as high as possible and remote from the source of interference, running the twin leads to the receiver aerial coil. For broadcast reception, no use can be made of resonant effects, and the aerial can therefore be cut to any convenient length.

To be fully effective, the twin leads must connect to the respective ends of the aerial coil primary. This will normally require the lower end to be disconnected from chassis and returned to a second aerial terminal.

Many new insecticides, germicides and fumigants have names composed of initials such as DDT; they are confusing but much simpler to the layman than their long and complicated chemical names.

## WIRING DIAGRAM OF THE 20-WATT AMPLIFIER

(Continued from Page 41)

potentiometer is connected by a second shielded lead, up through the chassis, to the grid cap of the first 6J7-G audio amplifier.

The audio amplifier valve is in the front left corner, with the phase splitter and the two 807 valves in line behind it. The plate leads of the 807 valves pass down through the chassis to the underside of the output transformer, mounted alongside

them. When wiring up these valves, make sure to take the feedback from the correct plate. Another point: It is wise to fit these with insulated plate caps to prevent accidental contact with the 400 volts of high tension supply.

We took a couple of heater leads and the high tension to a socket at the rear of the chassis to facilitate possible use of the amplifier with a preamplifier stage or a tone control valve. Please yourself about this point.

Take the voice coil leads to the rear speaker socket, lock a couple of suitable indicator plates behind the control knobs and your amplifier will have quite a pleasing appearance.

Use it with a crystal pickup, as a general preference, and operate into nothing less than a well baffled 12-inch loudspeaker.

The rest of the story, if any, is told by the diagrams and the pictures. Unless we miss our guess, this amplifier will prove just as popular as the 807 Radiogram from which it came. Thanks again, Mr. Hitler, for the cheap 807's!

## REPAIRS on meters and test equipment

done by

**Radio Equipment Pty. Ltd.**

5 NORTH YORK ST., SYDNEY.

## PHILIPS MANUAL OF RADIO PRACTICE FOR SERVICEMEN

**A MUST-HAVE FOR EVERY  
Serviceman • Engineer  
Amateur • Experimenter  
Student**

**496** PAGES • 250 DIAGRAMS • 400 FORMULAE • 105 CHARTS AND TABLES • 122 VALVE CURVES

PRICE  
**22/6**  
POSTAGE PAID

To Philips Electrical Industries of  
Australia Pty. Ltd.,  
Box 2703C, G.P.O., Syd

Please forward post-free to the address below one copy of the Philips Manual of Radio Practice for which I enclose cheque/postal note for 22/6.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

R.H.J.

OR OBTAINABLE FROM ALL LEADING BOOKSELLERS

G19

## "COYNE" Electrical and Radio Books

"COYNE" 7 Volume Applied Practical Electricity.

"COYNE" Electrical and Radio Trouble Shooting Manual.

"COYNE" Electronics.

"COYNE" Electrician's Handbook.

"COYNE" Electrical and Radio Dictionary.

"COYNE" Starting and OPERATING a PROFITABLE ELECTRICAL and RADIO BUSINESS.

All above titles available from stock.

ALSO SOON TO ARRIVE first shipment of

"COYNE" Radioman's Handbook.

"COYNE" Applied Practical Radio (New 3-Vol. Radio Set).

Write us for illustrated pamphlet and price list.

Exclusive Representatives for Australian and New Zealand territories.

## Associated Trade Journals Coy.

Frazer House, 42 Bridge Street,  
Sydney, N.S.W. Phone: BW1400.

Telegrams: Acrossland Cables: Acrosseas



# BARGAINS LIKE THESE HAVE

## HEADPHONES

4000 ohm high impedance.  
Definitely not rewinds. Complete with cord and plugs.  
Post 1/-.

**21/-**

## CONDENSERS

Tubular paper types: .01 mf 1000VW, .05 mf 200VW, .1 mf 200VW, .1 mf 350VW, .5 mf 350VW.

Each . . . . . **6d**

Tubular electrolytic types: 25 mf 50 volt, 50 mf 50 volt, 1 mf 350VW.

Each . . . . . **1/-**

Postage 1½d each extra.

Block type: 0.01 mf 750VW, 0.02 mf 750VW, 0.02 mf 350VW, 0.12 mf 250VW, 1 mf 500 V test, 2 mf 500 V. test.

Each . . . . . **6d**

Postage 3d each extra.

0.1 mf 600VW, 0.25 mf 400VW, 0.5 mf 400VW, 1 mf 400VW.

Each . . . . . **1/-**

Postage 3d each extra.

0.001 mf 5000VW, 0.001 rmf 900 V.ACW, 0.0028 mf 900V.ACW, 0.005 mf 2500VW, 0.25 mf 2000VW.

Each . . . . . **2/-**

Postage 6d each extra.

0.1 mf 4000VW.

Each . . . . . **2/6**

1 mf 1000VW.

Each . . . . . **5/-**

Postage 1/- extra.

0.5 mf 4000VW, 1 mf 1500VW, 2 mf 1000VW, 6mf 1000VW, 8mf 2000v. Test.

Each . . . . . **7/6**

Postage 1/3 extra.

## CABLE CONNECTORS

Telephone type 2 conductor (not suitable for high voltage).

Each . . . . . **6d**

Postage 3d extra.

Heavy duty type for transmitters, amplifiers, etc., 2, 4 or 6 conductor.

Each . . . . . **5/-**

12 or 18 conductor.

Each . . . . . **7/6**

Postage 6d extra.

## LAMPS

Replacements for Aldis signalling lamps, 12 volt.

Each . . . . . **1/-**

Postage and packing 6d extra.

Automobile 12 V 24 watt D.C. lamps.

Each . . . . . **1/6**

Postage and packing 6d extra.

## FUSE HOLDERS

Slydelock. Panel mounting type. . . . . **1/-**

Postage 1½d extra.

## VARIABLE CONDENSERS

400 mmF medium size. Ideal for crystal and small valve sets. . . **8/6**

Postage 9d extra.

## Microphone Cable

Heavy duty 2 core shielded and rubber covered.

**1/- yd.**

Special price for quantities.

## MORSE KEYS

Army Type No. 8 Key—very compact and fully adjustable.

Each . . . . . **5/-**

Postage and packing 9d extra.

Heavy duty Navy type on bakelite base. . . . . **5/-**

Postage and packing 1/3 extra.

Standard Navy keys. Heavy brass construction on wood base, with terminals. . . . . **5/-**

Postage and packing 1/- extra.

## MICROPHONES

Army No. 3 Carbon Hand Microphones, with cord and plug. . . . **7/6**

Postage and packing 1/- extra.

Army No. 7 Dynamic Hand Microphone, less cord and plug. Used but guaranteed in good order. . . . **10/-**

Postage and packing 1/- extra.

Navy Carbon Hand Microphone, with cord and plug. . . . **10/-**

Postage and packing 1/- extra.

Navy Magnetic Microphone, complete with cord and plug. . . . **3/6**

Postage and packing 9d extra.

Navy double button carbon Microphone, complete with cord and plug. . . . **7/6**

Postage and packing 9d extra.

Dynamic Inserts as used in No. 7 Microphones. . . . . **10/-**

Postage and packing 6d extra.

Covers for Dynamic Hand Microphones. . . . . **6d**

Postage 3d extra.

Rubber Mouth Pieces. Straight or curved. . . . . **3d**

Postage 1½d extra.

## INSULATORS

Bakelite aerial insulators, 3in. long. . . . . **6d**

Postage 1½d extra.

8in. Glass Aerial Insulator. . . **3/6**

Each . . . . . **3/6**

Post and packing 1/- extra.

12in. Glass Aerial Insulator. . . **5/6**

Each . . . . . **5/6**

Post and packing 1/3 extra.

Porcelain Spreaders, 11in. long. Each . . . . . **1/6**

Postage and packing 9d extra.

Two-piece porcelain lead thru insulators. Miniature type 1. . .

1in. dia. with flat top . . . . . **6d**

1½in. dia. with conical top. . . .

## CO-AXIAL CABLE CONNECTORS

Best quality silver plated. Chassis Socket and Plug.

**5/-**

Right angle adapter 2/6.

## TELEPHONE SPARES

Receiver caps for hand set. . . . **1/6**

Each . . . . . **1/6**

Postage 3d extra.

Microphone caps for hand set. . **1/6**

Each . . . . . **1/6**

Postage 3d extra.

Carbon microphone inserts. . . . **2/6**

Each . . . . . **2/6**

Postage 3d extra.

Receiver inserts. . . . . **2/6**

Each . . . . . **2/6**

Postage 3d extra.

4-way cords, approx. 4ft. long. . Each . . . . . **3/6**

Each . . . . . **3/6**

Postage 3d extra.

4-pin cable plugs. . . . . **3/6**

Each . . . . . **3/6**

Postage 3d extra.

4-pin sockets for above. . . . . **3/6**

Each . . . . . **3/6**

Postage 3d extra.

GROMMETS. ½in. x ½in.—½in. x ½in.—1in. x ½in. Each . . . . . **3/6**

BAKELITE SHEET. High grade. ½in. thick. 9in. x 7in. . . . . **3/6**

Each . . . . . **3/6**

Postage 9d extra.

FOR THE BEST IN RADIO

PRICE'S

5 & 6 ANGEL



# OPEN ONCE IN A LIFE TIME

Black bakelite lever knobs. . . . . 3d  
Each . . . . .  
Postage 1½d extra.  
Black bakelite instrument knobs. . . . . 1/-  
Each . . . . .  
Postage 2½d extra.

## HEADPHONES

Low impedance, double 'phones, complete with head band cord and plug. . . . . 7/6  
Postage and packing 1/- extra.  
Low impedance, single Army head-phone, with head band, but less cord. . . . . 2/6  
Postage and packing 9d extra.  
Genuine Dynamic Headphones, complete with hand band and cord. . . . . 15/6  
Impedance 90 ohms. . . . .  
Postage and packing 1/3 extra.  
Dynamic Set, consists of double head-set, as above, plus a dynamic hand microphone, complete with cord and special plug. Microphone impedance 45 ohms. . . . . 28/-  
Postage and packing 1/6 extra.  
Dynamic 'Phone Unit, as used in the head set. Ideal for a microphone. Impedance 45 ohms. . . . . 7/6  
Postage and packing 6d extra.  
Navy Magnetic Ear Pieces, 45 ohms resistance. . . . . 2/-  
Postage and packing 6d extra.  
Magnetic Telephone Sets. Consists of

## CO-AXIAL CABLE

High grade type with polythene insulation.

30/- per 60 feet

60 feet coils only.

pair of sensitive 'phones and microphone, complete with cord and plug. . . . . 25/-  
Postage and packing 1/6 extra.

## HEADPHONES SPARES

Ear caps for Army 'phones. . . . . 6d  
Each . . . . .  
Postage 3d extra.  
Diaphragms for Army 'phones. . . . . 6d  
Each . . . . .  
Postage 1½d extra.  
Rubber 'phone cords for double head sets, less lugs and tips. . . . . 6d  
Postage 3d extra.  
Standard Army type double circuit 'phone jacks. . . . . 6d  
Postage 1½d extra.

Single circuit miniature bakelite 'phone jack (used). . . . . 6d  
Postage 1½d extra.

## RECTIFIERS

Selenium Dry Disc. Half-wave, 12 volts, 50 mA. . . . . 2/-  
Postage 1½d extra.  
Selenium Dry Disc. Bridge type, full wave. 50 volts, 50mA. . . . . 3/6  
Postage 3d extra.  
Copper Oxide, bridge type, full-wave, 48 volts, 100 mA. . . . . 3/6  
Postage 3d extra.  
RESISTOR, mounting strip. Small lengths with 4 pairs of lugs. . . . . 3d

## RELAYS

P.M.G. Type, available with the following coil resistances: 15, 200, 250, 500, 1000, 2000, or 10,000 ohms. . . . . 7/6  
Postage 6d extra.  
A.W.A. 12 volt relays, DP.ST, large contacts, enclosed type. . . . . 15/-  
Postage 9d extra.  
Keying relays as used in No. 11 Army equipment (used). . . . . 3/6  
Postage 6d extra.

## RESISTORS

Heavy duty wire wound in following rating:-  
250 ohms CT 40 watts.  
1000 ohms 120 watts.  
20000 ohms 55 watts.  
30000 ohms 55 watts. . . . . 1/6  
Each . . . . .  
Postage and packing 6d extra.

## POTENTIOMETERS

Short shaft potentiometers for preset adjustments. In following values, viz.: 500, 20000, 25000, 50000 ohms, 0.1, 0.5

## RF AMPMETERS

2½" plugin type in either 0-3 or 1 amp. scales

20/-

and 2 megohms. . . . . 1/6  
Each . . . . .  
Postage 3d extra.  
PILOT LAMP HOLDERS for Miniature BC dial lamps. . . . . 6d  
Each . . . . .  
Postage 1½d extra.

PANEL INDICATORS, as used in 10-line switch board. Made for miniature E.S. bulbs. . . . . 1/-  
Postage 3d extra.

## VIBRATORS

Heavy duty double vibrator, as used in 109 equipment, 6 volt input. . . . . 12/6  
Each . . . . .  
Postage and packing 1/3 extra.  
Gas-filled 6 volt octal base vibrator cartridge, as used in FS6 equipment. . . . . 10/-  
Postage and packing 6d extra.

## WIRES & CABLES

Heavy duty 7-conductor shielded cable, rubber covered. . . . . 1/6  
Yard . . . . .  
Heavy duty twin microphone cable, shielded and rubber covered. . . . . 1/-  
Yard . . . . .  
5 conductor, rubber covered battery or speaker leads, 4ft. lengths only. . . . . 6d  
Each . . . . .  
2 conductor, rubber covered leads for microphones, etc., approx. 4ft. long. . . . . 6d  
TWO VALVE NAVY AMPLIFIERS  
Complete with 2-volt English type battery valves. . . . . 17/6  
Postage and packing 2/9 extra.

## VALVES

955 Acorn Triodes 6.3V . . . . . 17/3  
954 Acorn Pentodes 6.3V . . . . . 17/3  
446B UHF Lighthouse Triode . . . . . 32/-  
6J5G 6.3V Standard Triode . . . . . 10/-  
RL18 VHF Miniature Triode . . . . . 14/-  
RL37 9 Pin VHF Triode . . . . . 14/-  
RL7 9 Pin VHF Penthode . . . . . 14/-  
RL16 9 Pin VHF Triode . . . . . 14/-  
EF50 9 Pin VHF Penthode . . . . . 17/3  
EA50 Miniature VHF Diode . . . . . 7/6  
VR65A 4V UHF Penthode . . . . . 3/6  
CV6 UHF transmitting triode . . . . . 10/-  
PM2DX 2V Battery triode English base . . . . . 7/6  
PM625 6V Battery triode English Base . . . . . 5/-  
Postage & packing 1/- per valve extra.

## ORDER PROMPTLY

as stocks of some lines are limited.

No C.O.D. orders under 20/- please.

# RADIO

PLACE, SYDNEY

## FOR THE BEST SERVICE





Home recording allows you to make records of yourself, your friends, children speaking, singing, playing. With care, results can compare with commercial soft disc records, but have your own personal slant. It's fascinating.

# Home Recording

Here is a general article on disc recording, written especially for experimenters who have had no experience in this line. The article deliberately avoids intricate technicalities and reference to expensive equipment, but does give a good idea of what can be expected and achieved with home-made gear.

**T**HERE is an old saying which suggests that "we haven't much money, but we have an awful lot of fun." Whatever circumstances the originator had in mind, the saying fits particularly well the approach of the hobbyist to home recording.

Next month we will probably publish a further article on this general subject contributed by a reader who has operated his own commercial studio. His contention is simply that, if you want to make good recordings from the outset you forgo any thoughts of a new car and put the money instead into a commercial recorder and a good microphone and then proceed to build—or have built—the best amplifier and studio you can manage, with all "mod. cons."

## DIFFERENT APPROACH

And what we have to say in this article is not deliberately at variance with that idea. In a commercial venture your discs must be consistently good, and there is no room for explanations and repeat performances. And that means quality in studio and its appointments, in the microphone, the recorder, the amplifier, the discs, in fact, in everything through to the cue lights and stop watch.

For the home experimenter of course, such equipment can never be

more than a pipe dream. Everything has to be scaled down to conform to his pocket, or its contents. He may turn out an excellent disc, but more often has to be satisfied with something that plays back a reasonable image of the original sound. But what of it, if he has learned something new and the rest of the family are suitably intrigued and entertained?

## ABOUT DISCS

But enough of the preamble. Let us see what is involved in this business of disc recording.

Your medium, of course, is the discs which are variously known as acetates or playbacks or blanks. They can be bought commercially in approximate 8, 10, 12 and 16 inch diameters, and in varying grades. The hobbyist can usually forget the 16-inch discs, which are used widely for commercial slow-speed recordings and play for about 15 minutes. The smaller discs have an ordinary playing time at 78 rpm of about 2, 3 and 4 minutes per side. They cost a little more than ordinary commercial records of similar size, so that it becomes an expensive business to spoil too many discs during the course of one's experiments.

The ordinary commercial recording is referred to as a shellac pressing, and is essentially a hard moulded copy of the original. You can play it

with a heavy pickup, with oddly shaped needles, and handle it quite roughly without rendering it unplayable. Not that one should treat discs that way, but manufacturers have tried to make them just as tough as possible, consistent with other requirements.

But your playback disc is a very different animal. It has to be soft enough for the cutter to scribe a clean groove without chipping or blunting half-way through the operation. And because it has to be manufactured with that requirement in mind, it cannot withstand subsequent playing with a heavy pickup or a mis-shapen needle. But more of that anon.

Playback discs have a centre layer, which may be of cardboard, steel, aluminium or glass, coated on both sides with a thin layer (.006 to .01in.), of a plasticised resin or lacquer. With the return to normal conditions, most discs now have aluminium centres and a coating which is sprayed and spun to give the smoothest possible surface, which will cut cleanly without a tendency to chip or tear.

To be satisfactory, a disc must be flat. If not, the cutting head will tend to dig deeper into the material going up-hill, and conversely to cut a very shallow track when the record surface is receding from the stylus point. Records generally show minor imperfections in this respect, but obviously warped discs are to be avoided.



# Here's the Coil Kit for your

## “PERSONAL” RADIO

The restricted dimensions of the construction and layout of a personal radio demand components of the highest quality and performance. These factors have a greater reflection on the final performance than in any other type of chassis.

R.C.S. components are in conformity with the very latest developments of personal radio.


Specify R.C.S. components from your retailer and guarantee that your personal radio will have comparable performance with that produced in any part of the world.

### **This Personal Coil Kit type K118 consists of:—**


AT Right—1 Padding Condenser Type P21

2 Miniature Intermediate Transformers Type IF168 (not illustrated).

At right—1 Loop Aerial, Type F125.

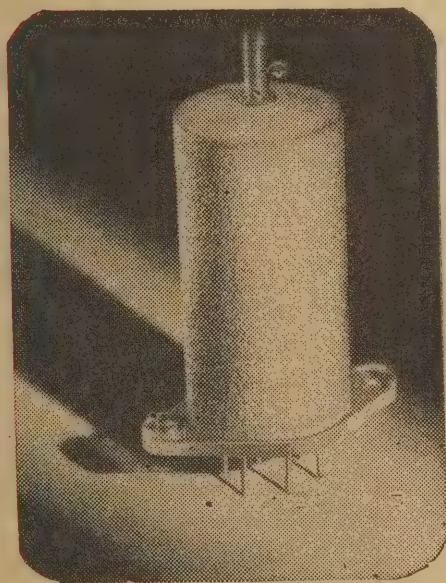

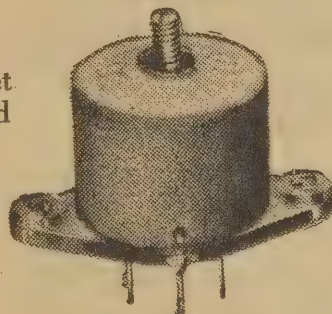At right — Midget coil (reproduced actual size).



At left—Iron clad R.C.S. Magnasonic Coil.

*These kits are available from your local retailer. Contact them NOW for full particulars and specifications.*





# MAXWELL'S RADIO


## Smallest 1 Valve Kit Ever Offered

### COMPRISING:

1 T4 Valve . . . Minimax Battery . . . Leatherette Case  
Min. Aerial Coil . . . Midget Single Gang FN Type

Complete with Circuit and Detailed Instructions

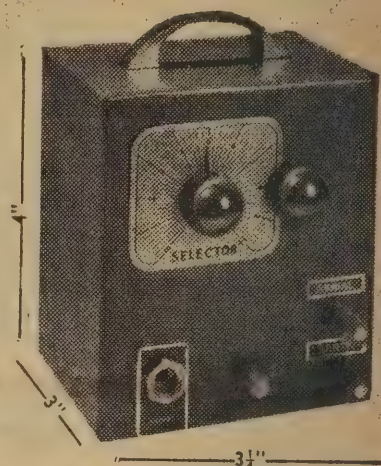**PRICE** . . . . . £5/10/- Headphones Extra 15/-  
Spare Minimax 67½ Volt Batteries 17/1.



### BLOCK CONDENSERS

.5 6000V Working -- 12/6  
2 mfd 2000 Working -- 10/-  
8 mfd 1000 Working -- 9/6  
0005 mfd 5000 Working 2/6  
1 mfd 1000 Working -- 2/6

### ENGLISH SPEAKERS

6" Per Mag by  
Waterhouse — London  
45/6  
incl. 5000 ohms Transformer

### 3 VALVE

#### ELECTRIC KIT SET

Complete in all detail.

**Price £9/10/-**

Featuring the following  
Valves: 6J7-6F6-5Y3.

This is a new type Circuit and gives excellent results. The Set is supplied with a Walnut veneered cabinet fitted with a neat dial. The whole job is easy to construct and a real money saver.

### ELECTROLYTIC CONDENSERS

8 mfd 350P.V -- 3/6  
8 mfd 525P.V -- 3/8  
8 mfd 600P.V -- 4/3  
16 mfd 525P.V -- 4/11

### 8" DYNAMIC SPEAKERS

1500 ohms Field  
5000 ohm Transformer  
50/8

### MIDGET SINGLE GANG CONDENSERS

F.N. Type  
12/6

### 0-10 MILLIAMPMETERS

2½in.

#### DIAL

Calibrated  
Brand New

**4/11**

Meter Assemblies  
For Above

**1/11**

### MIDGET COMPONENTS IN STOCK

**VALVES:** 1T4 . . . . . 22/4  
1S4 . . . . . 21/10  
1S5 . . . . . 21/10  
3S4 . . . . . 22/10  
WEARITE I.F.S. 455 KC 14/3  
"Q" Plus Osc. Coils 4/9  
"Q" Plus Loop Aerials 6/11  
Valve Sockets 7d  
Aer Coil Iron Core 5/7  
Osc Coil Iron Core 5/7  
RF Coil Iron Core 5/7  
FN Single Gang 12/6  
FN Two Gang 19/3

### 0-50 MICROAMPMETERS

English PULLIN make  
3½" DIAL . . . Brand New  
**Special 45/-**

### 0-1 MILLIAMPMETERS

English PULLIN make  
3½" Dial With Calibrations  
Brand New 20/6

### 0-10 English PULLIN Meters 3½" Dial

All Brand New 17/6  
These Meters Greatly  
Reduced.

Add Postage to all Amounts

Same Day Despatch

## MAXWELL'S

48 ELIZABETH STREET, MELBOURNE, C.1.

## RADIO

CENT 4913



It is possible to get a good idea of flatness by holding a disc so that it reflects the pattern from a steel frame window or a suitably ruled and illuminated card. A wavy image indicates that the surface is uneven.

Discs with cardboard centres are generally the worst offenders in this regard, the centre tending to warp appreciably. A further effect is that the surface is often pitted with tiny ripples caused by the texture and the absorption of the cardboard base. We have had little success with such discs, the groove depth tending to vary and the noise level to be very high.

## AGE AND TEXTURE

The age and texture of the coating is a controlling factor in the ultimate quality of a disc. If the disc is freshly sprayed just before use the coating may still contain a proportion of solvent which renders it unduly soft. The cutter will dig deeply into the material and the higher frequencies may not record well, owing to the resilience of the surface. Distortion and noise may become apparent later as the track is warped by the drying-out process.

An old disc, on the other hand, may be harder than normal, resulting in a shallow track for the same stylus pressure. And, unless the stylus is very keen and adjusted correctly, the coating will tend to chip and tear, with a resultant increase in noise level.

The quality of modern discs is more consistent with age than previously, but some variation in the behavior of the cutter under apparently identical conditions can be attributed to this cause. So buy the blanks as you need them and stick to the one brand for which you have initially adjusted your equipment.

Recordings can be made by having the stylus move laterally, from side to side, or vertically, to vary the depth of the groove. For the purpose of home recording only the lateral cut need be considered.

## TRACKING

To allow positive tracking with an average good quality pickup, each groove must have a certain minimum depth and width. In addition, it must have adequate "elbow room" for the lateral variations. Taking all factors into consideration, it is usual practice to record at a pitch of about 100 lines per inch. This is naturally one of the governing factors in the playing time of a disc.


If the grooves are spaced more closely than this the dimensions must be increased and the amplitude reduced, calling for a high degree of precision in the recording and the reproducing gear and careful control of the disc quality, if the noise level is not to become excessive. A coarser pitch, on the other hand, is simply wasteful of playing time.

The second main factor is the rotational speed of the disc. A slow speed lengthens the playing time but has the effect of reducing the physical wavelength of any frequency being recorded. The effect is naturally worse near the centre of the disc, where the lineal rate of travel of the disc sur-


face under the stylus is much slower than at the outside.

For high audio frequencies the physical dimensions of the recorded wave near the centre of the disc approach those of the stylus and reproducing needle, which simply means that they cannot adequately be recorded, even taking into account electrical compensation.

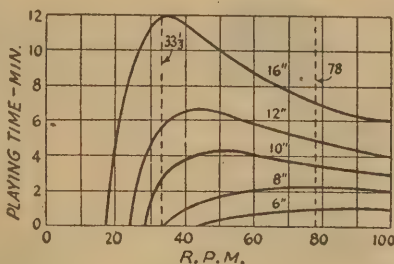
A speed of 78 rpm is recognised as standard for the ordinary commercial pressings, while 33 rpm is used for long-playing transcriptions. Assuming that frequencies up to 8000 c/s are required, longest playing time is obtained from discs up to 10 inches in diameter



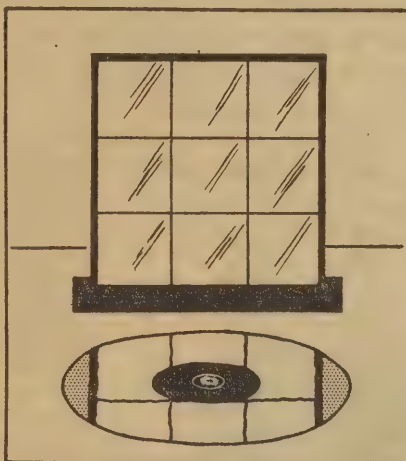This chart shows the playing time against groove speed for records of different diameters. The chart is based on 96 grooves per inch and sinoidal reproduction up to 8000 c/s.



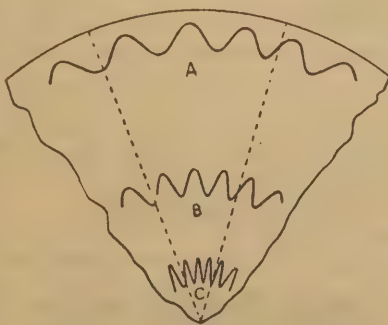To gauge the flatness of a disc, hold it so that the surface reflects the bars of a window or lines on a specially ruled card.



Curves A, B and C depict a recording of the same frequency at different groove diameters. Note how the smooth curve at A is compressed into the steep-sided pattern at C.

at 78 rpm. The reason for this is simply that the groove speed at 33 rpm near the centre of a small disc is too slow for reasonable fidelity.

With a 12-inch disc there is little to choose, the 33 rpm recording showing a very slight advantage. And, with a 16-inch disc the advantage is very clear with the 33 rpm recording. More will be said of the effect of groove speed in connection with the amplifier characteristic.

## DRIVING GEARS

Having now some idea of discs and their characteristics, the next problem is to arrange a suitable turntable mechanism. The requirements here are constant speed, adequate torque and complete freedom from vibration. Speaking generally, one seldom finds all three of these properties in adequate measure in an ordinary playback gramophone motor.

Since the stylus is actually cutting through the disc surface, the drag or loading on the turntable when recording is much higher than when playing back. Hence a motor which has adequate power for the record playing may slow down under the heavier load. Under these conditions, the governor ceases to exercise adequate control over the speed, with the result that unpleasant "wows" ruin the whole effect of the recording.

## THRUST BEARING

Under the heading of torque and constancy of speed, one must also consider any slight eccentricity of the driving gears, which will accentuate the trouble. A motor which may be satisfactory under the light loading of playback conditions, can be quite hopeless for recording purposes.

A further point is in the matter of vibration, which may come from the governor, from gears or bearings, or from the a-c windings in the fields or armature. Any such vibration of the turntable beneath the stylus causes modulation of the groove, which will further be accentuated by any inherent bass boost in the pick-up or amplifier.


The difficulties are overcome in part if a heavy turntable can be provided, either by turning from solid plate or by flowing lead into a hollow pressed metal turntable and subsequently trimming it for balance. The same driving torque is required, of course, but the inertia of a heavy turntable tends to obviate periodic variations in speed and also to absorb vibration.

Occasionally this treatment can be applied with success to an ordinary playback motor, but it is important to see that the thrust bearing is capable of taking the extra weight and that the gears are adequate for the task. But, generally speaking, the majority of playback motors are just not quite equal to the requirements.

Therefore, unless Lady Luck is co-operative, the home recordist usually has to consider buying or making a turntable for the purpose. Recording turntables are usually turned from solid metal, carefully balanced and mounted on a bearing free from looseness or rumble.

(To be continued)



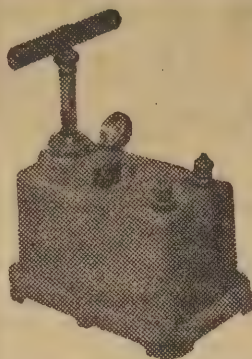

## DYNAMO EXPLODER

Made by  
Thorne and Dean

COST  
**£18/-/-**

BRAND NEW  
**37/6**

ALMOST NEW  
**30/-**

**BURGESS MICRO SWITCHES**  
British Made. Cost 22/6. 8/- each

**108 or 208 WALKIE TALKIE**  
Complete with Meter, IF's, Coils,  
Var. Conds. Etc. **32/6.**

**PEDAL OPERATED BATTERY CHARGERS.** Can be driven any Farm Machine. **£4/19/6.**

**MULTI-METERS,** Read 0.10 mill., 0.250 mill., 0.50 mill., 1250v. **32/6**



0/14v., 0/250v. double reading Meter. 1000 ohms per v. . . . . 14/6  
Excellent carrying case for same . . . . . 2/6



**MAGNETO PHONES**  
Bell  
Ringing  
Ex-Army

Cost £14  
Tested  
and  
Working  
**£5/5/-**



**Don 5 ARMY TELEPHONES.**  
ALL TESTED AND GOOD ORDER **£2/16/-.**  
Made in England. Brand New . . . . . **£4**



**OUTDOOR TELEPHONES.**  
join with wire  
and they work

**NO GEAR OR**

**BATTERIES**  
Useful sur-  
veyors, fire  
fighters  
**25/- per  
Single Set.**



**INDOOR TELEPHONES**  
NEW AND  
NOVEL.  
**NO GEAR**


**OR BATTERIES REQUIRED**  
fun, yet  
useful and  
educational  
**32/6 ea.**


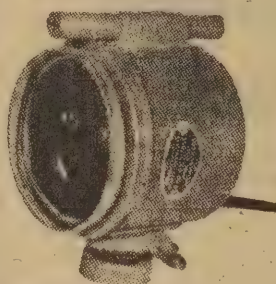
## LIFE BOAT TORCHES.



Complete with battery and globe . . . . . **3/6**




## SPOT LAMPS

Excellent for SHOOTING  
FISHING and HIKING

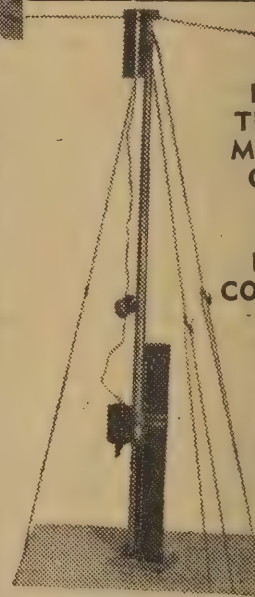**17/6 each**

**ARMY HIGH GRADE PRECISION STEEL LEVEL MEASURES**  
Angles  
Flat  
or  
Perpendicular  
Cost  
**£7/-/-.**  
**22/6 ea.**



**LIFE BOAT TRANSMITTER. ONLY A FEW LEFT. COMPLETE WITH VALVE.**

**12'6**

## BARGAIN BULLETIN

## CHOCK FULL OF BARGAINS

### FILL IN AND SEND

To Waltham Trading Co. Pty. Ltd.,  
393 Flinders Street,  
Melbourne, C.1, Vic.

Please send me your BARGAIN BULLETIN, chock full of Radio, Electrical and Campers' bargains, post free.

Block Letters

NAME .....

FULL POSTAL ADDRESS .....

State .....

**WALTHAM TRADING Co. Pty. Ltd.**

**393 FLINDERS STREET, MELBOURNE, C.1.**

**MU 4719**

*Mail Orders Carefully Packed and Despatched.*



# FROM THE SERVICEMAN WHO TELLS

Some relatives in the country insisted that I should spend a weekend with them and asked, as an after-thought, that I bring something to test Mr. So-and-so's amplifier, which was giving him trouble. Mr. So-and-so was a nice chap and I would be helping him and everyone else concerned if I could rectify the trouble. You know how it is in the country. So, in with the "odds and sods" for a weekend jaunt. I packed in the multi-tester and a variety of tools and spares to complete what I hoped would be a simple job.

ON the Saturday morning, thinking to get the job over and done with, I went to see Mr. So-and-so and enquire about the cause of all his trouble.

It turned out that he owned the local public hall, and his latest venture was to instal an amplifier system with the idea of running small functions and dances for charity. You know the idea. A small charge to go in, practically no costs and amplified recordings to substitute for an orchestra.

Without saying as much to our friend, I thought him rather an optimist. I stand to be corrected but have doubts about the success of such a scheme—unless one of the locals happens to be a genius as an MC. People may dance to canned music occasionally in an informal house party but, in a public function, they prefer a live orchestra on the stage—even if it is only a piano and violin combination.

## THE PROBLEM

What all this has to do with radio is rather beyond me, but even a radio serviceman sometimes has opinions of his own.

Mr. So-and-so explained that he had bought the amplifier from a chap in the neighboring town and had installed it himself. Said he: "It seemed terribly loud when I first heard it but it gets harsh when I turn it up in the hall."

This was not a startling statement, by any means. Even a couple of watts sounds awfully loud in a small acoustically "live" room. Heard in a large hall, the same output is lost in the open expanse of free air and the

lofty ceiling. Add to that the absorption of an audience and the shuffling of a couple of hundred feet and you may have to listen hard for the tempo.

Mr. So-and-so's amplifier turned out to be a push-pull circuit of fairly standardised pattern and with a power output of about 13 watts. This should have been enough for the particular hall, but I must say that the output did not sound very high in the quiet hall before overload distortion became evident.

## INSTALLATION

The amplifier was actually installed in a room which housed the light switches and was intended to serve as an operating booth for film shows. The speaker was installed in a good position above the proscenium at the other end of the hall.

It is worth noting, in passing, that a high position for such a speaker is always desirable. Point it obliquely downwards towards the far end of the hall and there is a good chance of people at the back hearing the sound to good advantage without blasting the ears off those at the front.

What interested me more was the method of conveying the output from the amplifier to the loudspeaker. Closer investigation showed that the output transformer was mounted on the amplifier chassis, the secondary leads being extended to the voice coil. The speaker itself was a prewar 12in. permanent of fairly good design and with a voice coil impedance, from memory, of just over one ohm.

While this speaker may not have been right up to the standard of mod-

ern types, as far as sensitivity goes, I knew that it could not be blamed for the obvious lack of volume from the amplifier system. So I checked the connecting leads.

Our friend had apparently bought a roll of twisted light flex and run it from the amplifier, up through the ceiling and along the side of the hall, down the full length of the building and ultimately to the loudspeaker. He had certainly gone to a lot of trouble to put the lead in a safe and tidy place and held it rigid by insulated staples. Stepping out the distance I guessed that there was the best part of 100 feet of twisted pair between amplifier and speaker.

## FLEX CABLE

The flex contained 10 strands of what I guessed to be 30-gauge wire, and it was immediately obvious that considerable loss was occurring in the d-c resistance of this lead.

Wire of this gauge has a resistance of about 100 ohms per thousand feet, so that a 10-strand cable would have a resistance of about 10 ohms per thousand feet. In this installation there would have been close on 200 feet of wire—100 feet each way—in circuit between the amplifier and voice coil. The resistance of the cable, therefore, would approximate two ohms.

So we have the amplifier valiantly delivering its output into a secondary load of about 3.2 ohms instead of 1.2 ohms. The reflected load across the primary would be, theoretically, 26,000 odd ohms instead of the requisite 10,000 ohms for the particular output valves. And as for power output—well I guess that one might get about half the expected audio with such a drastic mis-match.


## CABLE LOSS

So our friend was feeding, say, seven watts into one end of the twisted pair, and, of this, only a portion was serving to operate the voice coil. The rest would have been dissipated in the 2 ohms resistance of the cable. Hence only three or four watts would have been actually available to the loudspeaker.

I may appear to be devoting a lot of space to this matter, but it applies to anyone who may wish to operate a loudspeaker remote from an amplifier or radio set.

Where the connecting leads are more than two or three feet in length, it is wise, as a general principle, to mount the output transformer on the chassis and extend the secondary leads. In

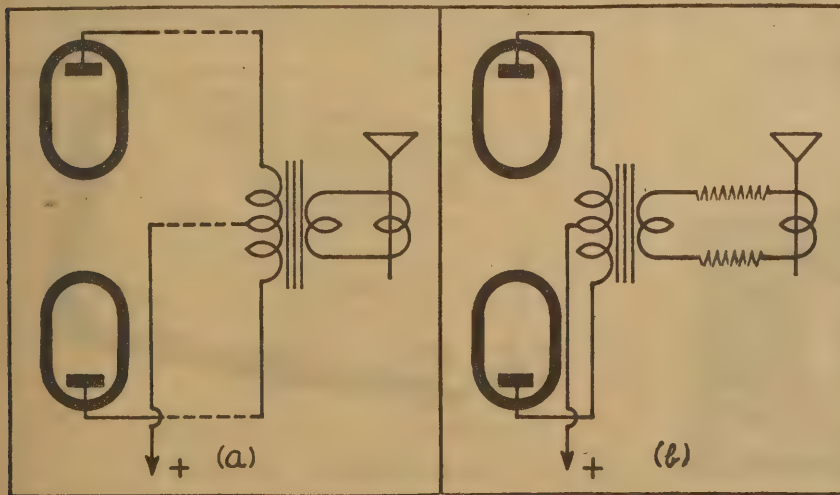Extension of the plate leads, as at (a) involves some risk of instability. When voice coil leads are extended, as at (b), the resistance of the leads must be kept small in comparison to the impedance of the voice coil.








## 4 VALVE A.C. KIT SET
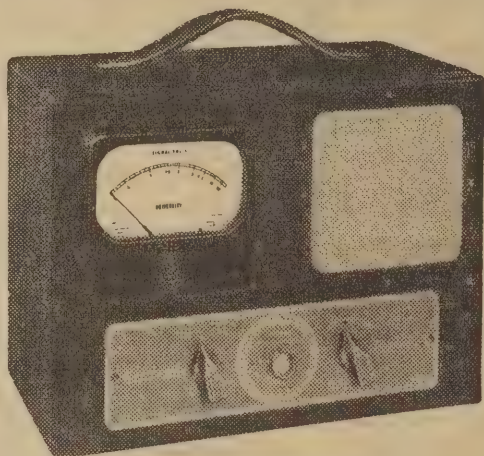
### Neat Kit is Easily Assembled


If you would like to build a really professional receiver, this 4-valve broadcast operated mantel set for 240-volt A.C. operation is ideal. In plastic cabinet. Colours: ebony, walnut, green or cream. This set comes complete with all necessary parts, including valves and Rola 5in. permag speaker. Circuit diagram and building instructions are included.

Price, £12/15/3 (plus freight). Green or cream, 15/- extra.



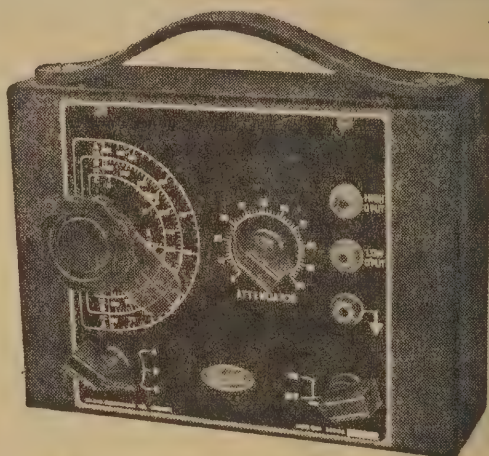
### SIGNAL TRACER

Tracing the signal RIGHT THROUGH the radio receiver from start to finish, the new "University" STB Signal Tracer makes fault-finding easy and quick. When the probe strikes a faulty section, indications are given on both meter and speaker. Portable—light—sturdily constructed, the STB is the versatile post-war service instrument you MUST have. Ask for Model STB "University" Signal Tracer. Price. £14, plus tax.


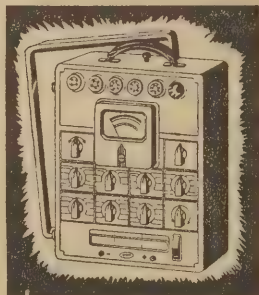
### NEW OSCILLATOR KIT

Designed to give years of accurate service yet simple to build at home with a few ordinary tools, the new University OKI oscillator kit covers all fundamental frequencies in the average receiver. Dial is specially calibrated. Kit uses standard batteries. Every OKI kit is complete with instruction book giving pictures and wiring diagrams, and all parts at the new low price of £7/10/- plus tax.




### UNIVERSITY SUPRETESTER (Left)

This is the most versatile Valve and Circuit Tester, featuring the extraordinary roller test chart—entirely new to Australia. Send for free descriptive brochure on this and other "University" instruments.

Price AC only .. .. £28/10/- plus tax.  
AC/Vibrator .. .. £30/0/- plus tax.
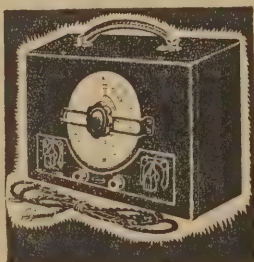
### UNIVERSITY OSCILLATOR

Model Job (Right) An extremely efficient instrument providing RF and AF signal frequency range from 160 K.C. to 32 m/cycles. Battery operated. £13/19/- plus tax. Send for free illustrated brochure.



### ELECTRONIC PARTS PTY. LTD.

E.S. and A. Bank Building,  
BROADWAY, N.S.W.

Phone: MA1661  
Telegrams: ELECPARTS SYDNEY.

WHOLESALE DISTRIBUTORS OF  
EVERYTHING IN RADIO



the first instance, this removes the danger of having long flex leads around the place carrying up to 400 volts of d-c plus the audio "ergs." More important still, it minimises the risk of instability which always attends the extension of plate leads over long distances.

But—and it is a very big "but"—watch the resistance of the wiring to the voice coil. There is certainly no d-c to worry about and very little risk of instability troubles. But—you are now delivering the power into a load of very low impedance, and it is essential that the d-c resistance of the connecting leads be small compared with the impedance of the voice coil.

## STANDARD PRACTICE

Our friend was particularly unlucky in that he was using a very low resistance speaker with a long length of light flex. The loss would still have been serious with a 2 or 3 ohm voice coil, but of little importance with one of eight or more ohms.

Standard practice in sound engineering is actually to fit amplifiers with output transformers with a secondary winding intended to operate into about a 500 ohm load. The loud-speaker system is then fitted with a second transformer to give an impedance transformation from 500 ohms down to the impedance of the voice coil or coils, as the case may be. The lead connecting the two transformers is then referred to as a 500 ohm line, because it operates from a 500 ohm source, and is terminated by a 500 ohm load.

Actually, one could choose an intermediate impedance value for the line at anything from a couple of hundred ohms to a thousand ohms, but the conventional 500 (or 600) ohms is a nice round figure, which has come into general usage. The impedance of a 500 ohm circuit is high enough not to be adversely affected by the d-c resistance of a few hundred feet of lead. But, the impedance is not so high that losses are likely to occur due to capacitance between the leads.

## 500-OHM LINES

Coming down to finer points, one can run unshielded input leads and use switching and attenuator circuits in a 500 ohm line, which would be very difficult, if not impracticable, in a circuit of much higher or lower impedance. So much for 500 ohm lines and networks which so many folk appear to regard with technical awe.


Actually, it is dubious practice to use a 500 ohm link where the length of connecting cables is not excessive, unless it is for reasons of convenience or versatility. Matching transformers average only about 80 per cent. efficiency so that the losses involved in an extra and unnecessary transformer may be equal to or greater than those in a direct low impedance cable.

Looking back through the pages, as I type, I feel that this discourse is truly encroaching on grounds sacred to the Technical Editor, but I must crave his forbearance. Maybe it will be a pleasant change from the eternal round of shorted bypass condensers

and pesky open-circuited coils. But I must conclude the matter.

Appreciating the difficulty which faced Mr. So-and-so, I obviously had to find a way out, and 500 ohm line transformers don't grow on trees in the country—or the city either, for that matter. There was nothing else for it.

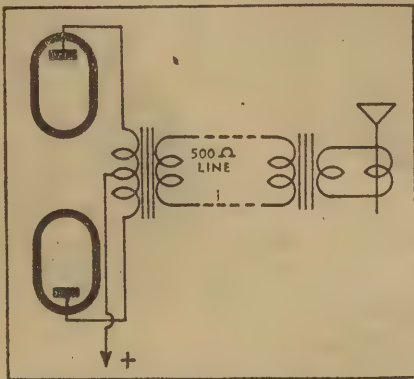I removed the output transformer from the amplifier and clambered up to install it in its original position on the loudspeaker. The amplifier wiring was rearranged to lead the valve plates to the output socket and thence via the twisted cable to the loudspeaker. Instead of making a direct connection to the plug, I wound about



Losses due to resistance and capacitance of extension leads are avoided by stepping down to an intermediate impedance value, generally about 500 ohms.

20 turns of enamelled copper wire round a pencil and stretched it slightly to link the plate pins with the output socket. The idea was to make it function as an RF choke.

A third lead was obviously necessary for the B-plus line, and this was run through to the speaker with some single core electrical cable which happened to be available. When the amplifier was switched on, there was fortunately no evidence of instability, either in overheating of the valve elements or a change in plate current as the plates were shorted across.

But the volume was there in no uncertain manner, and I left our friend in a very happy frame of mind. It is good for one's ego to be the hero of the piece rather than the necessary evil who fixes the radio and walks off with a proportion of the "hard-earned."

★ ★ ★

## A SECOND JOB

News of one's arrival travels rapidly by "bush telegraph" in small country towns. Especially when one happens to be a radio serviceman, and the town in question boasts "no such animal." Hardly had I finished lunch when a farmer from a couple of miles out came looking for me and asked me to look over his set. "It still goes," he said, "but doesn't get all the stations like it did when new."

So out we went to his small general farm. I must say, in all fairness, that the family turned on a delightful afternoon tea and subsequently loaded

(Continued on Page 78)

# "BRS" JUNIOR RECORDER & PLAYBACK UNIT

\* Suitable for use with Recording Amplifier described in September issue Radio & Hobbies.

- Records in the home.
- Immediate playback.
- Plays any record.



The "BRS" Junior Recorder and Playback Unit may be fitted to any standard radio-gram or used with most conventional receivers. The unit plays its own or commercial recordings with high quality and fidelity.

Recording discs are supplied in 3 sizes: 8", 10", 12" for amateur use and 16" for pro-

fessionals. A hardening fluid for record preservation is also available at low cost. As the initial outlay and cost of discs is reasonable the "BRS" Junior Recorder and Playback Unit is a sound investment in every way.

SOLE DISTRIBUTORS FOR N.S.W. & Q'LD.:

**BIRNBACH RADIO** CO. (A/SA) PTY. LTD.


5TH. FLOOR, 55 YORK STREET, SYDNEY, N.S.W. TEL. BX2500

**A. E. HARROLD**

123 CHARLOTTE STREET, BRISBANE, Q'LD. TEL. 82729



# Get Started On

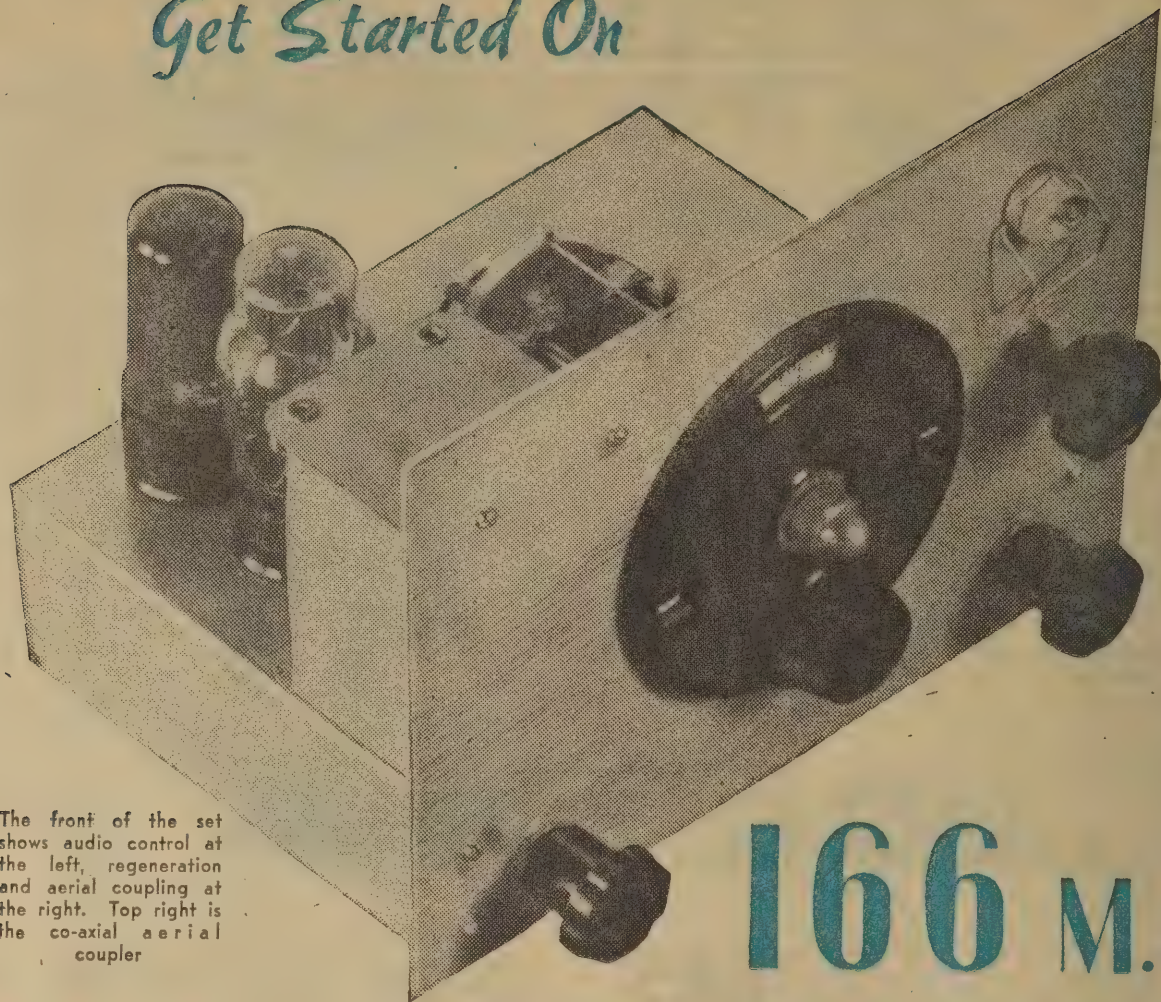

The front of the set shows audio control at the left, regeneration and aerial coupling at the right. Top right is the co-axial aerial coupler

## 166 M.C.

**This article describes the construction of a simple super-regenerative receiver to operate on the 166 megacycle amateur band. Many stations are to be heard operating there these days, and both amateurs and listeners will find much to interest them in this easy-to-make set.**

**T**HE signs of the times as represented on the ultra-high frequencies are to be seen in the activities of licensed amateurs these days.

While the DX bands are and always will be popular, an increasing number of amateurs is exploring the possibilities of the UHF bands. These are, in effect, in the vicinity of 50 and 166 mc, as still higher frequencies, which amateurs can use, call for equipment not normally in the possession of the average man.

### THE 50MC BAND

The 50 mc. band, once the realm of modulated oscillators and super-regenerative receivers, has now graduated into the realm of stabilised technique. No one contemplates using such elementary gear now on 50 mc. Almost without exception, transmitters for this band are crystal controlled, and receivers are superhets, or superhet converters.

But 166 mc. is a different story. It is much more difficult to make crystal-controlled transmitters for this band, and, for that matter, superhet receivers. Certainly they will cost more. For this reason alone and also because it is now the "pioneer" UHF

band, as was the 56 mc. before it, the use of simple gear on 166 mc. must be considered legitimate.

The obvious difference between the two types of equipment is that modulated oscillators are nearly always accompanied by frequency modulation, which makes them very broad, against the sharp, clean carrier which marks the stable crystal-controlled transmitter, or its equivalent.

Super-regenerative receivers, particularly those of the type described here, use an oscillating detector, which will radiate energy just as will a small transmitter. This radiation will cause interference with other receivers

operating in the immediate vicinity, which can be very strong and troublesome under certain circumstances. However, these are things one must be prepared to accept as more or less necessary evils, and with a little co-operation and care, their effects can be reduced considerably.

### SIMPLICITY

On the credit side, the simple apparatus can be made to operate well with very little trouble, and is cheap to build. To the man who has invested most of his available money in apparatus for the lower frequency bands, this is quite an item, and must be considered by those who normally, and with some justification, frown on the use of any gear which tends to interfere with the work of others.


At the same time, we must remember that amateurs are entitled to experiment—something we tend to forget in a world of regular frequencies, communication, and schedules. They are allowed to use simple gear on the 166 mc. band, whilst on the 50 mc. and lower, stabilised transmitters and non-radiating receivers are required. For this reason alone, we have no qualms about describing the receiver illustrated herewith.

In our Short Wave Handbook, to be published almost immediately, we will give details of a simple transmitter to operate in conjunction with this set, and from the same power unit.

by  
**John Moyle**  
**VK2JU**


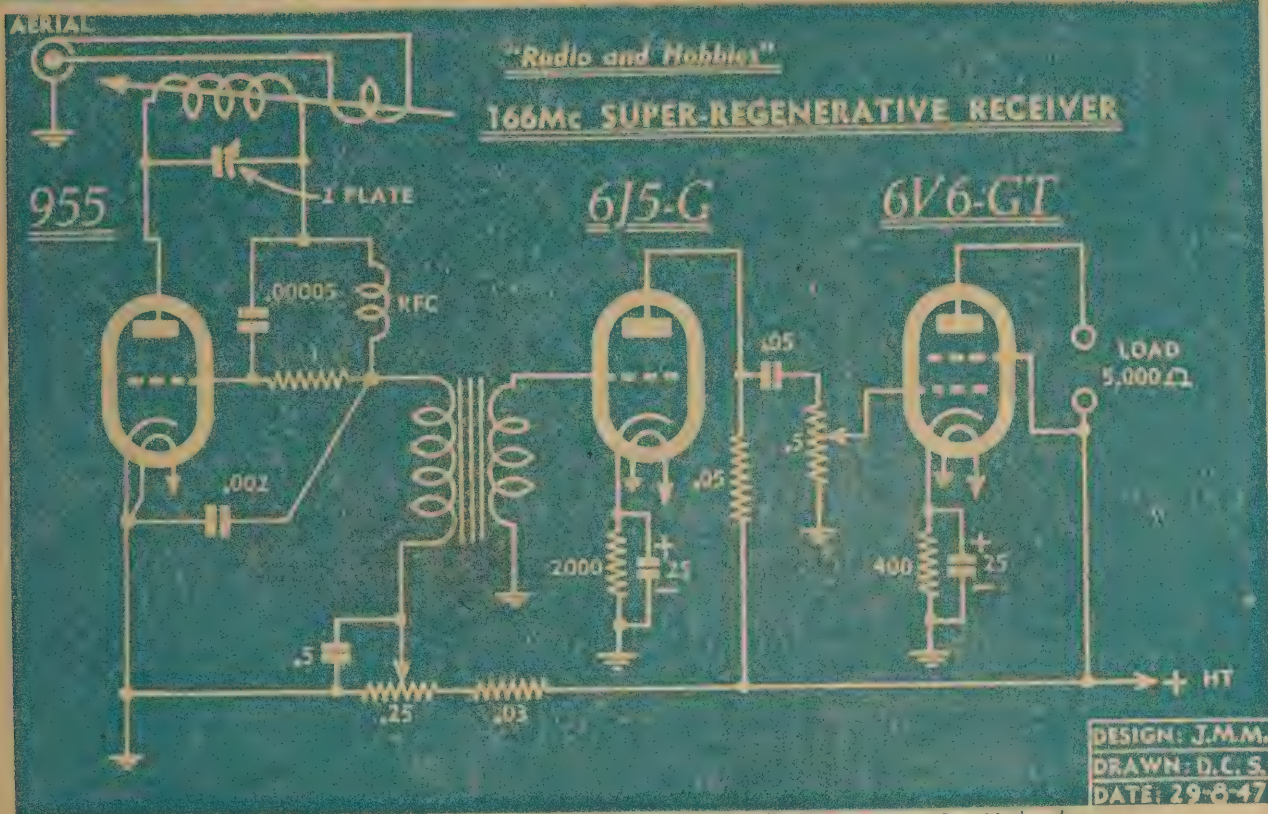
## CIRCUIT DIAGRAM OF THE 166 m.c. RECEIVER



There is little difference between this circuit and the standard arrangement for this band.

There are very few variations one can apply to a simple super-regenerative receiver. General practice has standardised on the self-quenched type, as the alternative to a set using a separate quench oscillator. The latter uses more equipment, and its advantages are doubtful.

### OSCILLATION FREQUENCY

The simplicity of the detector circuit shown here is obvious. We do not intend to describe fully the theory of super-regeneration, as it is fully set out in various handbooks, and isn't a thing to be covered in a few words. There are two oscillation frequencies involved, firstly the signal frequency, and secondly the quench frequency. This latter tends to send the detector rapidly in and out of oscillation at a rate equal to the quench frequency. Thus the set is maintained in a very sensitive condition, but obviously, as it is connected directly to the aerial circuit, radiating all the time, after the manner of oscillating valves.

To make the detector super-regenerate, the grid leak as you will notice is connected to a positive voltage, rather than to earth as is normally the case. So don't think this is a circuit error, assuming you haven't met up with a circuit of this type previously.

We have used a 955 Acorn valve here because it is about the best type to use, and is now obtainable for something less than the price of normal receiving valves. The 9002 is another valve which could be used with equal success, being very similar electrically.

For one thing, they are harder to get oscillating, will require more voltage, and will therefore radiate much more strongly. The 955 will oscillate readily with about 25 effective volts on the plate, and the amount of power fed into the aerial circuit is therefore very small indeed. The CV6, or 7193, is a special form of the 6J5, and will probably work just as well as the Acorn, and with about the same voltage. The layout must be modified to use this valve.

## TUNING CIRCUIT

The tuning circuit is very straightforward. Variations will be found at times in which, for instance, the R.F. choke is connected to the centre of

the coil. While theoretically this is the logical place for it, in practice we didn't find it made any difference, and it is generally more convenient to connect it directly to the grid, as shown. Mounting the valve socket upright, and back of the tuning condenser, means that grid and plate leads to the valve are kept very short—an essential precaution on this frequency. The plate lead is less than one inch long, and the grid lead is actually composed of the grid condenser itself, with the pigtails cut short.

The other fixed condenser, above the chassis, and visible in the illustrations, is the .002 mfd. condenser, which is earthed to the same spot as earths the cathode. The grid leak

## PARTS LIST

- 1 Chassis, 8in. x 6in. x 2in.
- 1 Front panel, 9in. x 6½in.
- 1 2-Plate midget variable
- 1 Audio Transformer.
- 1 Reduction drive dial.

CONDENSERS:

- 2.25 mfd. 40 PV. electrolytic, 1.5 mfd.  
tubular, 1.05 mfd. tubular, 1.01 mfd.  
tubular.

- 1 .002 mfd. mica, 1 .00005 mfd. mica.

**RESISTORS:**

- 1 .1 meg., 1 .05 meg., 1 .03 meg., 1  
2000 ohm, 1 400 ohm.  
1 .5 meg. Potentiometer, 1 .25 meg.  
potentiometer.

**SOCKETS:**

- 1 Acorn valve socket, 2 octal, 1 5-pin.

VALVES:

- 1 955, 1 6J7G, 1 6V6GT.

SUNDRIES:

- 5-pin plug, 1 insulated coupling, 1 coaxial cable panel mounting socket, 3 knobs, 4in. insulated rod, 1/4in. dia., resistor strip, 6in. shielded wire, panel mounting bushing, hook-up wire, spaghetti, nuts and bolts, &c.

COIL DATA:

- Tuning coil: 3 turns  $\frac{3}{8}$  in. dia., 18 s.w.g. wire.  
Aerial coil: 3 turns  $\frac{1}{2}$  in. dia., 18 s.w.g. enclosed in spaghetti.  
R.F. Choke: 23 turns closewound,  $\frac{1}{8}$  in. dia., 22 s.w.g.




# EDDYSTONE

## TRANSMITTER COMPONENTS

"Eddystone" components, precision manufactured, are designed to meet the needs of the Radio Engineer and Short Wave Experimenters. "Eddystone" products are renowned for the highest degree of efficiency and for outstanding performance.

### LOW LOSS COIL BASE

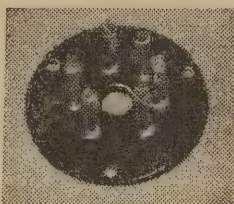


Chassis mounting coil socket for use with Eddystone Low Loss Interchangeable Coils. DL9 insulation with three fixing holes. A  $1\frac{1}{4}$  in. diameter hole is required in the chassis. Cat. No. 964.

### MINIATURE STAND-OFF INSULATOR

A midget insulator made from Frequentite with N.P. brass parts. A useful accessory in the design of ultra short wave receivers and transmitters. The new quality Frequentite closely approaches quartz in its characteristics as a low loss dielectric at high frequencies. Cat. No. 1019.



### MOULDED INSULATOR

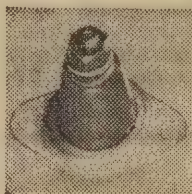

This moulded insulator will be found extremely useful as "Stand-off" Insulator, "Lead-through" or "Terminal Post." It is supplied in two colours, red or black. Construction is such that neither the insulator portion nor the screw will revolve when wires are attached and tightened. It is made with reversible fittings so that it can be mounted above or "through" the chassis. Each insulator is provided with two 2BA nuts and shake-proof washers. They are satisfactory for 1000 volts working.  $1\frac{1}{4}$  in. high,  $1\frac{1}{4}$  in. between fixing screws.

Cat. No. 564, Red. Cat. No. 565, Black.

**CHANDLERS Pty. Ltd.**

Brisbane, Toowoomba, Warwick,  
Bundaberg, Rockhampton, Townsville, Cairns.

**JOHN MARTIN Pty. Ltd.**

116-118 Clarence Street, Sydney.  
Telegrams - Jonmar, Sydney.  
BW3109.

**JOHN MARTIN RADIO and ELECTRICAL CO.**

360 Post Office Place, Melbourne.

bridges from the grid terminal across to the end of the R.F. choke, which lies parallel to the front panel immediately below the tuning condenser shaft. You can see the front end of the choke in the pictures, its rear end being obscured by the tuning condenser.

### TUNING CONDENSER

The tuning condenser must be insulated by mounting on a strip of good material, of which there are plenty of samples available from disposals equipment. Even good bakelite would probably be OK. An insulated coupling must be used for the shaft, and it is best to mount the whole assembly, as we have done, well back from the panel. This condenser is a 2-plate, midget type.

The tuning coil, as will be seen, is mounted directly on the tuning condenser, and juts out at the side, so that it may be coupled easily to the aerial coil.

We mounted the aerial coil by slipping a piece of insulation tubing over the end of the shaft, and fixing the ends through a couple of holes with a drop of acetone cement. The shaft is rotatable from the front panel, and supported in a tight-fitting bearing, taken from an old volume control. Some kind of spring tension may be fitted against the shaft if it is too loose, to prevent the loop from falling down under its own weight.

### AERIAL COUPLING

This aerial coil adjustment is important, so take your time over it, and make a good job. Some insulated covering should be used on the wire to prevent it shorting to the tuning coil.

Use heavy gauge wire for both these coils—at least 18 gauge. Silverplated copper is best, although enamelled wire will do just as well in this circuit.

The remainder of the circuit is self-explanatory. It might be possible to do without the last audio stage, although for loud-speaker work, the extra audio gain is valuable.

The audio transformer is a necessary component, but almost any type will serve. Ours was actually a sample job we have had for years, and there is no significance attached to its type. A good one would be the old Philips type, of which there are many in circulation.


We used a co-axial connector for aerial connection—a pair of terminals would do here just as well. Insulation is not so important, as the impedance in the aerial circuit, and consequently the R.F. voltage is quite low.

The chassis is large enough to build a small power supply on the vacant portion, using a 40 mill type transformer as sold for mantel sets. However, we used a separate supply built on a chassis the same size as that of the set, with a switch to change it across to the transmitter as required. This supply also houses a small loud-speaker, so that the three units make up a self-contained station. You can please yourself entirely on this point. Any voltage from 150 to about 300 will be OK, the only difference being in the amount of audio available.

The two major points in getting the set to operate are, firstly, in the



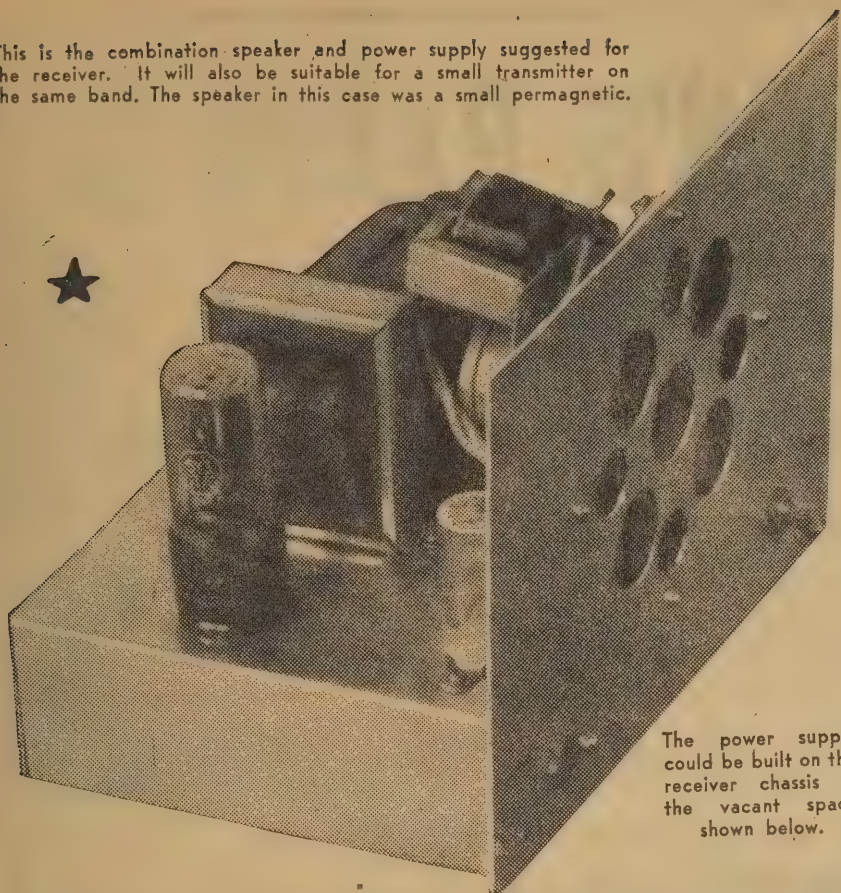This is the combination speaker and power supply suggested for the receiver. It will also be suitable for a small transmitter on the same band. The speaker in this case was a small permagnetic.




The power supply could be built on the receiver chassis in the vacant space shown below.

adjustment for best super-regeneration and, secondly, finding the 166 mc band.

If the values have been as set out, including the coil data, the set should operate immediately. On advancing the oscillation control, the valve will first of all oscillate normally, possibly with a small "pop" to indicate this condition. Advancing the control still

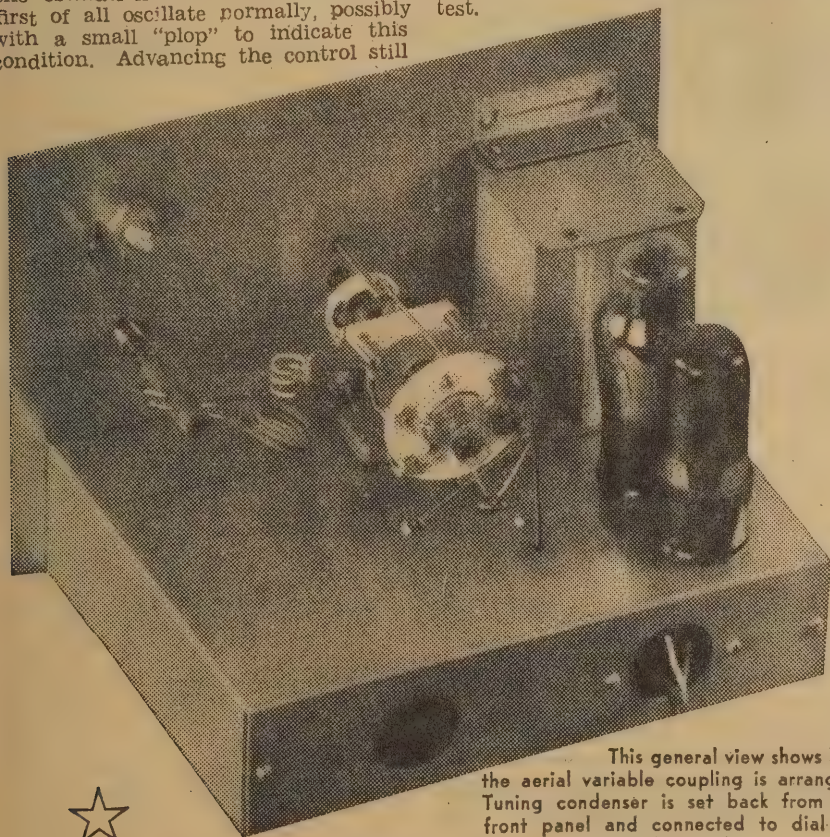further will commence a gradual rushing sound, building up to considerable proportions. This indicates super-regeneration, and is a necessary condition for proper reception. The aerial coil should be moved away from the tuning coil while making this first test.



This general view shows how the aerial variable coupling is arranged. Tuning condenser is set back from the front panel and connected to dial via a flexible coupler.



Permanency of Insulation resistance depends primarily upon the complete exclusion of moisture from the capacitor element. Tests have proved that Ducon capacitors can withstand many cycles of the standard humidity cycle test without any mechanical or electrical deterioration.

Type PC Tubular capacitors have been designed to meet the recent exacting demands of the electronic industry for a high grade capacitor.

We are in an excellent position to supply capacitors for any specification and provide the answer to such problems as space or weight limitation and temperature extremes, severe vibrations, altitude, humidity.

#### CHARACTERISTICS

- Small size.
- High Insulation Resistance.
- Low Price.
- Conservative Dielectric Ratings.
- Moisture Proof.
- Continuous Operation at 60 deg. C.
- Low Power Factor.

# DUCON

Capacitors



DUCON CONDENSER LTD.  
73-91 Bourke St., Waterloo.

RH2.



# FERGUSON'S RADIO PTY. LTD.

RELEASING

## "VIBRAPOWER"

### VIBRATOR POWER SUPPLY TYPE V.S. 140.

**GENERAL.** The Ferguson "Vibrapower" unit is a compact, self contained vibrator operated power supply designed to operate from a standard 6 volt accumulator.

The unit has been designed to simplify the conversion of battery operated radio receivers over to vibrator operation. However, it may be used as a replacement for "B" batteries in portable equipment, or as a complete power supply for standard vibrator receivers.

**DESCRIPTION.** A fabricated steel case measuring 9½" x 6" x 4" finished in grey wrinkle duco, and fitted with rubber mounting feet, houses the unit. A carrying handle is also fitted to the case for ease in transportation.

Weight . . . . . 10 lbs..

**ELECTRICAL SPECIFICATION.** Two output circuits are provided, one is a filtered low tension 6V filament supply, which can be used with current drains up to 300 mA. The other is the normal high tension supply, which will deliver an output current of 20 mA (max). The output voltage under these conditions is 140 volts D.C.

Both L.T. and H.T. outputs are adequately filtered for A.F. and R.F. noise

**INPUT**  
6v. at 0.95 Amp.

**OUTPUT**  
140v. at 0.02 Amp.


**CONNECTIONS FOR USE.** The input and output connections are made by means of a standard six pin plug, which is inserted in the socket provided at the end of the unit. Wiring to the plug is shown in the accompanying diagram. It is important that the recommended wiring to the receiver be observed, otherwise trouble may be experienced due to false earths, and "hash" may become apparent over portions of the short wave band. No trouble is experienced if the wiring diagram is adhered to.

**OPERATION.** Since the output voltage polarity is determined by the polarity of the input, it is important that the supply leads from the radio set are connected to the correct terminals on the accumulator. Incorrect connection will result in non operation of the radio, and damage may be caused to the condensers and vibrator cartridge in the "Vibrapower" unit.

One of the outstanding features is that either a Ferrocart Type P.M. 413 or an Oak Type V5124 vibrator cartridge can be used without any change in the operation of "Vibrapower."

When installing or replacing a vibrator cartridge, the six screws holding the base of the case should be removed, the lid slid off, and the cartridge inserted.

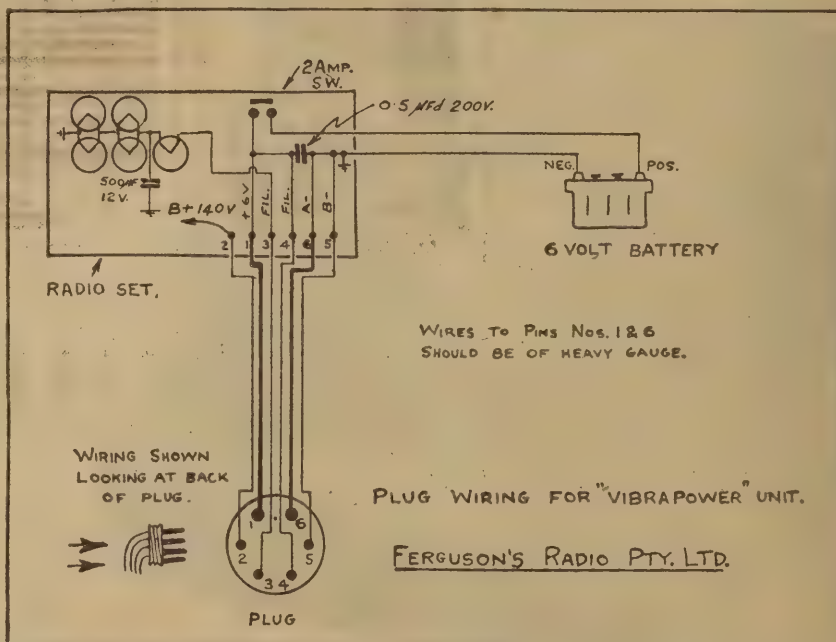AVAILABLE LEADING  
WHOLESALE AND  
RETAIL HOUSES.



FACTORY REPS.: N.S.W., VIC. & QLD., ELECTRONIC INDUSTRIES IMPORTS PTY. LTD.  
S.A., APEX AGENCIES.



Leaving the matter of the aerial for the moment, you should find 166 mc with the tuning condenser about half-way in. There are generally a number of stations operative from 7.30 to 9 almost any night, and often outside these hours, of course. In addition, there is the "SY" beacon, a harmonic which can generally be heard at 166.5 mc.

When listening for stations, the aerial coil is moved close to the tuning coil. When very tightly coupled, it will probably pull the set out of oscillation, and you must back it off until oscillation recommences.

Experiment with the controls will show that best signals are heard with the aerial coupled as closely as possible. As soon as a station is tuned in, it will automatically reduce the rushing in the speaker and, on strong stations, this rush may stop altogether.

The adjustment of the aerial control will soon be found to be the most important. It is possible to leave the oscillation control well advanced, and rely entirely on the tuning control and the aerial coupling control. Only practice will allow you to work out the best way to handle them.

### THE AERIAL

The aerial is an important part of the set-up, and calls for special mention. Unlike the "short waves," one does not merely string up a wire and tune in. A resonant aerial must be used.

This consists in simple form of a half-wave antenna cut in the centre to form two quarter-waves with the ends separated by about one inch. A length of co-axial cable is connected to the two ends, the outer to one, and the inner to the other. The other end of the cable is connected to the aerial socket or terminals, as the case may be.

The best set-up is one in which the aerial is mounted outside well clear of the ground. However, in the case of nearby stations, it is quite possible to use an aerial inside the room mounted clear of obstacles. The co-ax cable can be replaced quite successfully with two lengths of hook-up wire loosely twisted together, about six times per foot, to serve as a feeder. If you are in an elevated locality, you should be able to hear stations on such an aerial. Most transmitters have vertical aeriels, so arrange for yours to be vertical. When you have tuned in a station, you will observe many interesting effects by rotating your aerial, and noting the changes in signal strength.

The aerial elements can be made of stiff wire mounted on stand-offs, and supports by a wooden batten. The feeder should come away at right angles for at least six feet or more before it drops into the receiving room.

The exact length of the aerial sections will depend largely on the exact frequency used. A good length for a start is 16½ inches for each quarter-wave, making an overall length for the half-wave of 33 inches.

Various combinations of aerial elements can be made to form simple beams, with much improved results. You are advised to read the various amateur handbooks on this subject, as there is far more information given there than we have space for in this article.

# Homecrafts

## FOR BETTER VALUE




*Disposals Valves at  
Reduced Prices . . . .*

E.F. 50 High Gain R.F. PENTODE . . . . .	17/3
EA50 SINGLE DIODE . . . . .	17/3
VCR 87 6" CATHODE RAY TUBE . . . . .	37/6*
VCR 139 A 2 3/4" CATHODE RAY TUBE . . . .	20/-
41 MXT OUTPUT PENTODES . . . . .	14/-
807 Beam Power PENTODES . . . . .	16/6
VCR 112 5" Cathode RAY TUBES . . . . .	30/-*

\* Plus Sales Tax



*The Latest in Radio Testing Equipment  
"PALEC" v.t. (Probe) MULTIMETER*

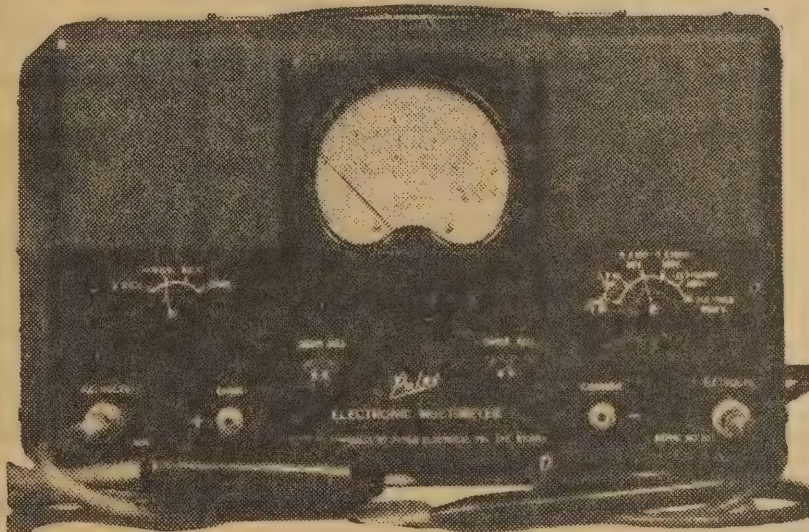

**MODEL V.T.M.** Every Amateur will find this the most useful test instrument yet devised—WRITE US FOR FULL PARTICULARS. This is a winner! and only **£29-10-0**

Plus Sales Tax



## SPECIAL SNAPS!

MULTIMETERS with 10 Ranges housed in Black Crackle Finish Cast Aluminium Case **£6/19/6** Magnetic PICK-UPS .. 25/6 5 Way BATTERY CABLE 9d. per yard.

BRADLEY POTENTIOMETERS, 10,000, 20,000 and 30,000 Ohm .. . . . 1/11.

### Homecrafts Pty. Ltd The Radio Specialists

Head Office: MELBOURNE, 290 Lonsdale Street and at 211 Swanston Street, Melbourne. 139 Moorabool Street, Geelong. 307 Sturt Street, Ballarat. 100 Clarence Street, SYDNEY. 26 Hunter Street, Newcastle. 161 Pirie Street, ADELAIDE. Hobart, Launceston and Burnie, TASMANIA.





# DISPOSAL



# SURPLUS



## Assorted Parcel

### USEFUL RADIO & TELEPHONE PARTS

Contains Earphone, Microphone, Relay, Full wave Copper oxide rectifier, Bundle Hook-up wire, resistors and condensers.

The lot for

# 10/-

POST FREE

### BATTERY OPERATED POWER SUPPLIES

#### 12 VOLT INPUT GENEMOTORS

Type No. 11 Low Power 230V Output

Type No. 11 High Power 320V Output

These units are in good condition and are supplied in metal cases.

Type No. 19 has 2 separate outputs, one 320V Plus 550V in metal case size. These units are ideal for conversion to A.C. D.C.

### ELECTRIC MOTORS

#### 2 VALVE AMPLIFIERS

In metal case size. Battery Operated.

CONTAINS—I VR35 Twin Triode. 2V Filament  
I VR21 Triode. 4 Transformers

BARGAIN 20/-

### POTENTIOMETERS

$\frac{1}{4}$  meg Carbon 20,000, wire wound, 2500 wire wound. These are new but have short shafts.

1/6 EACH

## NAVY

### POWER-OPERATED TELEPHONES

Comprise double Head-set and Breast Microphone. Two of these make ideal house to house phone. No Batteries Required.

EACH SET 25/-

### OPERATORS' SINGLE HEADPHONE WITH BREAST-MIKE

Standard type Carbon Mike and low resistance phone. Ideal for Switchboard.

PRICE 10/- EACH

### FIELD TELEPHONES TYPE "L"

With Generator and Handset—these units have been serviced and are tested before despatch.

PRICE 70/- EACH

BATTERIES 5/- PAIR

### EF50 VALVES 10/- ea.

6.3V. U.H.F., 6K7G. Guaranteed O.K.

### TRANSCIVER CHASSIS

Type No 22 covers 2-8 megs, with all parts less Valves and ANR Supply. These make good Communication Receivers.

PRICE £5 F.O.R.

# RADIO MART

439 PITT ST., SYDNEY, N.S.W.



# TRADE REVIEWS AND RELEASES

## SIMPLIFIES RECORD STORAGE


The problem of record storage is simplified by the use of the "Platterack", which can be used as a simple stand or built into a cupboard or radio cabinet.

**T**HE Platterack is essentially a simple wooden framework carrying steel wires which support the records on edge. The wires are covered with a braiding of silk and cotton to prevent scratching, while the discs rest on a silk cord.

The rack is 15 inches wide and provides space for 50 records, which may be a mixture of 10 inch or 12 inch discs. Each space is numbered and gummed labels are provided with each platterack together with a ruled sheet to facilitate indexing of discs and works.

It is interesting to note that the unit is now being incorporated by some manufacturers as a standard fitment in the more expensive radio-gramophone combinations.

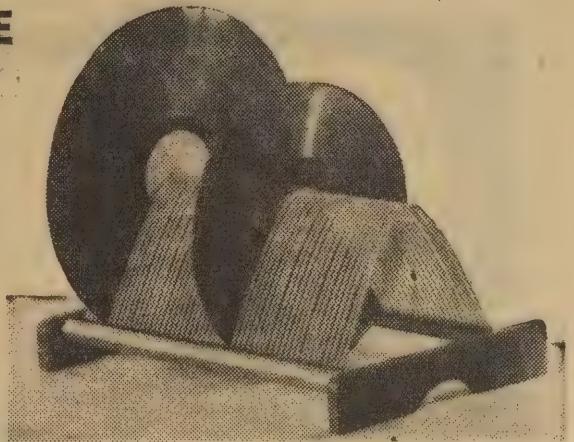The Platterack is being distributed by all music houses. The retail price is 25/- in capital cities, plus a small freight surcharge in country centres. Manufacturers are Fred A. Falk & Co., Post Office Box 28, GPO, Bondi, NSW.




## SMALL STRAIGHT LINE DIAL

**M**OST recent addition to the Eico range of tuning dials is the USL-37G. Employing cord drive, but without a flywheel, it has three alternative positions for the tuning spindle.

The model 37G is available with an edgelit scale for either broadcast or dual-wave coverage and using the "H" gang tuning condenser. Separate scales are provided for NSW-Qld.-Vic. or NSW-Vic.-Tas. or Vic.-SA-WA.

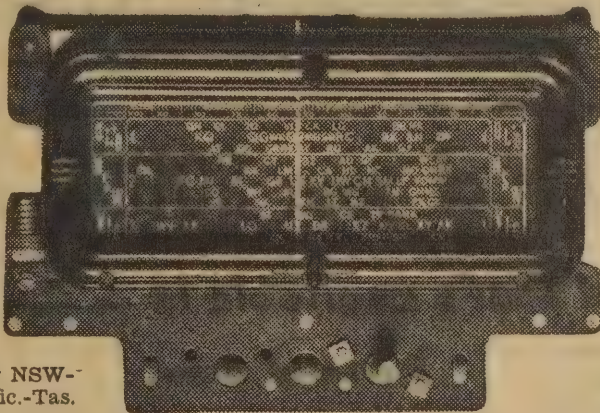For use in battery sets requiring no dial illumination, the dial can be supplied with a celluloid scale and is then



referred to as type USL-37. Overall dimensions are 7in. x 4 1/2 in., the escutcheon opening being 5in. x 1 1/2 in.

## NEW PHILIPS CONVERTER—ECH33

**T**HE present shortage of type ECH35 converters will be relieved to some extent by release of the new ECH33 triode-hexode.

These two types are identical in all respects except for heater current which, in the case of the ECH33, is 200 mA., and except in any possible AC-DC applications can be freely interchanged without alteration to circuit constants or socket connections.

The lower heater rating of the ECH33 is of distinct advantage for applications in vibrator operated receivers and also allows for the use of this type as a replacement for types EK2, EK2G and EK32 in AC-DC receivers using the 200 mA. valve series. In this case, of course, the question

of correct operating conditions, &c. should be taken into consideration.

Further enquiries as to prices, availability and technical information on this type should be referred to the Philips' Branch located in the capital city of each State.

Philips are also pleased to announce that a complete range of 150mA. Single Ended GT Valves for use in AC/DC receivers has now been added to the equipment types already available from stock. For the immediate present, supplies will be somewhat restricted, but commencing early October it is anticipated that sufficient supplies will be available to meet reasonable demands.

## MODULATION TRANSFORMER

**M**OST recent addition to the range of Ferguson products is this new M-25 modulation transformer, designed especially for use in amateur transmitters. With a nominal audio power rating of 25 watts, it is ideal for modulating a final R.F. amplifier stage having up to 50 watts input.


The primary loads are 6000 and 8000 ohms, centre-tapped, and the secondary impedance ratings are 5000, 7000



and 10,000 ohms. Maximum permissible secondary current is 100 millamps. Available through all distributors or from Ferguson's Radio, 12 McMahon-street, Willoughby, NSW.



# THE CD-31

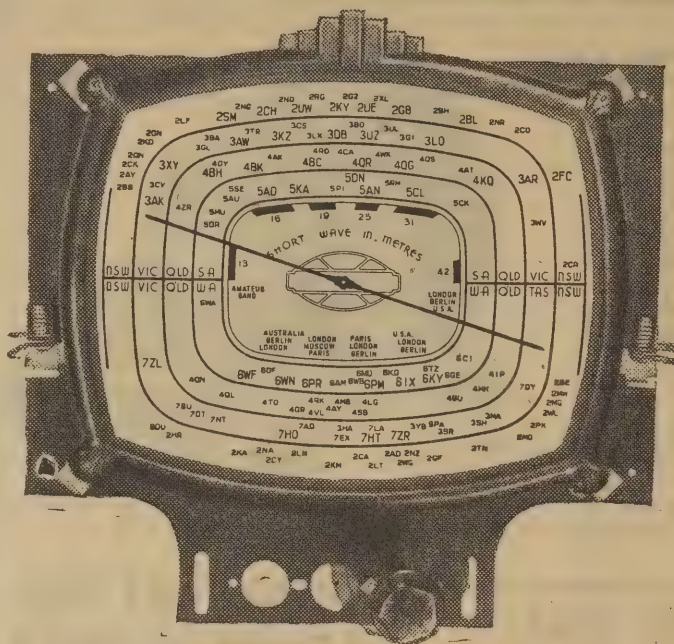

- Now available in B/C and D/W H, with new Edge-Lit Scale. Main local stations Green, S/W Amber, all other stations Cream.
- Three alternative positions are provided on dial plate for tuning control spindle.
- Dimensions: 10in. x 9in.

Escutcheon Opening:  $7\frac{3}{4}$ in. x  $6\frac{1}{4}$ in.

ON SALE AT ALL  
LEADING RADIO DISTRIBUTORS



**EFCO MANUFACTURING CO. PTY. LTD. ARNCLIFFE N.S.W.**

# Get the most out of your SOUND Hobby

***Use only the best that's available in***

## Microphones

## Pre-Amplifiers

## Amplifiers

## Consoles

## Spun Steel Flares

## Cellular Horns

## Exponential Horns

## Racks

## Speaker Boxes

## Speaker Baffles

## Line Transformers

## Microphone Transformers

**WRITE FOR OUR SPECIFICATIONS FOLDER.**

*for everything in Sound:—*

# STEANE'S SOUND SYSTEMS PTY. LTD.

60/80 MILLER STREET, MELBOURNE.

367 KENT STREET, SYDNEY.

FJ9149, FJ9140, FJ4543.


M3136, MA2588.




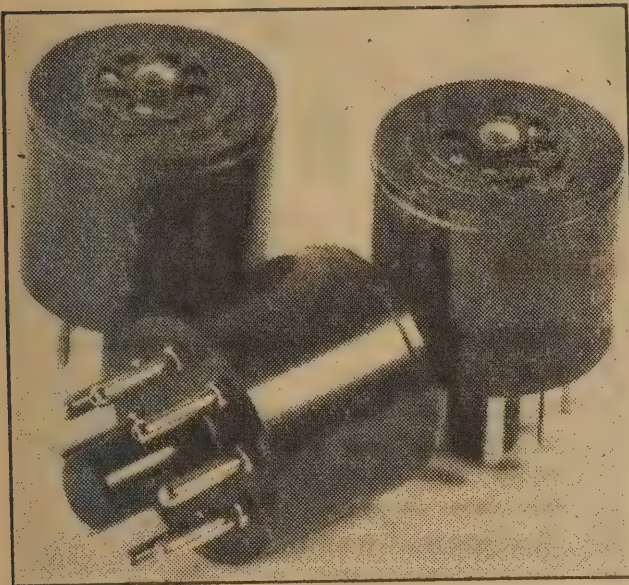
## ADAPTORS FOR BUTTON VALVES

Realising that few service valve testers could handle the new button-based valves, Philips Electrical Industries have made available a series of three adaptors which are designed to operate with most types of valve test equipment in use in Australia.



The adaptors are available from all Philips distributors and dealers for 4/- each.


**D**ESIGNATED as types TM1, TM2 and TM3, the adaptors simply plug into the normal octal test socket and take any one of the five locally made battery miniatures. Type TM1 tests the 3Q4, 3S4 and 1S4. Type TM2 is for the 1R5, 1T4 and 3V4, while type TM3 is for the 1S5 valve.

Philips are preparing a pamphlet explaining the use of the adaptors and giving test setting for all the better known valve testers.
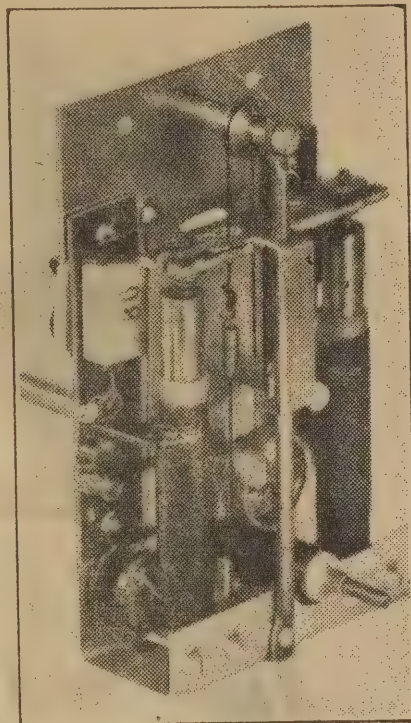
## KINGSLEY KFJB TUNING UNIT

**S**IMPLICITY is the keynote in the design of the new KFJB Kingsley Ferrotune unit. Operation of the tuning spindle varies the position of the iron slugs in the aerial and oscillator coils, which are mounted in the same plane, one on either side of the unit.

Cord drive is employed, and an important point is that the spindle turns



through only 180 degrees, making it possible for the unit to be used with a conventional dial movement and a suitably calibrated dial glass.

It is intended mainly for use with 3/4 or 4/5 valve receivers, employing a conventional converter valve, like the 6J8-G or ECH35. The KFJB tuning unit is included as part of a complete foundation kit, comprising chassis, tuning unit, IF transformers and dial movement.

## LOW LOSS COIL COMPONENTS



**I**LLUSTRATED on the left are some new RCS components which will be of special interest to amateurs. Four sizes of stand-off insulators are available, moulded in trolitul, and having an overall height of 1, 1½, 2 and 2½ inches. They can be fitted with a banana socket, or nut and bolt, and are normally supplied in clear trolitul. Colors can be supplied in quantity orders.

Trolitul tubing, fitted with banana plugs is available for use with the insulators, the overall length being 2½ inches and the diameter, either 1½ or 1 inch, as required.

To hold the wire secure, RCS have also released trolitul cement, which is normally supplied in 1oz. bottles.

## NEW LEAFLET DESCRIBES TRIMAX TRANSFORMERS

**F**OR many years Australian engineers in the communications field have been handicapped in the design of new equipment or the improvement of old, by lack of complete data on audio transformers.

With this in mind, Trimax Transformers have announced the issue of leaflet 47-1, which is fully descriptive of their standard range of low level high fidelity transformers. Due to labor and material shortages, not all types are in stock, but the objective is "Delivery off the Shelf."

Every unit is guaranteed to have a frequency variation not exceeding 1 db from 30 to 10,000 cycles when used under correct conditions. The transformers are designed for use

with secondary loaded. All types employ an astatic hum balancing structure with primary and secondary coils each in two separate sections.

Outer cases of mild steel or high conductivity non-ferrous metal give additional shielding. For particularly low-level operation, where freedom from hum pick-up is absolutely essential, special types are offered which, in addition to the above, incorporate triple shields of high permeability nickel iron alloy.

The transfer of longitudinal currents from primary to secondary is attenuated to a considerable degree by the provision of high-conductivity shields between windings.

"Trimax" transformers are obtainable through leading distributors in all States, but if difficulty is experienced, customers can contact the factory representatives, who can also give information on other associate lines:

Chandlers Pty Ltd., cnr. Charlotte & Albert-streets, Brisbane, Q'land.

Mr. L. B. Graham, C/- Radio Equipment Pty Ltd., 5 North York-street, Sydney, NSW.

Mr. C. N. Muller, Worraldo Buildings, Grenfell-street, Adelaide, SA.

Mr. R. D. Benjamin, 197 Murray-street, Perth, WA.

Messrs. W. & G. Genders Pty. Ltd., 53 Cameron-street, Launceston, Tas.  
69 Liverpool-street, Hobart, Tas.  
Mount-street, Burnie, Tas.



# Cathode Ray TUBES

## Visually Portray —

- Modulation pattern (depth) percentages.
- Wave-form analysis.
- Distortion in various equipments.
- D.C. Voltage and A.F. voltage measurements.
- Frequency response.
- Observation of transients.
- Phase relationships of A.C. voltages.
- Frequency calibration.
- Faults in circuit analysis.
- Measurement of very short time intervals.
- Receiver selectivity.
- Null or maximum readings.
- Balance of push-pull amplifiers.
- Output versus input measurements on amplifiers.

## PRICES OF CATHODE RAY TUBES

Type 5BP1 5" screen . . . £1/17/6  
 Type 4201 6" screen . . . £1/17/6  
 Type 4410 6" screen . . . £1/17/6  
 Type VCR516 12" screen . £1/10/-  
 (Plus 10% Sales Tax)

## SPECIAL PRICE REDUCTION

Type 913 1" screen . . . . 17/6  
 (Plus 2/- War Duty)



## Transmitting and Miscellaneous Valves are now available:—

TYPE	
2C40	6.3 v. Lighthouse triode
2C43	6.3 v. Lighthouse triode
2E24	6.3 v. V.H.F. beam power amplifier
2V3G	2.5 v. H.W. high vacuum rectifier
3B25	2.5 v. H.W. gas rectifier
3C33	12.6 v. Twin triode
559	6.3 v. U.H.F. Lighthouse triode
808	7.5 v. Transmitting triode

TYPE	
814	10 v. Transmitting beam power amplifier
841	7.5 v. Transmitting triode
845	10 v. Transmitting triode
865	7.5 v. Transmitting tetrode
902	2" Cathode ray tube
956	6.3 v. Acorn super-control R-F pentode
957	1.25V. Acorn general purpose triode


TYPE	
958A	1.25 v. Acorn general purpose triode
1614	6.3 v. Beam power amplifier
1622	6.3 v. Beam power amplifier
1654	1.4 v. H.W. High vacuum rectifier
1801	9" Cathode ray tube
8013A	2.5 v. H.W. High vacuum rectifier
8020	5 v. H.W. High vacuum rectifier
8025A	6.3 v. U.H.F. Triode

Further technical information available on request.


**AMALGAMATED WIRELESS VALVE COMPANY PTY. LTD.**  
 47 YORK STREET (BOX 2516, G.P.O.,) SYDNEY



# NEW STINSON HAS FOLDING WINGS

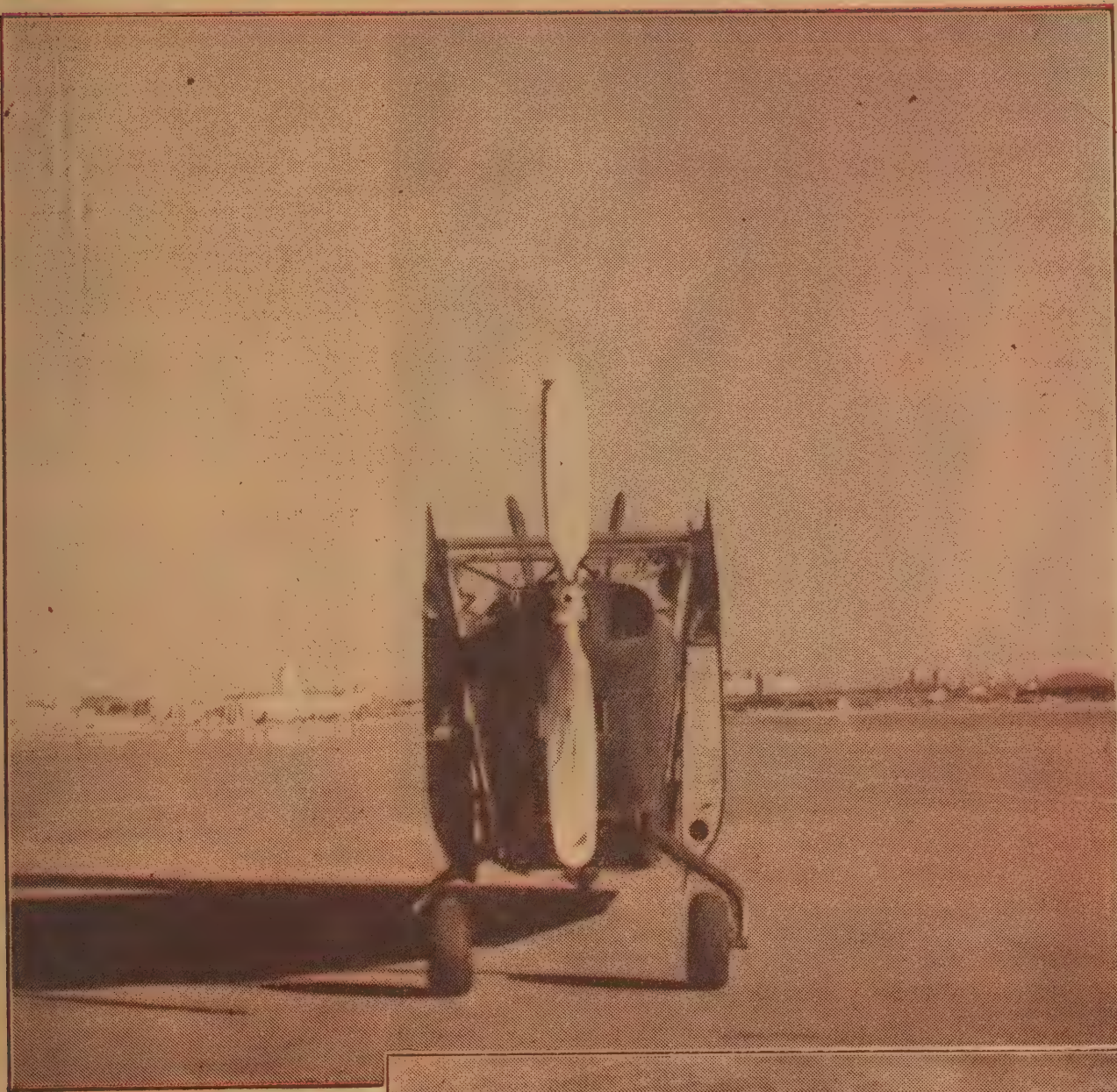


**T**HIS new versatile Stinson L-13 army liaison plane demonstrates folding-wing advantages which make it possible to be hauled or towed by a truck or car over rough terrain or down a highway. The landing gear is adjustable with a tread of 92.53 inches for take-offs and landings and 61.6 inches for ground towing. It is equipped with unusually large flaps which aid it in take-offs to attain the air after a 230ft. run and to land at 43.7 mph in 227ft. Top speed of 115 mph, cruising 92 mph, will carry six and has a range of 370 miles.

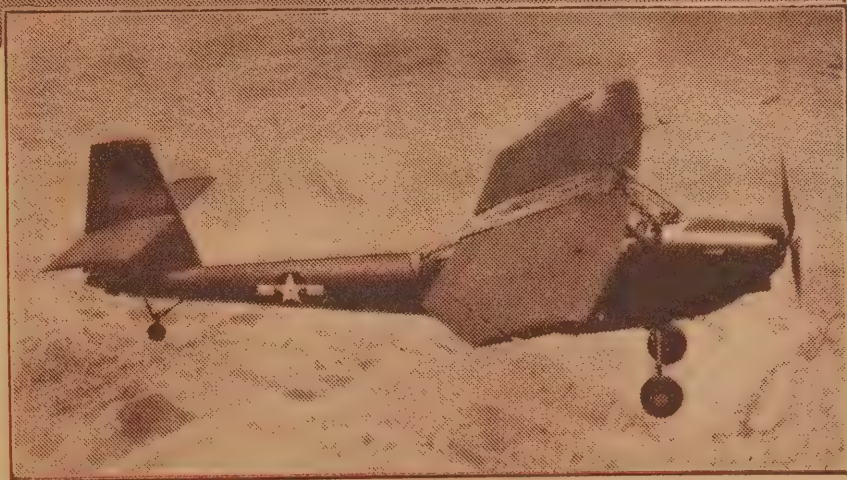



# STUDYING SECRETS OF SHOCK WAVE

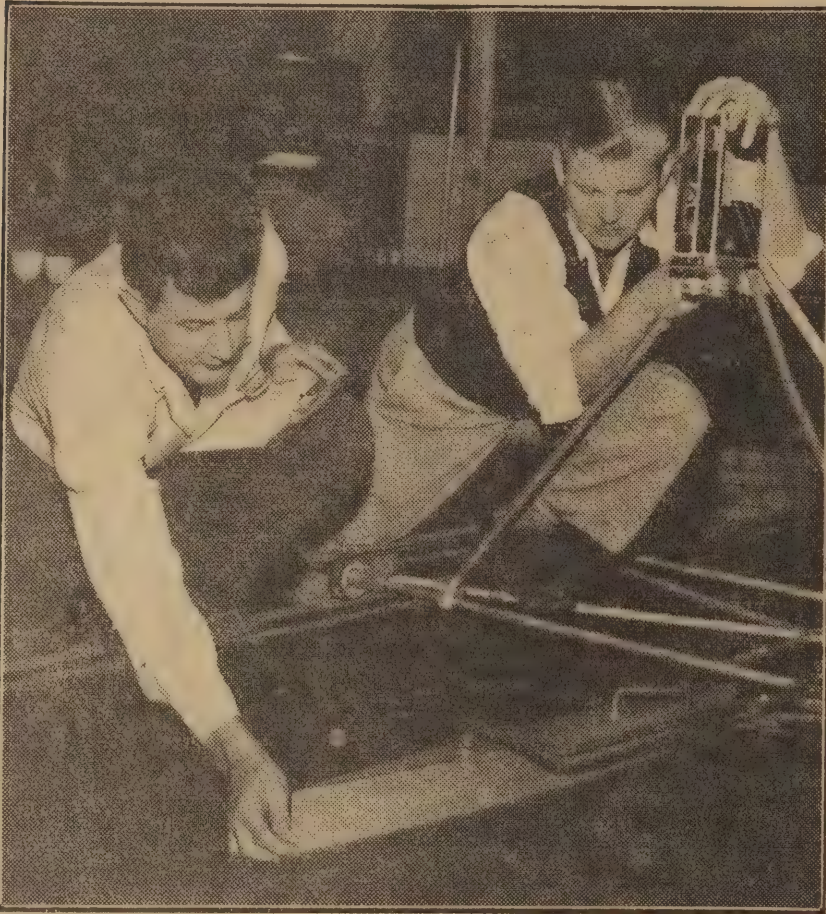

The special equipment used to simulate supersonic shock waves sent out by high speed aircraft and pilotless missiles by towing models in one-quarter inch of water.

A quickening finger stretches towards Nature's barrier that has for so long prevented humans from travelling faster than sound itself. Machines fly within the air minus human pilots, others spitting flames roar upwards to hundreds of miles where the air is thin.

IN the same breath science dallies with the thought of man-made satellites or space ships to revolve around the earth in orbits many thousands of miles up.

With this straining of man's environment has arrived a new vocabulary of expressions—guided missiles, pilotless aircraft, pulse, ram, turbo, prop-jet, meteorites, rocket projectiles, velocity of escape, &c.

We are beset by a jargon of Tiny Tims, Wac Corporals, Wizz Bangs, Buzz Bombs, Bazookas, Gapas, Holy Moseses, &c.

Millions of pounds and dollars have been invested in the competitive race toward higher speed to break down this barrier and reach aviation's long-sought goal—supersonic.

Britain attempted to take it in one jump and in doing so lost one of its foremost test pilots, Geoffrey De Havilland.

With this tragedy in their minds British experts changed the nature of their supersonic investigations to radio controlled planes without human pilots.

American engineers are approaching the barrier along conservative steps and their research programme is cautiously inching forward.

## TUNNEL TECHNIQUE

Lockheed Aircraft Corporation research scientists are using a method of studying flight characteristics of aircraft models in wind tunnels at any desired speed up to 850 miles an hour.

Several swept-back wing designs have been "flown" through the speed of sound in wind tunnel experiments, with lift, drag and stability being recorded progressively for the first time.

Since the wings may be used on future secret United States Army Air Force fighter planes, requirements of military security prevent any descrip-

tion of them beyond the statement that they embody the principles of "swept-back" construction.

Development of the Beman-Weaver "Bump"—a rounded, aluminium obstruction placed on the wind tunnel floor to produce a curved, speedier flow of air around the wing models—made the tests possible.

The "bump" was the discovery of Ward W. Beman, Lockheed's chief aeronautical research engineer, and John H. Weaver, Lockheed's wind-tunnel manager, and was made public only last month.

Supersonic wings have been designed in America and Britain and tested at speeds ranging from 2000 miles an hour, but data has never been obtained on them at and around the speed of sound due to extreme air turbulence which caused instruments to fluctuate.

## THE "BUMP"

When experiments proved the value of the wind tunnel "bump", Lockheed moved its research to the 700 mile an hour Co-operative Wind Tunnel at the California Institute of Technology in Pasadena, California.

First tests in the new 12,000 horsepower tunnel gave readings of 580 miles an hour, or a Mach Number of 1.1.

Tests made of conventional high speed wings, including models of wings now being flown on present high speed aircraft, have shown definitely that supersonic flight is impossible with these designs.

Solid brass models of conventional design broke up under the terrific shock waves of compressibility in the supersonic wind tunnel.

North American Aviation research engineers have contributed to the race with a simple technique of towing models through a water channel to simulate the supersonic shock created by high speed aeroplanes and guided missiles.

Speeds up to 7000 miles per hour can be simulated by towing models through a water channel filled to a depth of only one-quarter of an inch.

## TOWING METHOD

The engineers tow a model representing a supersonic wing, a ram jet or similar components through the channel by means of a wheeled stand.

The wheel holds both the model and the camera which records the shock wave patterns sent out by the models.

Wave patterns created by models being towed through the shallow channel are similar in shape to the shock waves sent out by a body flying through the air at supersonic speeds.

It is possible to simulate an aerofoil at a speed of 3000 miles an hour—



four times the speed of sound in the air.

The model is towed through the water channel at a velocity of 3.6 feet per second, which is four times the velocity of water waves in a channel one-quarter of an inch deep.

The velocity of sound is thus replaced by the velocity of the water waves.

Dr. William Bollay, head of the North American Aviation's aerophysics laboratory, points out that the water-channel system is less expensive than supersonic wind-tunnel tests, and also can be used to simulate accelerated motions.

The disadvantage, he said, is that the resulting data are not accurate as wind-tunnel tests, but are primarily useful for qualitative studies of supersonic flow.

The technique of using the analogy of water waves and shock waves in the air was first proposed in America by Theodore von Karman, of the California Institute of Technology, for the reverse problem of studying the optimum design of water channels for the Los Angeles County Flood Control District from the well-known theories of supersonic flow of air.

## ROCKET TRAVEL

North American Aviation's aerodynamicists are now working in the opposite direction — going from the experimental water channel to deduce the supersonic flow air.

Speaking before the National Aviation meeting of the American Society of Mechanical Engineers, Mr. E. H. Heinemann, chief engineer of the El Segundo plant of Douglas Aircraft Company, predicted that although rocket missiles may be fired to any point on the earth within the near future, everyday rocket travel appears to be remote.

In a paper entitled "High-speed Aircraft Development," the engineer said that from data presented and recent news, one might be led to the conclusion that rockets will be the next mode of high-speed travel.

"The development of rockets as uninhabited missiles capable of being fired to any point on the face of the earth appears to be within the realm of possibility in the relatively near future," Heinemann declared.


"The greatest unsolved problems in this field are generally considered to be those of obtaining satisfactory guidance and control.

"Since rockets operate most efficiently above the earth's atmosphere, the problem of using them for human transportation is somewhat more complicated, due to the necessity of re-entering the atmosphere at several thousand miles per hour and landing safely.


*The Keystone or Treaty oak at Jacksonville, Fla., is so large that 4000 persons can stand in its shade at noon, it is estimated.*

★ ★ ★

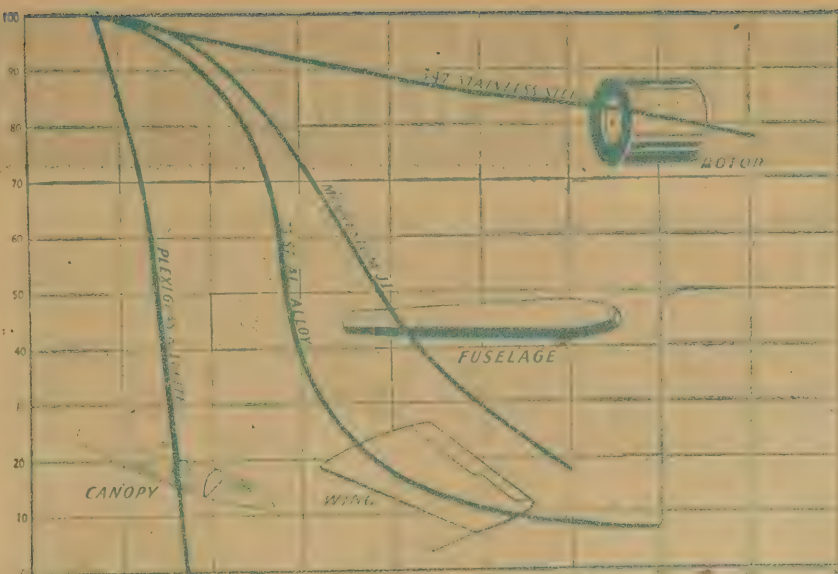
New fountain pen ink writes dry by vertical penetration into the paper and not by evaporation or drying of the solvent, the makers claim.



Speed does things to the materials of which aeroplanes are built. The figures on the left illustrate the percentage of strength retained by the different materials as speed—and with it temperature (the figures along the bottom) increase. Plastics are the first to go, stainless steel the last. Components of the Douglas Skystreak made from the materials shown demonstrate how different parts of the plane will stand up.

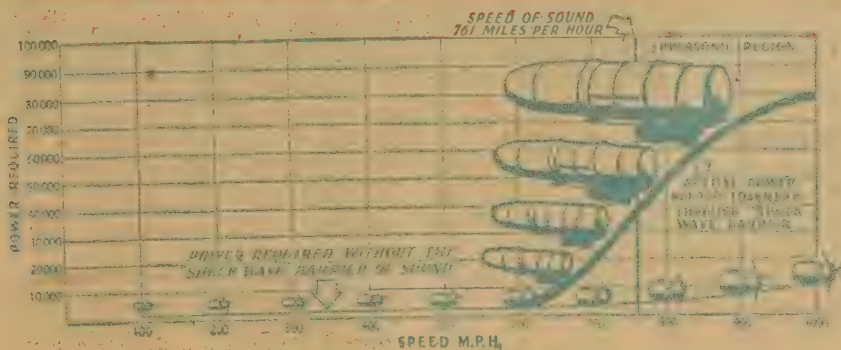

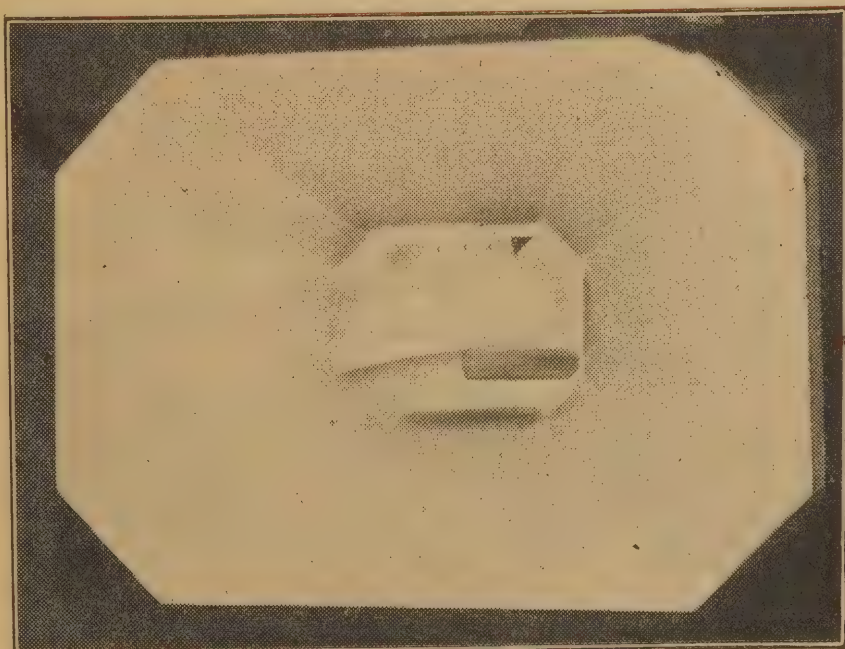The above chart shows what happens to power requirements approaching and crossing the sound barrier. The red line and huge jet engines illustrate the sudden surge of 80,000 horse-power needed to break through the barrier and beyond. Smaller propeller engines illustrate the normal rise in needed power if the shock wave barrier had not been there.



Model of the wind tunnel using the "bump."



# PICTURE NEWS OF THE WORLD'S SKYWAYS

## New British Engine

A 160-HORSEPOWER, flat six-cylinder engine, especially designed for installations submerged completely in the wing has been designed by Roy Fedden, Ltd., a British firm, and will go into production shortly.

Conceived with light plane pusher types in mind, where the propeller would be driven by an extension shaft, the engine is 14 inches high, 31in. wide and 34in. long.

The manufacturer is a newcomer to the British aircraft industry, being founded last year by Sir Roy Fedden, wartime principal technical adviser to the Minister of Aircraft Production, and president of the Royal Aeronautical Society.

An aircooled, horizontally-opposed four-cycle engine, the "Fedden Flat" has a two-piece aluminium crankcase with cylinders of low expansion silicon alloy and sleeves of nickel manganese chromium alloy high-expansion steel. Fuel system employs direct injection, rather than carburetion.

## Brabazon Contract

ARMSTRONG-WHITWORTH AIRCRAFT CO., LTD., has been awarded a contract to build the Brabazon II British transport.

It will be a low-wing monoplane with tricycle landing-gear, designed to carry 24 passengers on a long haul or 40 on short hops.

It will be powered by four Mamba gas-turbine prop jets, and have a range of 1000 miles at better than 300 mph, with a gross weight of 35,000lb.

Fuselage interior is to be pressurised and air-conditioned.

## A.N.A. Figures

STATISTICS on freight figures reached by Australian National Airways for the financial year ended June 30, 1947, totalled 18,645,518 lb.

For the six months ended December 31, 1946, ANA carried 8,891,240 lb., and for the six months ended June 30, 1947, 9,763,278 lb.

Compared with freight traffic of 7,705,221 lb. for the financial year 1945-1946, the 1946-1947 figures showed an approximate increase of 14 per cent.

These figures are equivalent to 8328 long tons and equals an average monthly turnover of 1,554,543 lb. gross weight per month.

The highest monthly poundage for the year was handled in the month of May, when Australian National Airways freighted just over 2,000,000 lb. gross weight for the month.

## British Jets Lead

RAF Group-Captain Frank Whittle, reporting in Britain on his American lecture tour, said American jet-engines are currently about two years behind British models in basic developments, but overhaul periods were amazingly lower (50 hours for American jets, compared to 270 for British engines).

The RAF will scrap all reciprocating-engined fighters in its operational squadrons as soon as sufficient jet-powered fighters are available for replacements.

## Atom Power For Planes

WITH a primary contract going to the Fairchild Engine and Air-

plane Company, the United States Army Air Force has undertaken a research programme to ascertain how atomic energy can be harnessed as the propulsive power for future military aircraft.

While it is technically feasible now to use atomic power for aircraft propulsion, the airplane would have to be so big—three or four times heavier than the 278,000 pounds B-36—that such a development will not occur within 10 years, Dr. Luis Alvarez, Robert J. Collier Trophy winner, recently told the Aero Club of Washington, USA.

Major-General Curtis Le May is in charge of the USAAF's research programme.

Although Major-General Le May has said nothing beyond the fact that research will be conducted at Farmingdale, NY, he has inferred that preliminary results prove that atomic air power is "not impracticable" even though the engineers are still seeking a final method for utilisation of nuclear energy in aircraft.

## U.S. Fighters

THE United States Army Air Force is thinking in terms of three types of future fighter planes: A penetration fighter to accompany long-range atom bombers; an all-weather, for use at night and under conditions where visual contact is impossible; and a short-range rocket-powered interceptor.

The bulk of the new order is for an undisclosed additional number of Republic's new P34 Thunderjet's, first American jet-fighter plane to exceed 600 mph.


Republic Aviation Corporation has received new military aircraft orders totalling more than 25,000,000 dollars, according to an announcement by the United States Army Air Force, Air Material Command.

At left: Latest photograph of the world's largest land-based aircraft, the six-engine XC-99 cargo and troop transport being built by Consolidated Vultee Aircraft Corporation for the United States Army Air Force.

The giant double-decked plane, capable of carrying 400 fully-equipped troops or 100,000 pounds of cargo, is now nearing completion at San Diego, California.

The AAF has revealed that the XC-99 will have a maximum range with reduced loads of more than 8000 miles. Flights of this distance will call for a five-man crew and an equal number of relief crew members.

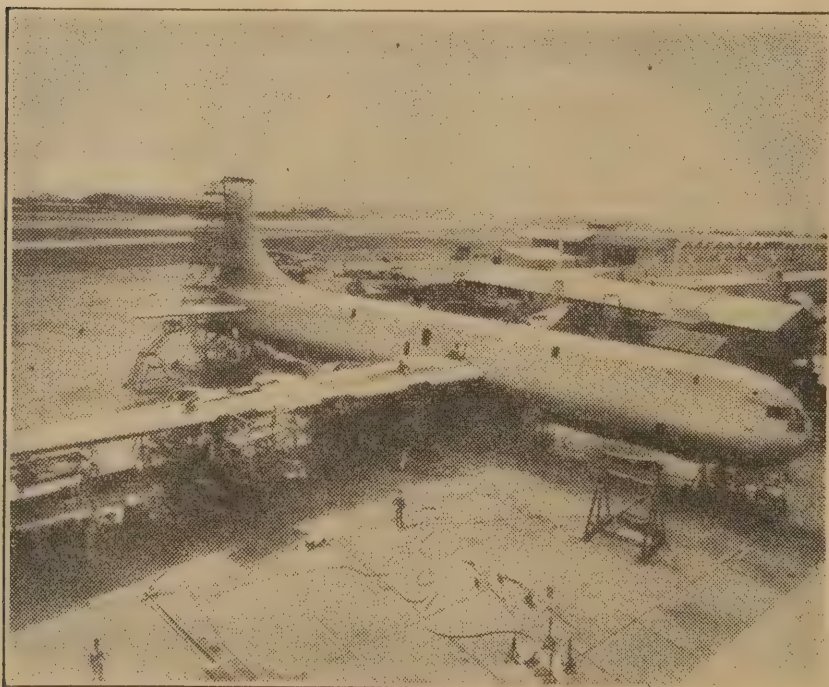The plane, transport version of the Corair B-36 bomber, is 182½ feet long, 57½ feet high and has a 230-foot wingspan.





## Allison Jet Engine

**T**HE Lockheed P-8A which held the world's speed record for 623.8 mph was powered by America's highest powered jet engine with a top rating of more than 4600 pounds.

Designated the Allison Model 400, this jet engine is of the same general type as the production AAF J33-21 engine, which powers production models of the P-80 Shooting Star.

Late this year, Allison will put this model in production for a new production series of the Lockheed P-80.

Performance data on the new engine, all of which have been exceeded in test stand operations are:

Take-off power (dry), 4600 pounds static thrust.

Military power, 4600 pounds static thrust.

Maximum continuous power, 3600 pounds static thrust.

Military power S.F.C., 1.13 pounds/pound thrust/hour.

Maximum continuous power, S.F.C. 1.12 pounds/pound thrust/hour.

Cruise S.F.C., 1.14 pounds/pound thrust/hour.

Engine weight, 1735 pounds.

## RR Made In China

**ROLLS-ROYCE**, Ltd., has concluded an agreement with the Chinese Government under which Rolls' jet engines will be manufactured in China.

Chinese engineers are supervising the construction of a plant in China.

This is the second notable foreign licensing agreement in which Rolls-Royce has figured recently, having previously licensed a private US firm, Taylor Turbines.

## Underwater Aircraft

**T**HE United States Navy conservatives are questioning feasibility of a submersible plane idea now being tested in model tanks by Navy technicians.

The project requires a plane built strongly enough, so it can land on sea, submerge to escape pursuit or ambush some surface craft, and then take off to continue flight.

The "underwater aircraft" would be powered with jet engines in the air, and air vents would close automatically when the plane struck the water.

An auxiliary power system would be used underwater.

## Packard Turbo-jets

**D**EVELOPMENT of a new type of turbo jet engine which has operated successfully on a test stand, has been announced by the Packard Motor Co. of America.


President of the company, Mr. George T. Christopher, said the engine will remain on the restricted list until it goes into production later this year.

Packard is engaged on the project at Toledo, Ohio, under an agreement with the Air Material Command of USAAF.

At Toledo Packard has built a new \$500,000-dollar turbo jet laboratory which is scheduled for completion this month.

It will include facilities for testing jet engines, and parts, in temperatures as low as 70 degrees below zero, and at altitudes up to 42,000 feet.

## LATEST U.S. JET FIGHTER PLANE

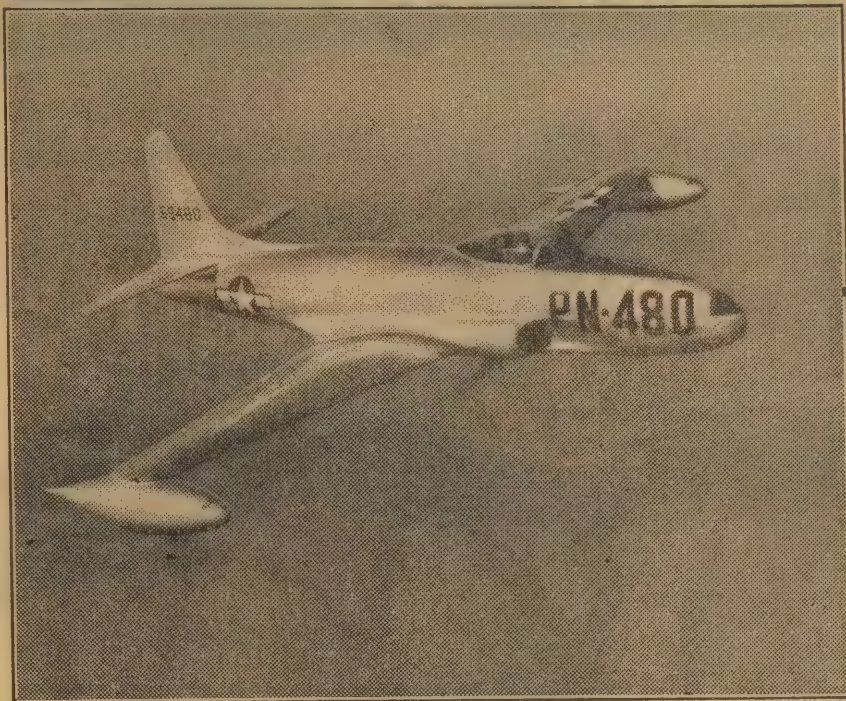

This is the first photograph of the United States Army's new Lockheed P-80B "Shooting Star" jet propelled fighter now in production at the Lockheed Aircraft Corp. factory in Burbank, California. There are many improvements on the P-80A—note the extended dive flaps below the plane to slow it down to the speed of the accompanying camera plane. Faster firing guns have been installed and the aircraft has been given more resistance to battle damage. The airplane is delivered with an unpainted, shiny aluminium surface, since earlier P-80's which flew into rainstorms at high speed emerged with paint chipped off. A pilot ejection seat has been added and radio masts and antenna wires have been enclosed in the pilot's canopy for the first time on any aircraft. The P-80B is believed to have the greatest fire-power of any jet fighter in the world.

## Fate Of Wright's Plane New Bomber

**T**HE first powerplane to fly, the historic biplane which Orville Wright lifted from the sands of Kitty Hawk, nearly 44 years ago, may be expected to remain in England indefinitely, until a suitable place is designated for it in America.

Sources close to Orville Wright, recently reported that the 75-year-old co-inventor of the first successful aeroplane, contrary to recent and recurring reports, has made no definite plans for the plane's early return to America.

He intends to take it back—but not until he is satisfied with the arrangements made for its exhibition.

In 1942, the Smithsonian Institution promised that if the plane were brought back it would have "the place of highest honor which is its due."

Presumably this would be in the New National Air Museum recently authorised by Congress.

## Swedish Sreed

**SVENSKA** Aeroplan A.B., Swedish aircraft manufacturers, are working on a new fighter type designed to outfly the British Gloster Meteor.

Prototype is expected to fly by the end of this year.

This new model known as the SAAB R1001 will have sweptback wings and a planned top speed in excess of 650 mph.

**T**HE US Navy's new four-engine patrol bomber, the Martin XP-4M-1, made its first test flight recently.

Principal feature of the new plane is its top speed of 398 mph, and its unique engine installations, which have a Pratt and Whitney R-4360-4 reciprocating engine and a General Electric I-40 jet in a single nacelle.

Service ceiling is 16,400ft, and gross weight 81,887lb.

## Fast Haul

**A** UNITED STATES Army Douglas XA-26F, powered by a combination of two Pratt and Whitney Double Wasp "C" engines and one General Electric 1-16 jet engine, set a new international speed record recently of 413 miles an hour over a 1000 kilometre course with a 1000 kilometre payload.


The plane, piloted by Lieutenant-Colonel T. P. Gerrity, flew the round trip from Wright Field and St. Louis in one hour, thirty seconds.

The previous best world's time for the distance with a similar pay-load was 369 miles an hour, established by a US Army bomber in May, 1945.

Otters sometimes take over burrows dug by muskrats or beavers, some naturalists claim.



# DOUGLAS SKY-STREAK BREAKS RECORD

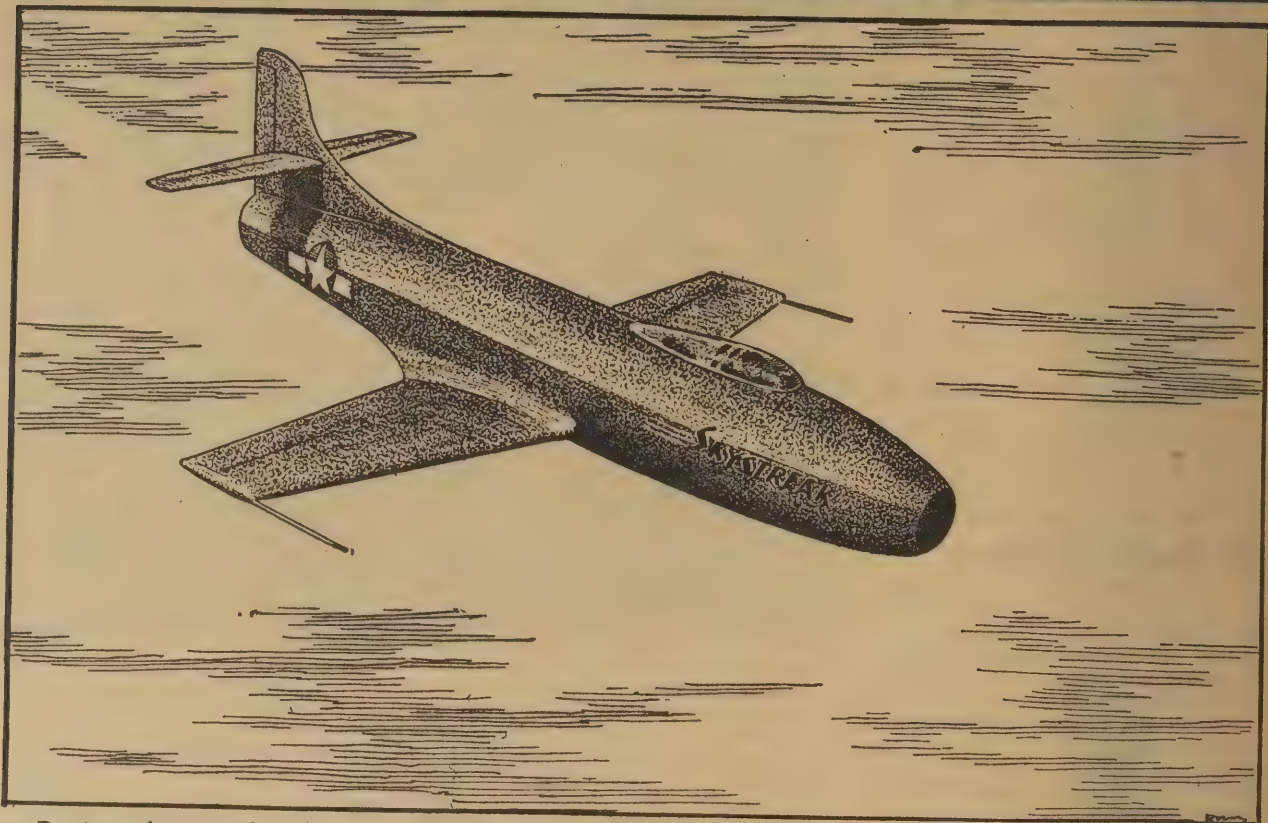

Designed to probe the secrets of the trans-sonic speed range, the US Navy's experimental single-seat "Skystreak" has set up a new world speed record of 650.6 miles an hour.

**T**HIS turbo-jet, piloted by Marine Major Marion Carl, covered four runs at an average of 650.6 miles an hour. A week earlier the same plane, piloted by Commander Turner Caldwell, had set up a record when it averaged 640 miles an hour. Its fastest run on that occasion was 653.4 miles an hour.

Designated the D-558, the Skystreak is a small, finely-streamlined low-wing monoplane, with clipped wings. In its record-breaking runs it was fitted up as a "flying test-tube," carrying 500lb. of recording instruments.

The air intake for the jet is in the nose, and the air is ducted to the turbine located behind the pilot's cabin.

The tailplane is placed almost halfway up the tail fin.

In its record runs the Skystreak approached the speed of sound. At sea level the speed at which sound travels through the air is 765 miles an hour; at higher altitudes, because of lower temperature and air densities, the speed is below 700 miles an hour.

Design of aircraft parts for planes that are to reach such speeds must be adapted to meet the special conditions. The wings of planes designed for trans-sonic and supersonic (faster-than-sound) ranges must be swept back slightly and are thinner in sec-

tion than those of normal speed planes.

This is because in flight at or near the speed of sound, air fails to flow over the wing in the way it does at subsonic speeds. Instead, the air builds up into a phenomenon known as "compressibility," which is a wave of air that is as "solid" as a brick wall.

This "shock wave" spoils the lift of the wing, resulting in loss of control. It can start up a battering process that may actually tear the aircraft wing to pieces.

Jet propulsion has been instrumental in bringing aircraft speed ranges into the realm of "trans-sonic" and "supersonic" speeds.

Spectacular advances have come since the perfection of jet propulsion,

first announced in 1944. "Jets" have been responsible for raising flying speeds beyond 500 miles an hour—which is about the limit for propeller-driven planes.

The Skystreak has added to the achievements of jet propulsion and taken it one step further in fulfilling the hopes held out for it as a propulsion system. Further experiments being undertaken with the Skystreak will open the way for ultimate in speed by jet propulsion, after which rocket power will take over.

It is believed that jets will take speed range beyond 700 miles an hour, after which rocket craft will carry on to limits that appear to depend only on the strength and durability of the aircraft and the power of the human being to stand the hazardous conditions.

## The Australian Short-Wave Handbook


**O**UR new handbook—actually the 1947 edition of our old Call-Sign Book—will be on sale some time during October.

It will be something new for Australia. In addition to printing Australian and New Zealand amateur station call signs, all the short-wave stations of the world will be listed. More than half the pages will be devoted to technical and constructional articles describing short-wave receivers, transmitters, modulators, &c. including circuits for UHF work and a slashing new short-wave set.

There will be about 100 pages, and the price will be only 2/-—available everywhere or post free from our office, 60-70 Elizabeth-street, Sydney.



# MAKING A THREE-WHEELED SCOOTER

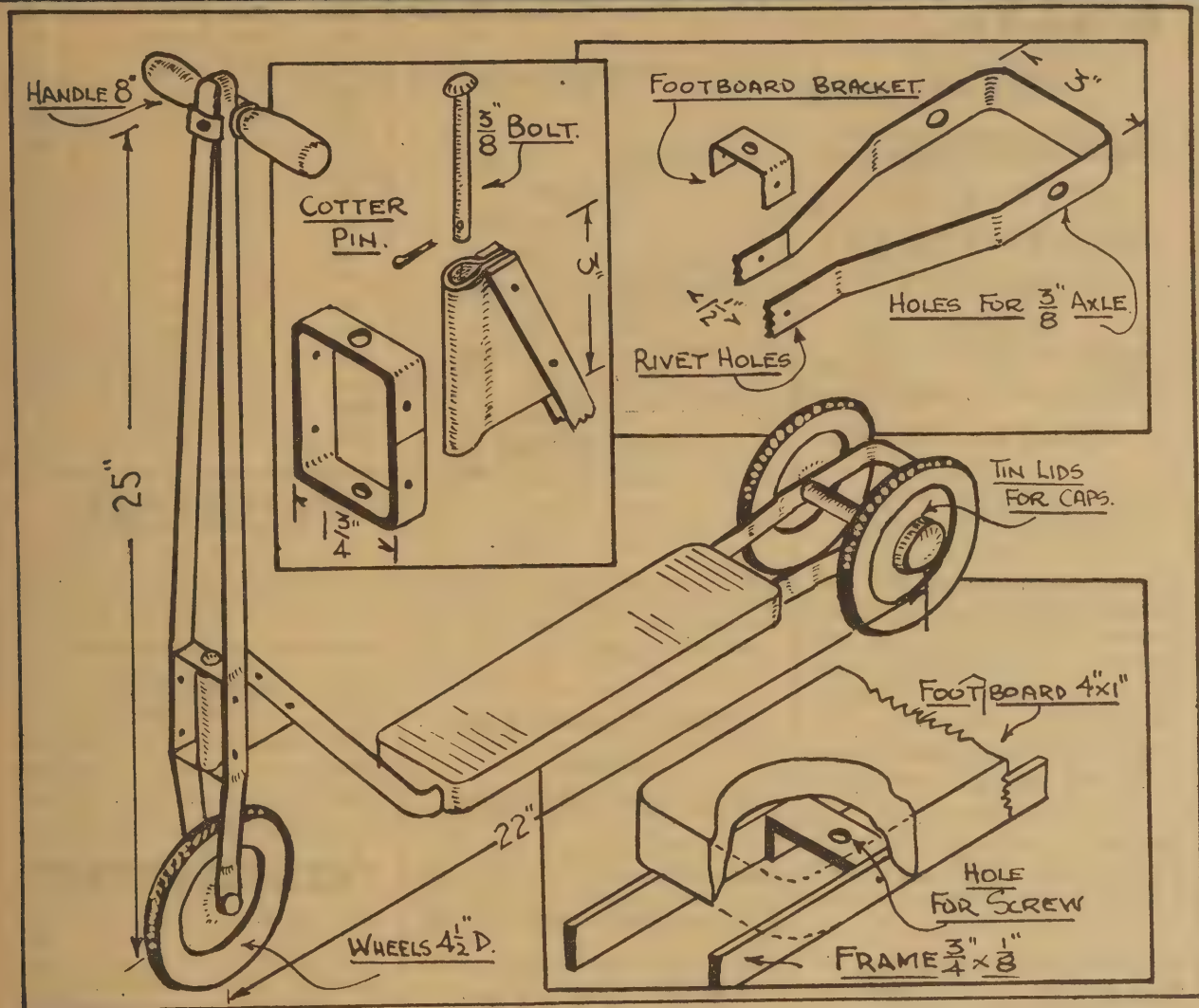

A scooter rather unconventional in design, that is one with three wheels instead of the usual two, is much easier for the small child to handle whilst still in the stage of learning to use such simple aids to walking. The ease with which it is balanced coupled with its lightness and strength will make it a delightful acquisition to the small boy's playthings.

AS can be seen from the illustration, the design is straightforward, the chief parts being made from strips of  $\frac{3}{16}$  in. x 1-8 in. flat mild steel. These are readily bent to shape and when the various pieces are riveted together they make a very strong construction.

It does not matter much which piece of the scooter is made first, but suppose we start with the front forks. For these, a strip of steel is needed the approximate length being 52 in. Measure to the centre from end to end, and mark the position with a piece of chalk. Then bend the strip double across a length of small-diameter pipe. This will make the top of the forks nicely rounded.

Afterwards the two arms can be cut off to equal length. Mark out all of the holes needed here and drill them through the two arms, thus

making sure that the holes will be opposite each other. Those for the front axle are  $\frac{1}{2}$  in from the ends, whilst those to hold the hinge bracket are  $\frac{1}{2}$  in apart and  $\frac{1}{2}$  in from the centres of the axle holes.

After the holes are drilled, the forks can be bent to a suitable shape, an indication of which is shown in the sketch, and then rivet the hinge bracket in place. This bracket is made from a piece of strip steel and is bent

to the shape of a rectangle,  $3\frac{1}{2}$  in x  $1\frac{1}{2}$  in, with the join coming in the middle of one of the long sides. Along the short sides centre punch the positions for the hinge-bolt holes, and drill them 3-8 in. Then mark out the position of one side rivet hole, drill it and rivet the bracket in place. The remaining three holes can now be drilled quickly and accurately with the assurance that the rivets will fit without any trouble.

The next large part needed is the bottom frame, and for this 50 in of the material is required. Measure 25 in from one end to find the middle, and come  $\frac{1}{2}$  in on either side of this, thus marking the position of the two 90 degree bends for the back. As before, form the frame around a piece of pipe to make nicely-rounded curves, then cut the arms to length, if they are unequal. Now a strong vice and

by T. E.  
Le Sueur



# F.N.

## RADIO and ELECTRONIC Co.

(For FM and AM)

265 MILITARY RD.,  
CREMORNE,  
N.S.W.

XM7063

XM7063

### 6" ENGLISH P.M. SPEAKERS.

Less Transformer. 42/6.

As above in attractive Bakelite case with  
50 ohm Trans. & vol. control 58/-

MIDGET. 2/GANG Condensers -- 19/3  
MIDGET. 5/GANG Condensers .. 12/6  
MIDGET. Reinartz Coils .. . 6/3  
MIDGET. Spk. Trans. 5000-7000 .. 12/4  
MIDGET. Valve Sockets .. . 8d. & 1/-  
MINIMAX 67½. Batt's .. . 17/1

PLEASE ADD EXCHANGE,  
FREIGHT.

SWITCH UNITS, contains Multi-contact  
Rotary SWS, 1w. 2w Resistors etc. 11/6 ea.

STEEL CASES, contain Audio Trans., (3)  
Phone Jacks etc. -- -- -- 4/6 each.

A LARGE NUMBER of 18v and  
24v GENEMOTORS VARIOUS  
OUTPUTS

PRICE ON APPLICATION.

## "RELAYS"

"LEACH," 24v D.C. D/Pole Relays.  
(Suitable change over aerial etc.).  
Works in Exciter H/T Supply 15/- each.

P.M.G. TYPE RELAY 2000 ohm 2 pole S/T.  
12/- EACH.

### LIGHTWEIGHT CERAMIC SPREADERS

6" x ½" 1/3 each 12/- Doz.

### DURALIUM ANGLE STRIP

4" x ½" x ½" (12G)

(Suitable Construction Racks etc.).  
3/- per length.

### AUDIO OUTPUT TRANSFORMERS

To clear 3/- each.

4 Valve T.R.F. Receiver, uses 2 volt. L/T,  
100v H/T, Suitable country use. Plug  
in coils, 200 kc to 13.5 Mcs.

WHILE THEY LAST .. . £13/0/0

### QUANTITY HEAVY STEEL RACKS.

PRICES ON APPLICATION.

Steel Case containing (4) 2mfd 600v  
Conds., (1) Audio Trans. Carbon and  
W.W. Pots, Resistors, Cond's etc. 16/- ea.

## "TX. XTALS"

3995, 4450, 4550, 4970, 5300, 5570, 5660,  
5910, 6370, 6450, 6500, 6670, 6940, 7270,  
8790, 9065, 9675, kc's .. . 5/- each.  
9400, 9660 kc's -- -- -- 12/6 each.  
20.1 Mcs to 27.4 Mcs .. . 3/- each

## "VALVES"

### New Cartoned

IT4	22/4	EF50	9/-
IR5	22/10	6AC7	21/-
IS5	21/10	6AG5	20/-
3S4	22/10	807	14/6
IS4	22/10	811	30/-
1L4	22/4	813	48/6
3A4	22/10	837	22/6
954	15/-	866	28/6
955	15/-	12A6	12/6
958	20/-	12K8	12/6
6C4	16/-	12SA7	12/6
6J6	16/-	12SG7	12/6
9001	15/-	12SH7	12/6
9002	15/-	12SK7	12/6
9003	15/-	12SQ7	12/6
9004	15/-	12SR7	12/6
9006	10/-	1625	25/-

## "RESISTORS"

660 ohm 120w, 1000 ohm 120w,  
(For AC-DC Filament Dropping etc.)  
7/6 each.

## "POTS"

20,000 Midget Pot .. . 2/- each  
25,000 Pots .. . 2/- each  
5 Meg. Pots .. . 2/- each

## "CONDENSERS"

1mfd. 250 DCW .. . 6d.  
3mfd. 250 DCW .. . 8d.  
1mfd. 500 DCW .. . 8d.  
25mfd 25v. (Can) .. . 1/-  
2 x 1mfd. 600v. .. . 2/3  
.1 4000v. .. . 3/3

WE CARRY A LARGE ASSORT-  
MENT OF MINIATURE AND  
STANDARD PARTS ETC.

WE CARRY AN EXTENSIVE STOCK OF ALL RADIO COMPONENTS.

## SPECIAL ATTENTION COUNTRY AND INTERSTATE MAIL ORDERS

(PLEASE ADD FREIGHT AND EXCHANGE WITH ORDERS)

We manufacture and repair all types radio and  
electronic equipment, ie. P. A. Systems, Ampli-  
fiers, Communication Receivers, Inter-Office  
Systems, Transmitters etc. All work under the  
personal supervision of Mr. Alan H. Nicholls  
VK2NI (AMIRE), who will be pleased to help  
you with your problems. Write direct to . . . .

# F. N. RADIO

(Ferguson & Nicholls)

Radio And Electronic Engineers,

265 Military Road, Cremorne, N.S.W.  
XM7063



some patience is required for the neck of the frame must be bent up at an angle to take the hinge flap. Hold one arm of the frame flat in the jaws of the vice, say, about 8in from the end, and very carefully exert pressure until it bends. (A piece of pipe slipped over the end will give extra leverage.) Watch the bend carefully, and if it tends to buckle, take it from the vice and flatten it out with a hammer. Continue these steps until the neck reaches up to the hinge bracket, which has previously been riveted in place in the forks. The exact angle for the bend can be tested on the job itself. When one arm is correct, bend the other to the same angle. Drill two holes in the neck, 1½in apart from the rivets.

## HINGE FLAP

The hinge flap requires a piece of heavy sheet steel, 6in x 3in. Fold it in two around a 3-8in bolt, then squeeze it together in the vice to form the shape desired. Hold the flap temporarily in place in the frame, and, after making sure that it is set correctly, mark out and drill the holes and rivet this piece in place. Any excess metal left protruding can now be cut off with a hacksaw, and the rough edges smoothed up with a file. The arms along the centre of the frame must now be made parallel, to take the wooden footboard. The rear end of the frame is bent to a shape approximating that in the plan, whilst the front being riveted together tapers up smoothly. Use a vice and hammer for this.

Two small footboard brackets are also needed and these are made from pieces of strip steel, 3in long. Drill three holes in each of these, then bend them into a U-shape, so that the distance between the two bends is 1½in. Drill holes in the frame and rivet the brackets in place.

The footboard is a piece of wood 4in x 1in x 13in, and is screwed in place from underneath by two screws.

Before assembling, plane up the edges and carefully round the corners. The 8in handle can be turned on a lathe or worked by hand to the shape desired. It is held in place by means of a small bolt and clip. If a groove is filed in the back edge of the forks, the handle will stop rigidly in place.

## WHEELS

Wheels can be bought, but if made the cost will be much less. Three of these wheels, 4½in in diameter, are needed, and when turning them on the lathe, recess a groove around the rim to take a ½in rubber tyre. The centre bearing will have to be reinforced and the best way to do this is to drill the hole oversize, say, about ½in, and bush it with a piece of 3-8in inside diameter brass tube. The ends of the tube can be burred over to keep it in place. After the wheels are tyred, they can be adjusted on the scooter.

The front wheel is on a short 3-8in axle, the ends of which come through holes previously drilled in the ends of the forks and are then riveted over. Washers may be necessary to take up any slack, and don't forget to put these on before fastening the axle in place. The rear axle of 3-8in rod is somewhat longer, but it also, after passing through the holes drilled in the frame and the wheels, has the ends riveted over (or, if desired, small holes may be drilled and split-pins used instead).

## AXLE ENDS

It is advisable to cover the axle-ends on the rear wheels with a protecting cap of some sort. Two powder-tin lids or similar will be useful here. Drill two holes through the lids to take small screws and fasten them securely in place. File off any rough edges on the screws. A 3-8in bolt is dropped through the hinge and fixed in place, with a nut or a cotter-pin to hold the frame and the forks together. After painting and oiling, the scooter is ready for use.

# The Australian Short-Wave Handbook

OUR new handbook—actually the 1947 edition of our old Call-Sign Book—will be on sale some time during October.

It will be something new for Australia. In addition to printing Australian and New Zealand amateur station call signs, all the short-wave stations of the world will be listed. More than half the pages will be devoted to technical and constructional articles describing short-wave receivers, transmitters, modulators, &c. including circuits for UHF work and a slashing new short-wave set.

## DONKEY ENGINES

**STEAM DONKEY ENGINES.** Drive your Builder Construction. Set Models with this Powerful Engine, stands 9 inches high, with safety valve and whistle. In box with instructions.

Price 26/9 each.  
Post 1/3 N.S.W.

## AIR RIFLE

Powerful and Reliable.

**THE NEW AIR RIFLE.** Attractively made, 32 inch long, with 28 Day Guarantee. Fires "B.B." or slugs. Packet of pellets



available for purchase with each gun. Spare parts available. Price 35/- ea. Pellets, 11½d packet. Post 1/6 N.S.W.

Children are having Chemistry Lessons



at School—they can have lots of fun with one of these sets.

**CHEMISTRY SETS** available in 2 sizes—similar to set shown above. Each set complete with book of instructions. Set No. 1, Price 9/10 each. Post. 1/- N.S.W. No. 2 set, Price 17/11 each. Post 1/3 N.S.W.

**WALTHER & STEVENSON PTY., LTD.,**  
391-5 George Street, Sydney.

## LEARN

AT HOME for 2/6 WEEKLY



It's "Quicker"—easier under **MONEY-BACK GUARANTEE** with a Sampson Home-Study course for:

- ★ BANJO MANDOLIN
- ★ Hill-Billy Guitar
- ★ Steel Guitar
- ★ Piano Accordion
- ★ Saxophone
- ★ Clarinet ★ Ukulele
- ★ Mouth Organ
- ★ Button Accordion
- ★ Violin ★ Piano

**5000** have succeeded—why not YOU?

It takes 3 Lessons to play first piece — 10 Lessons a variety, and 20 Lessons any piece. It doesn't matter where you live.

**Instruments.** Exclusive models available on small payments to any part of Australia — Freight paid.

**Free.** Illustrated catalogue and descriptive booklet **FREE**. Write for yours. (MENTION INSTRUMENT FAVORED).

**Sampsons, Dept. 14, 481 Kent St.,**  
Box 4184X, G.P.O., Sydney.

## INSTRUMENT CASES


We Specialise in All Classes of Covered Cabinets — Instrument, Portable and Mantel Radio Cabinets in either Leather or Leatherette.

## GIBBONS & DENHAM

122 DARLING ST., BALMAIN  
Phone WB2772 SYDNEY



# Listen to this!

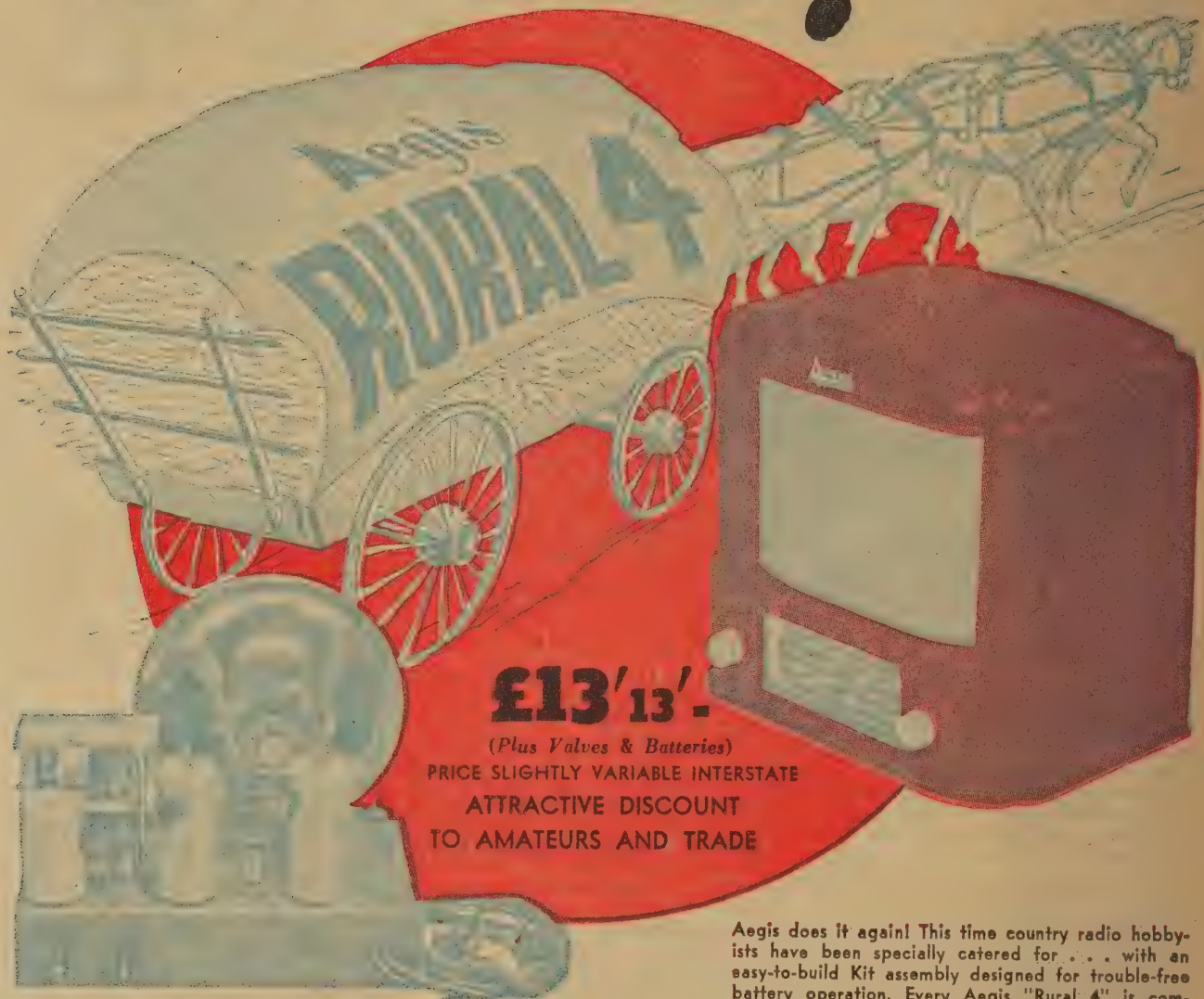

**£13' 13' -**

(Plus Valves & Batteries)

PRICE SLIGHTLY VARIABLE INTERSTATE

ATTRACTIVE DISCOUNT  
TO AMATEURS AND TRADE

## Features of the Rural Four

- Attractive mottled Bakelite cabinet.
- Button Valves for low drain with maximum gain —IS4, IR5, IT4, 3S4.
- "Aegis" Iron Core I.F.'s J9 and J10 specially designed for optimum gain.
- "Rola" 6" Permagan Anisotropic Speaker with Isocore Transformer—highly important for Battery Sets.
- Chassis and all metal brackets cadmium-plated.
- W.S.T. Switch Potentiometer.

**FREE!**

Write for 12 page illustrated  
Booklet on Circuits and  
Construction.

Aegis does it again! This time country radio hobbyists have been specially catered for . . . with an easy-to-build Kit assembly designed for trouble-free battery operation. Every Aegis "Rural 4" is complete from Valves to the last Nut and Bolt, together with full constructional details, all packed in sealed cartons with the "Aegis" symbol of satisfaction.

# AEGIS

**MANUFACTURING COMPANY** PTY LTD  
208 LT. LONSDALE STREET,  
MELBOURNE, VICTORIA

DISTRIBUTORS IN ALL STATES.

**VICTORIA:**  
Replacement Parts Pty. Ltd.  
J. H. Magrath & Co.  
Lawrence & Hansen Elec. Pty. Ltd.  
John Martin Radio & Elec. Pty. Ltd.

**N.S.W.:**  
Geo. Brown Pty. Ltd.  
John Martin Pty. Ltd.  
**QUEENSLAND:**  
Chandlers Pty. Ltd.

**S.A.:**  
Healings Ltd.  
Harris, Scarfe Ltd.  
Newton, McLaren Ltd.

**TAS.:**  
Lawrence & Hansen Elec.  
Pty. Ltd., Launceston  
and Hobart.

**W.A.:**  
Nicholsons Ltd.  
Atkins (W.A.) Ltd.



# "HANDIE-TALKIE" — Continued

from Page 33

sleeves of the sockets to A-minus or to a convenient earth point. If you don't, the set will be hopelessly unstable.

For ease of wiring we suggest that you use plastic hook-up. Cut each lead to the exact required length, trim the tip of the insulation with a sharp knife or razor blade, and solder quickly and cleanly. If you let the wire get too hot, the insulation will recede, leaving the wire bare.

Finally, connect the filament circuit through to the off-on switch, and, if you have a voltmeter handy, connect to a 1.5 volt cell and check the voltage across the filament pins.

The 3S4 valve has a centre-tapped filament, which can be operated from either a 1.4 or 2.8 volt supply. We use the parallel connection in this set, so that pin 5 becomes filament minus and is earthed. Pins 1 and 7 are bridged across and connected to A-plus. Incidentally, we wired the switch as shown in the circuit to allow one side of it to be earthed. This lends itself to possible switching schemes worked by the opening and closing of a door on the cabinet. A small point, but of possible future value.

## TRANSFORMER CONNECTIONS

Next step is to put in the other leads, including the high-tension wiring and the plate and screen leads in the IF amplifier.

Be very careful about the connections to the IF transformers, as reversal of the windings makes an enormous difference in the gain of the receiver. In the transformers used in the original set, the B-plus connection was indicated by a small rubber sleeve around one pin. The other pin of the same winding is obviously plate, while the grid pin is alongside it—not in the opposite corner. Other midget IF transformers may not employ the same connections, but the point is mentioned because it is vitally important in terms of gain.

If there is any danger of the lugs shorting to the chassis, slip a length of spaghetti tubing over them to remove this danger.

The wiring components can now be added, and, to facilitate duplication of the original set, we have coded each condenser and resistor in the circuit and marked its position in the underneath photograph. In a tiny set of this type, it is almost impossible to draw a wiring diagram, but the carefully marked photographs and the socket connection diagrams should be of considerable assistance.

## USE SMALL COMPONENTS

Once again, we must stress the absolute necessity of using midget components. It would be practically impossible to fit into the available space resistors and condensers of the normal size.

As previously mentioned, avoid straining the connecting lugs excessively or bending them at the point of junction with the component. Work with a pair of sharp-nosed pliers, or even a pair of tweezers. Bend and

snip the leads to the right shape, slip a length of 1-mil. spaghetti tubing over them and solder carefully in place.

The AVC bypass condenser, C3, can be mounted vertically in the corner between the gang condenser and the 1R5 converter. If you use a small scrap of resistor strip to anchor it in place, it makes a handy junction point for the AVC lead to the loop aerial.

The only other small component mounted above the chassis is the 1S5 grid bypass, shown as C12. This can be mounted directly between the appropriate pins on the volume control, where it will just clear the alignment of the front and edge of the chassis.

There is no need or space for shielded wire, but the short length of all leads and the layout adopted did not allow for any trouble with instability.

Having completed the wiring, assemble the speaker and transformer to the chassis and wire into circuit. We earthed one voice coil connection and used the lug as an earth point for the trimmer across the front or aerial sec-

tion of the gang. The trimmer should be mounted clear of the rotor plates and accessible to screwdriver adjustment when the set is installed in the cabinet. The proximity of batteries and the chassis to the loop has some effect on the alignment.

No variable trimmer is shown on the oscillator section of the gang. Actually, after the photograph was taken, we wired a 10 mmfd ceramic fixed condenser across the oscillator section of the gang, and this allowed a nice peak to be obtained on the aerial trimmer. With a purely numerical dial scale there is no need to worry about calibration, and the fixed condenser is naturally much smaller.

## PADDER CONDENSER

Further to conserve space we used a .0004 mfd fixed condenser for the main padder capacitance, shunting it with a small trimmer for adjustment purposes. Even if a further midget condenser has to be added in parallel the resultant combination is far smaller than the usual variable broadcast padder.

The loop aerial is bolted or screwed

Continued on Page 87.

Engineering offers so many opportunities today that the young man who is mechanically minded hardly knows in which direction or in what branch of Engineering to turn his attention.

One recommended branch is **MOTOR CAR ENGINEERING.**

Another recommendation is **DIESEL ENGINEERING . . .**

*We are again making a very special offer of training students—by Correspondence . . . you owe it to your future to get the facts!*

HERE ARE A FEW EXTRACTS FROM STUDENTS' LETTERS, which speak

for themselves:—

"I must thank you for helping me. Since getting my certificate my wages have been over £8 per week."

"I must congratulate you on the way you put me through the Motor Course. I have been able to secure a first rate job with the largest garage here."

"It is thanks to your Motor Engineering Course that I am now in the position I hold as Chief Mechanic."

"Thanks to your technical training, I have a good position as Chief Mechanic on a station."

"Eight years ago one of my sons successfully completed your Motor Engineering Course. He then opened his own garage, and has done well. I now wish to enrol two more sons."

"You have done more for me than I can put into words. When I enrolled I was just a Farm Hand. Now I own my own garage."

"I have been appointed Service Manager for the International Harvester Co., for the Northern District.—I thank you."



**GET THIS  
FREE  
BOOKLET**

**POST COUPON FOR  
FREE BOOKLET**

The Supervisor (R.H.),  
AUSTRALIAN TECHNICAL SCHOOLS,  
Assembly Hall, 8 Jamieson St., Sydney.

1047

Please send me, without obligation, your FREE BOOKLET, "All About Motors," giving details of your CORRESPONDENCE COURSE in MOTOR CAR ENGINEERING, and Special Offer.

Name .....

Occupation ..... Age .....

Address .....



# SHORT WAVE NOTES BY RAY SIMPSON

## N.Z. STATIONS TESTING ON S.W. NOUMEA AGAIN CHANGES FREQUENCY

For a long time now Australian listeners have been looking forward to the opening of the New Zealand short wave stations and at last it appears that they have commenced preliminary testing. In one of the DX sessions from Radio Australia it was announced that Wellington had been heard testing from 7 pm to 8 pm from stations ZL2 on 9540 kc and also ZL3 on 11780 kc.

AT time of writing, we have had no reports from listeners as to these tests being logged in this country, and we did not hear them ourselves. Listeners should watch these frequencies, however, as further tests will surely be made.

**READERS' REPORTS.**—Owing to altered times of going to press, and the later publishing date of the magazine, it will be impossible to acknowledge all letters intended for this issue, but these will be dealt with in the following issue. Readers should, therefore, note in each issue when reports are required for the next two months' issues, so that they will be in time to ensure their inclusion.

Over three weeks elapse between the time these notes are handed in and the date the magazine is on sale in Sydney.

**SYDNEY GET-TOGETHER.**—There has not been sufficient time to receive replies to our paragraph in the September issue concerning the proposed meeting of Sydney listeners, so it will be impossible to fix any date for this function at this time. When sufficient replies are received the writer will drop a postcard to all listeners who will be able to attend, advising them of the date and location.

A good night should be had by all those able to be present, and an opportunity made to get better acquainted with each other. Bring along a few of your best verifications and let the other chaps see what success you have had.

**RADIO FRANCE, HANOI.**—Just as we write these lines we have logged this station on a new frequency of 6055 kc in the 49-metre band. This frequency appears to be instead of the one they were formerly using, 9465 kc. At 10.0 pm a male announcer gives the news in English, and at the end of the news, at about 10.15 pm, gives their frequency as 6058 kc, and invites listeners to tune in again.

Another Indo-China station, Radio Vietnam, has also been heard lately, first on 12020 kc, and latterly on 11920 kc, but as the quality of transmission is very poor indeed, it has been hard to get any details beyond the fact that they also give news in English at 10.0 pm.

### PIETERMARITZBURG NOW USING 4878 KC.

WE have just received advice direct from the South African Broadcasting Corporation that Pietermaritzburg is now on the air using a frequency of 4878 kc at the following times, 2.45 pm to 4.30 pm, 6.15 pm to 10.10 pm, and midnight to 7.05 am, using a power of 500 watts. We do not seem to remember having had any report of the reception of this station before, so here is a chance for someone to log it, which should be possible in the early hours of the morning, and possibly till as late as 6.0 am, or a little after. Perhaps by the time our next issue is out we may have had definite word of someone hearing it.

SHORT wave notes for the November issue are due on October 4th. For the December issue they are due on November 1st. Please send them direct to Mr. Ray Simpson, 80 Wilga Street, Concord West, N.S.W.

### READERS' REPORTS

THE following readers have written us regarding stations they have heard during the past month.

Mr. A. D. Addis, Ascot, Q'land.; Mr. M. Foster, Mount Vincent, NSW; Mr. T. R. Boyd, Ripponlea, Vic.; Mr. W. G. Leeming, Alphington, Vic.; Mr. G. A. E. Major, Manjimup, WA; Mr. R. K. Clack, Punchbowl, NSW; Mr. P. Kayser, West End, Q'land.; Mr. A. W. Harris, Benalla, Vic.; Mr. H. R. Cox, Cobden, NZ; Mr. F. J. Smedley, Landsborough, Q'land.; Mr. Art Cushen, Invercargill, NZ; Mr. Rex G. Gillett, Prospect, SA; Mr. W. R. Holland, Canterbury, Vic.; Mr. R. Rooke, Manly, NSW; Mr. R. O. Block, Petersham, NSW.

### NEW STATION LOGGINGS

Call	KC	Meters	Location.	Time heard
Radio France	6055	49.55	Hanoi, Fr. Indo China.	10.00 pm
Italian	7250	41.38	Italy.	6.30 am
Luxembourg	9527	31.49	Luxembourg.	4.00 am
ZL2	9540	31.45	Wellington, N.Z.	7.00 pm
Singapore	9690	30.96	Singapore, Malaya.	10.00 pm
OTC5	11645	25.76	Leopoldville, Bel. Congo.	7.00 am
WGEA	11770	25.49	Schenectady, N.Y., U.S.A.	8.00 am
ZL3	11780	25.47	Wellington, N.Z.	7.00 pm
Manila	11840	25.34	Manila, Philippines Is.	7.00 pm
Radio Vietnam	11920	25.17	Hanoi ?, Fr. Indo China.	10.00 pm
Luxembourg	15350	19.54	Luxembourg.	8.00 pm

## NEW STATIONS LOGGED

**PHILIPPINE ISLANDS.**—On the 1st September we heard a very interesting new station operating from Manila, this being one of the Voice of America outlets. They come on the air nightly at 7.0 pm, with the playing of the "Star Spangled Banner," followed by the announcement, "This is the Voice of the United States of America, testing from Manila, on a frequency of 11840 kc in the 25-metre band."

Records are then played continuously for a complete hour, followed by the same announcement each hour thereafter. This is the only announcement we have heard from this station, so cannot give any details as to the address, &c., but a report should easily find them, we think.

**MALAYA.**—During August, Singapore opened up again on one of the prewar frequencies used by that station, 9690 kc, and since that time they have been heard at very good strength every night. The call letters of this outlet used to be ZHP, but so far the stations operated by both Radio Malaya and The British Far Eastern Broadcasting Service do not appear to use any call letters.

This new outlet for Singapore is operated by the BFEBs authorities, but late at night they carry the same programme as Radio Malaya. The best time to hear them is around 10.0 pm. Mr. Smedley and Mr. Block have also reported this station and, as we stated elsewhere, we received our verification nine days after sending our report.

**ITALY.**—For some weeks now we have been hearing an Italian station, operating on 7250 kc in the mornings, around 6.30 am. Usually the programme is the same as that on Busto Arsizio, which uses 9630 kc and 11810 kc, but on other mornings it carries a different programme. Strength of signals is never as good as Busto Arsizio, and on some mornings it is very hard indeed to follow the programme at all.

This new station appears to close at about 7.35 am, but by that time at our location it is nearly inaudible. A report has been sent to the Italian authorities on this station, so in due course we should know where this new one is located, and whether reports should be sent to the same address as for Busto Arsizio.

**LUXEMBOURG.**—From both Rex Gillett and Radio Australia we learn that Radio Luxembourg has been heard testing on two new frequencies, 9527 kc and 15350 kc. Rex has heard this 15350 kc outlet. The station authorities give the following new schedule of times on the air, all being EAST: 2.10 pm to 3.10 pm, 15350 kc; 3.10 pm to 3.30 pm, 6090 kc; 8.0 pm to 8.40 pm, 15350 kc; 8.40 pm to 9.0 pm, 9527 kc; 3.0 am to 3.40 am, 15350 kc; 3.40 am to 4.0 am, 9527 kc; and 5.0 am to 7.30 am, on 6090 kc. No doubt they will later use a frequency in the 25-metre band, so listeners should watch out for it.

**BELGIAN CONGO.**—The Belgian National Short Wave station in Leopoldville has been heard using a new frequency of 11645 kc, in their programme directed to Great Britain and the British Territories in Africa, from 6.30 am till 7.45 am. Strength of signals is good throughout the transmission, and the lady announcer has a very pleasant voice.

The call letters of this new outlet are not known, as when the station closes they announce as OTC5 in the 16-metre band, so evidently they are using this new outlet unknown to the announcer, who just gives the call for the 16-metre channel. Incidentally, there is no sign of OTC5 at our location at the times mentioned.

**NEW ZEALAND.**—According to a report from Art Cushen to Radio Australia, the long-awaited New Zealand short wave stations have at last begun test transmissions. So far, the only channels reported as being used are ZL2 on 9540 kc, and ZL3, on 11780 kc. The time of these test transmissions were from 7.0 pm till 8.0 pm.

At time of writing we have not heard either of these stations nor have we heard any reports from other listeners, though we expect that before very long they will be reported from many parts of this country, as they should put in a good signal, considering the power they intend using.



# GEAR BEHIND RADIO PHILLIPINES

## PROGRAMMES AND TECHNICAL DETAILS

IBC's general manager is Norman Paige, noted war correspondent and formerly with each of the major networks of the United States at different times. Just prior to the war, Mr. Paige was production manager of KGEI, powerful short-wave station in San Francisco.

Production manager of PBC is "Hank" Miller, formerly with the "Voice of America." Chief engineer is Gerino Pancito, outstanding engineer in Philippine radio prewar as well as today. News editor is P. J. Rappaport, formerly with United Press. A staff of 60 persons is required to operate PBC and the programme policy is designed to provide the best in radio entertainment and information for Philippine listeners and short-wave listeners as well. Its policy of good music is highlighted by four major transcription libraries, Standard, MacGregor, World, and Associated, the latter two being of vertical cut and being of particularly good quality in reproduction. Supplementing this is a large library of recordings and world-wide news coverage is provided by Associated Press.

### SPORTING

One highlight of the programming of PBC's stations is special events, and "on the spot" broadcasts. The average monthly total of remote broadcasts of KZPI alone is well over 300. These include dance bands, US Navy weather forecasts, stock market reports, coverage of large fires, sporting events, governmental functions, concerts, and countless others.

Making this great number of remote broadcasts possible are 28 permanently installed special broadcast lines to all parts of Manila and vicinity; special equipment allowing the immediate use of any telephone line (and frequently the telephone) for a regular broadcast; and two additional portable large VHF transmitters for use in remote districts or for long broadcasts where lines are not available. The studios of the Philippine Broadcasting Corporation's two stations KZPI and KZOK and the main offices of the company are located on the 5th and 6th floors of the Filipinas Building, Plaza Moraga, Manila.

### SCHEDULES

KZPI is on the air from 6.0 am to 12 midnight, Manila time (2200-1600 GMT) daily and Sunday from midnight to midnight (1600-1600 GMT). The programmes are broadcast simultaneously on 800 kc and 9500 kc. This station broadcasts almost entirely in English with a very small amount of Tagalog (the Philippine national language), and Spanish. The identifying phrase of KZPI is, "This is the Philippine Broadcasting Corporation, Radio Philippines . . . KZPI Manila 800 on your dial."

KZOK, which started broadcasting on May 15, 1947, is on the air 24 hours a day except from midnight to 5.30 am, Sunday, Manila time (1600-2130 GMT Saturday), when its transmitters are off for maintenance. (KZPI is on the air during these hours.) Simultaneous transmissions of the programmes are made on 1000 kc and 9690 kc. The daytime schedule of broadcasts is almost exclusively in Tagalog, with some few programmes in Spanish. The significant identification of KZOK is "It's ang Philippine Broadcasting Corporation, Radio Filipinas, KZOK, Maynila, Ang Tinig Ng Bayan." The transmitters of KZPI are located at Polo, Bulacan, approximately 13 kilometres

north of the Manila studios. The 800 kc transmitter is a 1000-watt output, "Pactron" custom built unit made by Pacific Electronic Corporation of Long Beach, California.

The final tubes are a pair of 4-250A's, and the output is fed to a 300 feet vertical radiator, the tallest standard broadcast antenna in the Far East. The short-wave transmitter was put into operation in December, 1946, on the 31-metre band, first on 9710 kc, then 9690 kc, and now on 9500 kc. It is a 250-watt transmitter built by Technical Radio at San Francisco, Cal., and 813's are used in the final. A half-wave vertical "L" antenna is used. KZPI transmitters are fed from the studios both by line and by VHF transmitter operating on 97.4 mc.

KZOK transmitters are located in Quezon City (in the outskirts of Manila and formerly called San Francisco del Monte). The 1000 kc transmitter was built by Craig B. "Tex" Kennedy, of KZIOB-KA3CB amateur radio fame, and Harry T. "Slim" Chaney.

Gamatron 454 H's are used in the final stage, and the output is fed to a Hertz antenna, the maximum radiation of which is north and south. The short-wave transmitter was commissioned the latter part of July, 1947, in the 31-metre band on 9690 kc. It was built by Technical Radio of San Francisco, Cal., using 813's in the final with an output of 250 watts, which is coaxially fed to a dipole antenna having maximum radiation north and south.

### F.M. TO COME

Future plans of the Philippine Broadcasting Corporation call for the almost immediate operation of an FM transmitter "Pactron" 250-watt on 101 mc; soon there will be an increase in the power of all transmitters now operating; construction of a Philippine network (medium wave) with outlets in Cebu, Iloilo, Zamboanga, Davao, and Tacloban. Plans are also in the making for moving the studios and offices of both KZPI and KZOK to a new and bigger location. Reports of reception are requested and will be verified.

As readers will see from the above description, the Philippines Broadcasting Corporation is a very modern organisation and has already become very popular with Australian listeners due to a large extent to the prompt and courteous way they verify listeners' reception reports. They are now also sending out their monthly advance programmes by air mail.

### STATION ADDRESSES

XMAG.—Army Advisory Group, APO 909, c/o P.M., San Francisco, Cal., USA.  
XMPA.—10 Snake Mountain, Hanchung-man, Nanking, China.  
CRTRE.—Radio Clube de Malange, P.O. Box 83, Malange, Angola.  
HHCN.—Avenue Christophe Number 25, Port-au-Prince, Haiti.  
VP4RD.—Trinidad Broadcasting Co. Ltd., Broadcasting House, Port of Spain, Trinidad, B.W.I.  
XURA.—Chong Sun Park, Taipei, Taiwan.  
PCJ.—P.O. Box 137, Hilversum, Netherlands.  
CXA.—Radioemissora CXA19, 18 de Julio 1393, Montevideo, Uruguay.  
XEFT.—Radioemissora XEFT, Independencia No. 74, Vera Cruz, Mexico.  
XEQQ.—Radioemissora XEQQ, Jose Maria Marroqui No. 11, Mexico City, Mexico.  
VUC.—Station Director, All India Radio, 1 Garstin Place, Calcutta, India.

## FLASHES FROM EVERYWHERE

**SWEDEN.**—In one of the recent DX sessions from Radio Australia we heard that Sweden is another country to enter the high power field. The Swedish Radio has ordered two 100 kw transmitters, which, used with beam aerials on seven frequencies, will have world wide coverage. These transmitters, however, are not expected to be in operation until some time in 1950. Mr. Arne Skoog, DX editor of Roster I Radio, has offered to send any listener a world-wide short-wave call list on receipt of two International Reply Coupons. Send your application and two coupons to R.I.R., Box 16174, Stockholm 16, Sweden, and Mr. Skoog will forward the list.

**AUSTRIA.**—There seems to have been quite an amount of frequency shuffling by the Vienna station, and it is hard to keep track of just where they are to be found. An observer in North Africa informed Radio Australia that Vienna was to be found on 6150 kc, 7195 kc, 9670 kc, and 11,765 kc. At our location we have heard them on 7180 kc in the mornings and also in the late afternoon on 11,780 kc. In addition to these frequencies, Vienna has also been reported by overseas listeners as using 9830 kc and 12,210 kc though we believe both these frequencies are no longer in use. The loudest signal just now is between 6.30 am and 7.0 am on 7180 kc.

**IRAN.**—The well-known Iran station EPB located in Teheran and operating on 15,100 kc can now be heard quite well when they give news in English at 10.15 pm. Most of the items can be followed, which makes good material for a report, and in addition both before and after the news, they play popular recordings, some of which will be identified by most listeners. Radio Tabriz has also been in the news of late and Rex Gillett reports a station on 12,000 kc with native type music, closing at 6.0 am, which we think may be Tabriz. We have also heard what seems to be the same station on 11,995 kc, though on all occasions when we have heard it, 7.0 am has been the closing time.

**AUSTRALIA.**—As a change from the normal type of stations, have a listen for some of the trawlers operating along the NSW and Victorian coasts. The best time to hear them is at 8.0 am and 5.0 pm, when they are in contact with VIS Sydney and VIM Melbourne. The frequencies most used are 6280 kc, 6400 kc., and 6675 kc.

Some time can also be spent listening to the various aircraft in contact with the radio towers at many points from Mascot to as far north as Townsville. The best frequencies to hear these are those around 6500 kc, and it was while listening on these bands the writer was able to advise the Sydney newspapers that the Dutch airliner which disappeared a few months ago, had been located. There is always something of interest around these bands.

**PANAMA.**—It is some considerable time since we have had any report about the Panama station HOB, and we were, therefore, surprised to log this one again at quite good strength recently when it opened at 9.30 pm. Its frequency is 6175 kc, and it is rather difficult to separate HOB from LRM, which uses 6180 kc. When this station opens, it gives both its broadcast band call HOA, followed by the short-wave call HOB.

### 100 FIRST AUSTRALIAN REPORTS—1000 VERIFICATIONS

**THIS** month we are very pleased to be able to advise listeners that something the writer has been striving for over the past few years has at last been obtained—100 First Australian reports and 1000 verifications. Actually the total at time of writing is 103 "firsts" and 1002 verifications.

These verifications have been obtained over a period of about 14 years and all of them are for phone reception, 98% are for commercial short wave stations with only 2% amateurs.

For some reason or another we have been particularly successful with Singapore and from a total of 22 verities from this location, 13 of them have been "firsts."

The "first report" verifications are from 36 different countries while total number of countries verified now stands at 131 with reports out to 7 others. Only about 5% of our reports have been sent by air mail and these almost exclusively to Malaya, India, Ceylon, &c. The quickest verification we have ever had was the last one we received being for Singapore on 9690 kc which arrived nine days after posting our report.

We hope the above will prove of interest to listeners, especially the younger ones who are just commencing the hobby, as it shows what can be done by watching the bands carefully and always being on the lookout for new stations. It is also an incentive to have something you are trying to get and eventually to be successful.

## THIS MONTH'S VERIFICATIONS

**KZPI, Manila.**—In addition to a very nice letter from the Production Manager, this station sends a very attractive card showing the call letters in red. Full details regarding this station and also its sister station, KZOK, are covered in the special article in this issue. Unfortunately KZPI is rather hard to log on its new 9500 kc channel but late at night it seems to be much better.

**RADIO INTERNATIONAL, TANGIER.**—This African station sent a very nice letter in English verifying our report on their transmission on 6200 kc and stated that they are at present giving programmes in French, Spanish, Arabic, and English. They gave their schedule as 0000-0300, and 1800-2300 G.M.T.; the address of this station is Radio International, Sociedad Africana de Radiodifusion, 34 Goya-street, Tangier.

**SINGAPORE, Malaya.**—The British Far Eastern Broadcasting Service are now using

a very simple verification card which gives their schedule as 0830-0030 G.M.T. daily using a power of 7½ kw on frequencies of 6770 kc, 11,735 kc, 9690 kc, and 15,300 kc. In their accompanying letter the Programme Director advised that they were planning to use a new frequency in October but did not state what it would be so readers should keep a check on the bands. Our card for this one was sent by air mail.

**JERUSALEM, PALESTINE.**—The Forces Broadcasting Station in Jerusalem in verifying reception of their test transmissions on 7220 kc and 7250 kc sent along a list of their programme for the ensuing month. The verification was very simple being just a few words on a very large sheet of paper, what one might say British officialdom at its best. However these verifications came along in very quick time, both being sent by air mail.



# With our Short Wave Reporters

## MR. ERN. MOORE OF BRISBANE

# SERVICEMAN WHO TELLS

(Continued from Page 53)

JUDGING by the few letters we have received before this issue goes to press, our new feature giving details of our various readers has been well received, and it will be continued during the next few months. This month we have information concerning a well-known Brisbane listener, Mr. Ern Moore, and without any further preamble we will let Ern tell his story.

"I have been interested in DX listening for about 10 years or so, but it was not until October, 1940, that I sent out my first report, this being to KGEI. At the present time I have 235 veries from commercial short-wave stations, though some of them are second or third verifications from the same station, but counting one verie from each station, my total would be about 216 from a total of 53 different countries. In addition to the above I also have 264 veries from broadcast band stations, mostly Americans, and 149 from amateur stations on the 20, 40, and 80-metre bands. Cards from these amateur stations are from 23 different countries.

The verifications I prize most are those from LRM, HJCX, HJDE, OIXIA, HJCA, ZNE, CKFX, PZX5, and ZPFY. I do not think there are many listeners in Australia who have a verification from HJDE. I am afraid I do not have any "first" from Australia veries for short-wave reception, but have a few for broadcast band Americans and some of them low-powered stations.

My main interest in short-wave stations are the Latin Americans, and also I am very interested in the amateurs.

When I first became interested in short-wave stations I was using a one-valve battery regenerative set, which gave very good reception and then in 1937 we bought the set we are now using, a 6-tube DW commercial job with short-wave range from 16 to about 52 metres. The antenna used is an inverted L, 75 feet long, 30 feet high, running NW to SE. In the near future I hope to have a BC348, which is an American Air Force receiver covering from 200 to 500 kc and 1500 to 18,000 kc in six bands with dial calibrated in MC. I also hope to erect some different antennas in the near future, and this will be of great use when tuning to different parts of the world.

I am a member of the URDXC, NZDXC, and ADXRC, and am Queensland official observer for ADXRC.

As will be seen from the above details, Ern is a very enthusiastic listener, and he certainly has some very nice verifications, which prove beyond doubt his ability to log the hard ones as well as the more common type of station. We can expect to hear more of him when he gets his new receiver in operation.

Next month we hope to give details of a DX listener who is known by name to all keen DX'ers both in Australia and overseas.

the car with farm produce. I rather felt that the few hours so spent added to the variety of the weekend, despite the service job sandwiched in.

The radio receiver turned out to be a four-valve superhet of a general design which branded it as about 1935 vintage. Although justifiably popular in the suburbs, the basic four-valve superhet arrangement is definitely on the borderline as a rural receiver. Valve for valve, the gain is lower than in the a-c job and, of course, the strength of signals is much less.

I could find nothing obviously amiss with this particular receiver. All operating voltages were OK, and the alignment was accurate, as far as I could judge without the services of an oscillator. Aerial and earth were OK, but it definitely sounded weak.

The final step was to test all the valves, which fortunately I could do, because the a-c had just been connected to the house. Sure enough, each of the four valves registered on the "doubtful" part of the scale, indicating that they had just about reached the end of their useful life. Perhaps it was only to be expected, because the set had been in operation for a good 10 years.

In a larger set, or on strong signals, one or two valves can be in this condition without much difference being apparent to the casual listener. But four weak valves in a four-valve battery superhet makes the difference between just enough gain and the reverse. So much for that one.

## OUR OWN LISTENING POST

Radio International 6200 kc, FZI 17,530 kc, KZPI 9500 kc (1st report from Australia), Jerusalem 7220 kc (1st report from Australia), Jerusalem 7250 kc, WLWR 15,130 kc, VUD4 11,830 kc (1st report from Australia), Singapore 9690 kc (1st report from Australia), SEAC 15,230 kc.

## THESE STATIONS VERIFY

CARDS or letters have been received by these readers confirming their reception of the following stations:

Mr. W. R. Holland.—VUC 9590 kc, VLQ3, KRHO 9650 kc.

Mr. Rex Gillett.—Jerusalem 7250 kc, SEAC 17,770 kc, TGWA 15,160 kc, Johannesburg 9450 kc, WNRX 21,610 kc, WNRA 17,780 kc, WNRE 15,280 kc, WNBI 15,150 kc, ZQP 7290 kc, 9710 kc, CKRA, HSPD 6125 kc, Dakar 15,380 kc, CE1180.

Mr. Art Cushman.—XECC, TGWA, Monte Carlo, WLWL 17,965 kc, CKRA, Kuala Lumpur, Luxembourg, VUM2 4920 kc, VLW7, VLC9, VLO, VLA7, CKCS, WLWR 9700 kc, WRUW 17,750 kc, WRUS.

Mr. H. R. Cox.—SEAC 17,770 kc, Malaya 15,275 kc, CKRA, CKNC, VLC9, VLA6, VLW3, VLB8.

Mr. F. J. Smedley.—WLWS 11,710 kc, WLWR 15,250 kc, WLWO 11,710 kc, WLWL 17,950 kc, WLWK 17,800 kc, VLA8, VLA10, VLO, VLC6, VLB8, VLB10, VLG4, KRHO 15,250 kc, PCJ, HCJB 12,450 kc.

Mr. T. R. Boyd.—VLB5.

Mr. P. Kayser.—VLR2.

Mr. R. K. Clark.—KU5Q 13,360 kc, VLG6, VLC9, FZI 11,170 kc, XGOY 11,913 kc, Noumea 6180 kc, Macao 7500 kc, HCJB 12,455 kc.

Mr. M. Foster.—Noumea, VLR2, VLR, VLO4, VLW3, VLB3, VLG10, VLA5, VLA6, VLH4, VLH5, VLW7, VLB7, VLB, VLG6, XGOA, XGOY, FZI, SEAC 17,770 kc, 15,120 kc, Malaya 15,275 kc, CHOL, CKLO, HER5, WOOW, Madrid.

Mr. R. O. Block.—Omdurman 9650 kc, Rangoon, VLA4, Saigon 6190 kc, WLWR 9700 kc, WLWO 15,350 kc, VLG3, VLG6, VLA5-7, VLB8-9.

## READER'S REPORTS

THE following readers have sent in letters and reports of their reception. These are greatly appreciated and also the many kind remarks concerning the short-wave notes.

Mr. W. Gunn, Christchurch, NZ; Mr. W. Milne, Christchurch, NZ; Mr. R. Shave, Eastwood, NSW; Mr. M. Foster, Mount Vincent, NSW; Mr. H. R. Cox, Cobden, NZ; Mr. R. Matthews, Perth, WA; Mr. A. Cushman, Invercargill, NZ; Mr. G. Major, Manjimup, WA; Mr. C. W. Jones, Gladesville, NSW; Mr. G. D. Gilbert, Burwood, NSW; Mr. P. Kayser, West End, Qld; Mr. L. Donnelly, Port Campbell, Vic; Mr. A. D. Addis, Ascot, Qld; Mr. A. T. Lane, Dalby, Qld; Mr. D. A. Ramsay, Greymouth, NZ; Mr. J. Jensen, Bankstown, NSW; Mr. N. Armstrong, Burwood, NSW; Mr. M. Krumbeck, Carlton, NSW; Mr. J. Hughes, Smithtown, NSW; Miss M. Woods, Geelong, Vic; Mr. J. Nash, Parkville, Vic; Mr. G. Garside, Melbourne, Vic; Mr. Rex Gillett, Prospect, SA; Miss D. Sanderson, Malvern, Vic; Mr. F. J. Smedley, Landsborough, Qld; Mr. J. Malcolm, Dunedin, NZ; Mr. R. Holland, Canterbury, Vic; Mr. R. E. Yates, Glenelg, SA; Mr. R. O. Block, Petersham, NSW; Mr. E. Moore, Brisbane, Qld; Mr. A. Lee, Merewether, NSW.

## "VOICE OF AMERICA—MANILA

The new Manila station on 11,840 kc mentioned in this issue began regular transmission of the Voice of America programmes as from 11th Sept. An announcement regarding this was given from KRHO and Mr. J. Saunders was kind enough to advise of this announcement. Quality of this station is not particularly good as yet, but will probably improve.

## CR6RL LUANDA, ANGOLA

THIS new station has just been logged at our new location and can be heard every morning till it closes at 7.0 am with the Portuguese National Anthem. Popular recordings are played and then just before closing, a male announcer gives two calls, the first of which sounds like CR6RA, which would be the call of their other outlet on 9470 kc which has also been heard on some mornings. CR6RL is being heard on a frequency of 15,900 kc, though Graham Hutchins of Radio Australia, advises that they are actually assigned to 16,172 kc. We understand that this station is operated by the Radio Club of Luanda and this is the only address we have at the present time.

# A Wealth Of Information

## Dymock's Book Catalogues

For an excellent selection of books on Radio, Television, Electronics, Telephony and Electroplating send for our RADIO AND ELECTRICAL CATALOGUE.

### ALSO


An enormous collection of books of value to the scientific minded is to be found in our catalogue of SCIENTIFIC BOOKS.

Dymock's Catalogues are Free and Post Free to any address.

## DYMOCK'S BOOK ARCADE LTD.


424 GEORGE STREET, SYDNEY.



RED  LINE

## EQUIPMENT

Precision in Design and Construction

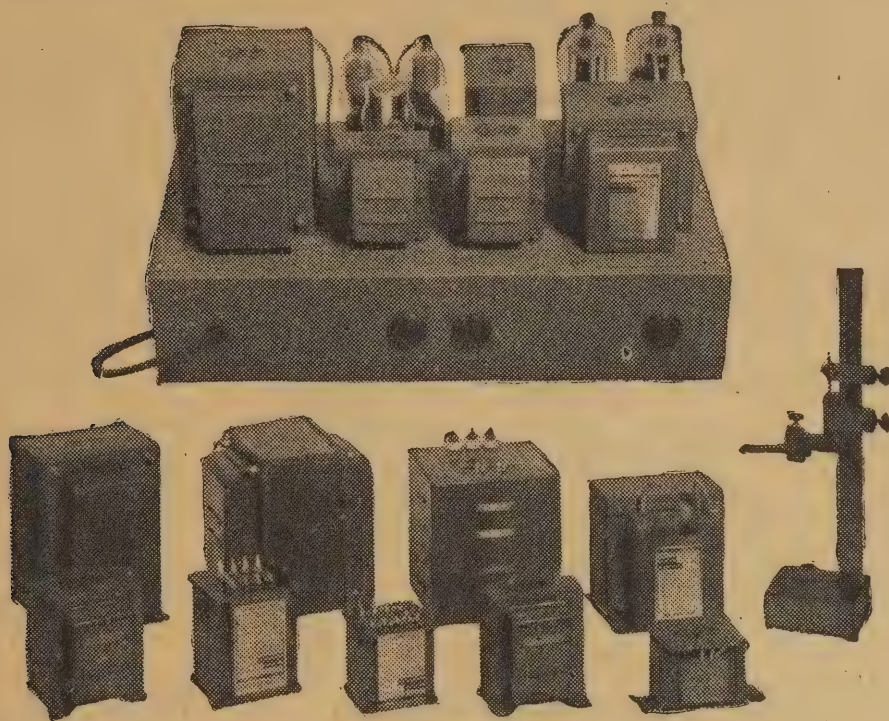

**Red Line Equipment includes:—**

- High Tension Plate Transformers
- Low Tension Filament Supplies \*
- Class B Driver Transformers
- Multi Impedance Modulation Transformers
- Heavy Duty Power Supplies
- Swinging and Smoothing Chokes
- Wide Range Audio Equipment
- Frequency Dividing Networks

\* Insulated up to 4000 volts if required.

# SWALES & SWANN

Technical Service, Wholesale and  
Manufacturers

A. T. SWALES, Gen. 4773  
2 Coates Lane, Melbourne



Trade Sales: Allen SWANN

MU 6895 (3lines)  
157 Elizabeth Street, Melbourne.

**A GUARANTEE**

**OF DEPENDABILITY**



# THE HAM BANDS WITH BILL MOORE

The amateurs of the world received news late in August, giving an indication of how they would fare in the handing out of frequencies, at the I.T.C. Atlantic City.

It was the news, that they had lost 50 kc. of their now more than fully occupied 14mc bands. The new band would now cover from 14,000 to 14,350 kc's, the lost 50 kc's going to fixed services.

The news came from the ARRL via the WIMK broadcasts and stated, that, after seven weeks' study, the new limits were arrived at and the effective date would be decided later. A footnote stated, that, the higher 100 kc's would be shared with Russian domestic stations. The final decision was unanimous, USA and Canada reluctantly agreeing (whatever that means).

We can only hope that the shared portion is shared with the KW American phones, it won't be much use for even domestic work then.

It didn't take long for the various nations to forget the remarkable war efforts of the world's 100,000 hams. We know in Australia that it was the amateur that was called on to pull the services out of their communication problems early in the war. Now it seems a matter of how much of the ether can be acquired to blast forth propaganda, for the consumption of the unsuspecting SWL.

The British Empire group incidentally, were not too generous in their support of amateur requirements. Great Britain herself being particularly reticent. Recently we heard praise of Australia's amateurs in war, we feel however that more support in peace would be a little to the point.

There seems to be only one way—a respectable slice of the radio spectrum around 21mc, in compensation. American manufacturers of ham equipment are so optimistic, that they are including this band

in their newly designed receivers and we can only hope their hunch is correct.

## AMATEUR AWARDS

QUITE a number of amateur national societies award certificates for outstanding amateur work. Those of an international nature, are mainly awards for DX and operating prowess.

The best known of these are the WAC (worked all continent), WAS (worked all States-USA), and DXCC (DX century club) issued by the ARRL; the WBE (worked British Empire) and BERTA (British Empire Radio Transmission Award) issued by the RSGB; the DXCC issued by the WIA. The following information gives an idea of the qualifications necessary to acquire the awards.

The first of the ARRL awards, the WAC is available to amateurs, who contact a station in each of the six continental areas; namely North America, South America, Oceania, Africa, Asia and Europe. The exact boundaries have been presented in QST on numerous occasions. The applicant must be a member of the IARU national society of his country and should submit the 6 QSL cards for verification to the HQ of the National Society. They will advise the ARRL to issue the award. The WAS is an award available to all amateurs who can produce QSL cards verifying contacts with stations in all 48 States of the USA (district of Columbia and Maryland interchangeable).

The cards should be submitted direct to the ARRL.

The DXCC award is divided into two qualifying sections.

The first award is made to amateurs who can produce verification of QSO's with 100 countries at any time, either prewar or postwar. The postwar contacts must, however, be listed as countries in prewar QST lists.

The second award is for a postwar DXCC and stickers will be available for each additional 10 countries confirmed. These 100 countries must conform with postwar QST lists.

The certificate is a very handsome one and an ornament for any shack. The cards must be submitted direct to the ARRL and return first class postage should be enclosed.

The RSGB's two awards are the WBE and BERTA. The first is awarded for verified two-way contacts with a British station in five areas. The same as for the WAC except that North and South America are combined. The certificate will be endorsed for phone or CW and for 28mc phone or CW. The certificate is free to RSGB members or at a cost of 2/6 to non-members. Apply to the RSGB, New Ruskin House, 28 Little Russell-st., London, W.C1. Cards must be forwarded together with application.

The BERTA is available under the same conditions, except that cards must be produced showing two-way contacts with 25 call areas in the British Dominions (VK2 to 9, VE1, ZS, &c.) and with 15 stations in the colonies (VQ2, ZMG, VRL, &c.). A minimum of R3 and a note not worse than T8, must be shown on each card for RSGB awards.

The Australian DXCC run by the WIA, is a postwar club and is open to all Australian amateurs. When you get your 100 countries confirmed send them along to your divisional secretary, who will do the rest. The call signs of club members will be listed under Phone, CW and Open sections in Amateur Radio. The ARRL countries list will be used for checking.

If you feel you would like any of the above awards and you have qualified, it won't take long to pen the necessary letter.

## 6 MX RECORD

THE 6MX distance record has been broken again, at 0310Z, 26th August, VK5KL in Darwin and W7ACS/KH6 made history in a two way contact. The previous record between KH6DD in Hawaii and J9AAK on Okinawa, made on January 25th., was over a distance of 4600 miles. The new one should be over 5000 miles.

VK5KL was using 100 watts and a three element horizontal beam and congrats. to 5KL on the first confirmed international contact from Australia on 6MX.

On the evening of the 24th August, the band again opened up for a short period between NSW and SA, and 2YQ, of Schofields, chalked up his first interstate contact. Time: 1930 hours, EAST.

Ross Treharne, VK2IQ, lectured on "Propagation" at the NSW UHF section meeting, on August 29th. Overseas visitor Paoum, UHF enthusiast, was present at the meeting.

UHF section secretary Morrie Finlay, VK2PW, has been rebroadcasting 2WI on 166mc, for the Sydney UHF gang. Incidentally, it is intended to make special 2WI Broadcasts on 6MX shortly.

The Newcastle and Coalfields gang are working extensively on 6MX and the first week in September saw their efforts rewarded, when they worked both into Katoomba and Schofields, 20 miles west of Sydney. Signals have been exchanged between 2LY, of Katoomba, and 2ADT, Cessnock, also 2BZ, Newcastle. 2YQ, Schofields, has worked both 2BZ and 2ADT. Maximum distance covered would be between 2LY and 2BZ, about 95 miles, the distance to Cessnock and 2ADT, 85 miles.

Prewar 2LZ, Wentworth Falls, and 3YU, Singleton, used to contact on 58mc, the distance being much the same, as those covered now, but 2LY is in a somewhat more shielded location.

The contacts were made using vertically polarised antenna. It is intended to try horizontal polarisation in keeping with overseas, and radar practice at these frequencies.

At this stage it is only possible to review the NSW UHF gang's effort on the Australian wide UHF field day, September 7th. Main NSW activity was centred on 166mc. 18 stations were active on the band and the following were operating mobile, 2YU, at Dural, 2AHG, Kurraong, 2ADY, 2PW, Kimsa and 2KI, in the Goulburn district.

Highlights included, a contact between



**FERRIS  
CAR  
RADIO**

See your local garage,  
radio or car dealer or  
write for literature.

The Ferris is a modern 2 unit set with speaker and dial fitting to the dashboard as intended by the Car Manufacturers. The exclusive Ferris "Noise Limiter" effectively reduces static.

Only 2½ amps battery drain means I'll never be left with a flat battery.

DISTRIBUTORS:—

**BLOCH & GERBER LTD.**

WITH WHICH IS ASSOCIATED

**THE WELDON ELECTRIC SUPPLY CO.**

16-18 MOORE STREET, SYDNEY

TELEGRAMS: "LESAB" SYDNEY

MA6291 (10 LINES)



2AHG, at Kurrajong, and 2PW, at Kiama, a distance of 85 miles—believed to be a new record for NSW.

2LY, working from Katoomba, to 2AHG, mobile travelling in a car back towards Parramatta. 2KI struck trouble from the start—not radio problems, but someone trying to steal his car, besides get mixed up with a local character. Stations active and not previously mentioned, included, 2ABB, 2ABZ, 2ALG, 2LZ, 2FI, 2TR, 2AGL, 2WJ and 2AHF.

Nothing opened on 5MX and it will be interesting to see how stations in the other States progressed.

BERU CONTEST

THE result of this year's BERU Contest are to hand and none of the major places in either the senior or junior sections were taken out by VK stations.

Senior Section:—  
First, ZS2AL, 1864 points, second, VQ3HJP, 1350, third, ZLIBY, 1225, VK2EO, 1118, G5WE, VK2ADE.

Junior Section:—  
First, ZL4GA, 828 points, second, VS9AN, 732, third, ZBIAD, 658, VK4RO and VK5RX tied for fourth place.

SWL—

SOME of us who haven't kept records of our incoming QSL cards, often wonder what percentage of contacts really QSL. We would quote the case of well known SWL, Harry Whyte-Meach, of Katoomba. He has forwarded 10,000 reports to amateur stations and with a complete filing system covering all stations heard, has kept a close check on QSL's. His efforts have realised 1900 QSL card inwards. It's generally accepted that the average ham receives about 50 per cent. inwards cards.

CLUB NOTES

THREE meetings were held during July, at the society's room, Melody Hall, George-street, Burwood. The first meeting of the month took the form of a social evening with the YL's and XYL's in attendance.

The two latter meetings were well attended despite cold weather. Lectures were delivered by Sid Clark, VK2ASD, "Data on Service Type Tubes," and John Warren, VK2QX, "The Controlling and Switching of Broadcast Programmes."

The society's membership is still increasing and the financial statement was presented by the Treasurer, on July 17th.

FEDERAL NEWS

THE Federal Executive of the WIA intends to run during the weekend, August 14 and 15, 1948, a contest in memory of amateurs who fell in the 1939-45 war. The weekend being the third anniversary of VP-Day.

It is intended to inscribe on the trophy, the names of all amateurs who paid the supreme sacrifice. The suggested name of the contest will be the "Remembrance Day Contest."

Amateurs could greatly assist the contest manager, if they notified their respective divisional secretary of any amateur friend who fell during the war.

Don't forget the WIA's VK DX contest during the four weekends in October, full rules appeared in the September issue of "R. & H."

Ray Howe, VK2ARH's lecture on "Aerials" at the August meeting of the NSW division was well received and quite a few left with better ideas on feeding their arrays.

The Queensland division's station 4WI broadcasts simultaneously on the 40, 20 and 6 metre bands. The 20 metre transmission being necessary to cover northern Queensland and Papua. 4WI broadcasts at 9 am on Sundays.

The WIA has grown rapidly since the war and membership is over 2000 throughout the Commonwealth. The turning point in the Institute should come soon with the appointment of a full time HQ staff. It is up to every amateur to give the WIA his full support.

PERSONAL

VS6AP is very pleased to contact any stations down under, he is ex-ZL2CP, well known NZer prewar.

The Jamalcans have been consistent during the month. VP5JB 14,070, 5MU 14,135.

GET YOUR TICKET!

And join the ranks of licensed amateur transmitters. The W.I.A. holds regular classes in theory, practical work, and code. Fully qualified instructors.

Write for particulars to the Amateur's official organisation,

THE WIRELESS INSTITUTE OF AUSTRALIA,  
Class Manager, Box 1734, G.P.O., Sydney.

5AO 14,080. They generally work morse at pretty high speed—loudest VP is VP4TZ Trinidad 14,050, an American serviceman.

The queer ones of the month are V zero AK whose QTH sounded like Harbarrows and FA3XR RAC and wandering. Quotes Tahiti as a QTH, should be using FO8 as a prefix anyway.

HSISS's contacts are hoping and praying for a QSL—2YC, authority—quotes VP5's as the worst QSLers.

Three HK's have been consistent in the evenings, 3CX, 5RY, IOK 14,090, 14,120, 14,035 respectively. KX6USN on Bikini and KJ6AA on Johnston, were viciously attacked during the month by VFO's.

The Fijians had a hamfest on August 23. VR2AR, 2AO, 2AN, 2AT and 2AQ plus ZL210 were all celebrating in a liquid not made from coconuts.

VK4EL has 518 postwar G contacts up now.

The Port Moresby gang now boast VK9 callsigns and active are 9B1, 9NK, 9OU, 9GW and 9BM. 9B1 is packed up ready for a move to Finschafen. The rest of the gang work for the PMG.

TG9JK has been on 20MX with NBFN, sounds OK on a conventional receiver.

The new Middle East calls are in use, MD4AN in Somalia is very strong at 0430 hours—Swan Island, West Indies, produces KS4AF on 14,020 kc's.

The latest VFO stunt is being worked by a few W2's, they come up on the rare one's frequency towards the finish and implore you to give them a leg in—VFO attacks seem to be on the decrease or maybe one gets used to them.

The Africans on phone and CW are quite good from midnight onwards. ZE2JN, Box 225 Bulawayo, especially consistent, his delayed morse is a little hard to copy at first, CR7's ZS's and VQ2 to 6, all at fair strength.




## THE STORY OF HENRY JONES

Young Henry was wiser than they thought. He was wise to his future and in his spare time became a

# REFRIGERATION SERVICE EXPERT

ELECTRICITY • GAS • KEROSENE







The story of "Henry Jones" may be your story, and his future of independent prosperity may well be yours, too. Modern Refrigeration Service, Electricity, Gas, Kerosene, opens up a wonderful field for young men of average education who wish to make good money in an uncrowded occupation...

ELECTRICITY... GAS... KEROSENE

STEADY EMPLOYMENT • CONGENIAL WORK

The DIESEL ENGINEERING COLLEGE (Est. 10 years),  
Dept. 7, 255a GEORGE ST., SYDNEY. Phone: B 2902.

Please send me immediately full particulars and Syllabus, free of obligation, of your modern REFRIGERATION SERVICE COURSE.

Name \_\_\_\_\_ Age \_\_\_\_\_ R. & H. Oct. \_\_\_\_\_  
Address \_\_\_\_\_

GOOD MONEY • INDEPENDENCE • TRAVEL



# OFF THE RECORD — NEWS & REVIEWS

In addition to the "Planets" Suite, of Holst, a notable record issue of recent weeks, and probably the most important, is of Schnabel playing the Beethoven G Major concerto. This is undoubtedly one of the greatest of concerts, and vies with the "Emperor" and the C Minor as Beethoven's best.

By JOHN MOYLE

ARTHUR SCHNABEL, Pianist and the Philharmonia Orchestra, conducted by Issay Dobrowen.—"Concerto No. 4 in G. Major, Op. 58." (Beethoven). HMV. ED.510/3.

Not so long ago, I commented on the stamp of maturity which stands out so clearly in Schnabel's work as compared with that of younger pianists. It is probably the most definite impression you will receive from this performance.

It has become almost a banality to praise Schnabel playing Beethoven, but how can it be avoided? You can examine this performance, movement by movement, subject by subject, phrase by phrase, and in each find the evidence of thought, of assessment, and execution. On this basis alone, not a note is out of place, every one falls unmistakably into the structure of the whole. So fully formed is this structure, so balanced and complete, that we are left, as always, with the impression that a great man has said the final word.

This does not mean that the earlier Gieseking records, for instance, are not in their own way, fine in performance. But it does mean that Schnabel has given his version, in full-bodied, "old master" style, in such a manner as to lessen by sheer comparison the achievements of others.

It may be that Schnabel has somewhat over-awed the conductor in the first movement, for I felt he had not the same fine control over his players as he shows in the remainder. This does not spoil the work, but it tends to outline Schnabel a little more clearly in relief than otherwise would have been the case.

In a recording with no real weaknesses, I was particularly impressed with the short second movement—probably the shortest in all Beethoven, and certainly one of the most beautiful. Both the pianist and orchestra show the most exquisite control in tempo and tone.

Against this movement, the scintillation which opens the third and last, shines like a shower of light. No one can make a piano shine and glow like Schnabel. His work here is a lesson in tone production to those modern pianists, who, if they are given half a chance, apply their hammer-like fingers to everything in the same manner.

The recording is immeasurably superior to the old pressing, and although not in the very top line for brilliance, is completely satisfying. You will need no urging to hear this excellent set.

ARTHUR GRUMMAUX AND JEAN POUGET (Violins), with Philharmonia String Orchestra. Conducted by Walter Susskind.—"Concerto in D Minor, for two Violins and Orchestra." (Bach). COLUMBIA DOX.854/5.

One of Bach's loveliest and noblest works of its kind, I thought this concerto captured all one could desire in its performance. That precision that is so essential is there, together with the flexibility and clear outlines required to bring out all the intricacies of counterpoint and orchestration. The fine second movement, always a favorite of mine, is splendidly performed, although all three are on the same general plane.

The soloists and orchestra blend well in this regard, it is a better work than I have heard produced by more famous names, who possibly, are somewhat more conscious of that fact.

To sum up—another must for your list. THE HALLE ORCHESTRA, conducted by John Barbirolli.—"Symphony No. 3" (Bax). HMV. EB.376/81.

I cannot be considered a satisfactory reviewer for this symphony, for I find great difficulty in maintaining interest through its twelve sides. I can only say that my impression is of careful, and, at times, distinguished work, produced, I was almost going to say manufactured, by a man who unquestionably knows music and orchestras.

But more than that, I can't recognise, at least in this sample of it. There is to me, much more of perspiration than inspiration, if Bax can be accused of a natural function so piebald.

I am, therefore, sufficiently honest to let you be the sole judge of its merits. Apart from Elgar, Vaughan Williams, and a few others, many of these English large-scale composers are somewhat beyond me.

From a recording point of view, it is quite good, and it is recorded under the auspices of the British Council.

ARTHUR FIELDER'S SINFONETTA.—"Concerto Grosso No. II in B Flat Major, Op. 6." (Corelli). HMV. EB.385.

A good record, as are most produced by this orchestra. Everyone likes Corelli, and it will deserve your approval.

WOODY HERMAN AND HIS ORCHESTRA, conducted by Igor Stravinsky.—"Ebony Concerto." COLUMBIA DOX.853.

One of the most striking records I've heard for many a day. I may be in a minority—amongst many friends to whom I've played it I certainly am, but it has a vitality and force, obtained almost entirely by musical and dynamic accentuation and omission, which makes it a musical cartoon of the highest order.

The recording is equally striking. If I am not mistaken it is certainly a PFRR job. Played on some special equipment with which I have been experimenting, its high frequency range is amazingly good. One is struck with admiration at the realism of the muted trumpets, in which the metallic quality is equal to anything I've heard on a disc.

The reeds of the saxophones, too, are astoundingly life-like. If you have a good amplifier, you will, I'm sure, get just as big a shock as I did on hearing the first notes.

Musically, I warn you, it's not for everybody. But of its kind, it is truly a sensation on all accounts.

JAN PEERCE, Tenor (With Victor Orchestra).—"Bluebird of Happiness" and "Because." HMV. ED.514.

Although the first named song is in my opinion, one of the worst ever written, this record gets by because of its fine recording of a fine voice. Jan Pearce isn't well known yet, out here, although very popular in America. He is typically American in style, but with much more music in his voice than at least one popular brass-lunged producer of decibels. This record has all the earmarks of being a best seller.

## Other Recordings Recently Released

DECCA

BING CROSBY AND THE JESTERS.—"Dear Old Donegal" and "McNamara's Band." Y.6038.

INK SPOTS.—"That's Where I Came In" and "I Want to Thank Your Folks." Y.6035.

BOB CROSBY'S BOB CATS.—"Way Down Yonder in New Orleans" and "Jazz Me Blues." Y.6037.

BING CROSBY WITH ORCHESTRA.—"O! Man River" and "I've Tried Ev'ry Little Star." T.6036.

ADA ALSOP, Soprano with BOYD NEEL STRING ORCHESTRA Conducted by Boyd Neel.—"Oh Sleep! Why Dost Thou Leave Me" and "Come, Beloved." Z.876.

WATSON FORBES (Viola) and Denise Lasmonne (Piano).—SUITE OF THREE DANCES.—Pt. 1.—Rigaudon; Pt. 2.—Menuet; Tambourin. Y.6026.

REGAL-ZONOPHONE

TOMMY TUCKER AND HIS ORCHESTRA.—"Another Night Like This" and "Oh Why, Oh Why, Did I Ever Leave Wyoming." G.25133.

KAY KYSER AND HIS ORCHESTRA.—"If My Heart Had a Window" and "Boin-n-n-ing." G.25134.

BILLY WILLIAMS AND THE PECOS RIVER ROGUES.—"My Adobe Hacienda" and "I'll Ride Across the Purple Sage." G.25135.

JIMMY LEACH AND HIS NEW ORGAN-OLIANS.—"Mister Moon, You've Got a Million Sweethearts" and "Accordian." G.25136.

TOMMY TUCKER AND HIS ORCHESTRA.—"Maybe You'll Be There" and "You Don't Learn That in School." G.25137.

GEORGE FORMBY WITH ORCHESTRA.—"It Could Be" and "We've Been a Long Time Gone." G.25138.

DICK JURGENS AND HIS ORCHESTRA.—"I Miss That Feeling" and "That's Where I Came In." G.25132.

ANNE SHELTON WITH ORCHESTRA.—"More Than Anything Else in the World" and "I'll Dance at Your Wedding." G.40324.

THE RHYTHMIC TROUBADOURS.—"Each Little Hour" and "When China Boy Meets China Girl." G.25142.

ELTON BRIT WITH VIOLIN, BASS AND GUITARS.—"Darlin' I've Loved Much too Much" and "She Taught Me to Yodel." G.25143.

RILEY PUCKETT, Singing and Yodelling.—"Way Out There" and "Cowboy's Dying Dream." G.25121.

MICHAEL O'REGAN (the Singing Broadcaster) with KNIGHT BARNETT AT THE ORGAN.—"Smiley" and "Where the Blue Gums Turn Red in the Sunset." G.25144. "The Paradise in Mother's Eyes" and "Beautiful is My Old Lady." G.25145. "The Silver in My Mother's Hair" and "When I was One Year Old." G.25146.

FELIX MENDELSSOHN AND HIS HAWAIIAN SERENADERS.—"Carefree" and "Wabash Blues." G.25122.

HMV.

LOUIS ARMSTRONG AND HIS ORCHESTRA.—"Endie" and "Do You Know What It Means to Miss New Orleans?" Louis Armstrong (Vocal Refrain & Tpt.); Barney Bigard (Cl.); George "Red" Callender (Bass); Charlie Beal (Pno.); Arthur "Bud" Scott (Gtr.); Edward "Kid" Ory (Tmb.); Minor Hall (Dms.). EA.3558.

LOUIS ARMSTRONG AND HIS DIXIELAND SEVEN.—"Where the Blues Were Born in New Orleans." Louis Armstrong (Vocal Refrain & Tpt.); Barney Bigard (Cl.); George "Red" Callender (Bass); Charlie Beal (Pno.); Arthur "Bud" Scott (Gtr.); Edward "Kid" Ory (Tmb.); Minor Hall (Dms.) and "Mahogany Hall Stomp" Louis Armstrong (Tpt.); Barney Bigard (Cl.); George "Red" Callender (Bass); Charlie Beal (Pno.); Arthur "Bud" Scott (Gtr.); Edward "Kid" Ory (Tmb.); Minor Hall (Dms.). EA.3559.

PHIL HARRIS AND HIS ORCHESTRA.—"It's a Good Day" and "The Possum Song." EA.3548.

BETTY RHODES WITH ORCHESTRA.—"How Could I" and "They Can't Convince Me." EA.3549.


LIONEL HAMPTON AND HIS ORCHESTRA.—"Dinah" Lionel Hampton (Vibraharp); Edmund Hall (Cl.); Coleman Hawkins (Ten. Sax.); Benny Carter (Tpt.); Joe Sullivan (Pno.); Freddy Green (Gtr.); Art Bernstein (Bass); Zutty Singleton (Dms.); and "Shades of Jade" Lionel Hampton (Vibraharp); Toots Mondello, Bud Johnson, Buff Estes, Jerry Jerome (Saxes); Ziggy Elman (Tpt.); Art Bernstein (Bass); Ernie Ashley (Gtr.); Spencer Odon (Pno.); Nick Fatool (Dms.). EA.3550.

TEX BENEKE WITH THE MILLER ORCHESTRA.—"It Might Have Been a Different Story" and "Hoodle Addle." EA.3551.

ANNE ZIEGLER AND WEBSTER BOOTH WITH ORCHESTRA.—"Love is the Key" and "Laugh at Life." EA.3553.



## PLATTERACK

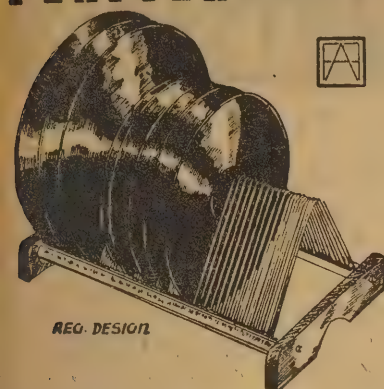

REG. DESIGN

The ideal record stand for tabulated storage of up to 50 gramophone records. Complete with register and label stickers.

**£1/5/-** plus freight plus packing

NO C.O.D. We supply also: Jewel Point Permanent Needles. Bakelite Needleclips and lids. Leatherette Record-carrying cases for 10in. and 12in. Records.

Available through distributors in all States.

**FRED A. FALK & CO.**

115A Bondi Road, BONDI, NSW.  
BONDI P.O. Box 28. 'PHONE FW1610.

## Hummelstad Harris HIGH FIDELITY PICKUPS

FOR

**Acetates & Pressings**

**LOW RECORD WEAR**

only ½ ounce vertical pressure with high lateral compliance.

**UNCHANGING CHARACTERISTICS,**

no rubber or other perishable material used for armature damping.

**FLAT RESPONSE,**

within 3db from 25 to 9,500 c.p.s. Range from 15 to 16,000 c.p.s. Output level. -45db, impedance 500 ohms.

SAPPHIRE TIPPED STYLUS EASILY CHANGED.

**PICKUPS**

For 17" discs **£10/18/6** For 12" discs **£9/12/6**

**LOWERING JACKS**

For 17" discs **£1/17/6** For 12" discs **£1/15/-**

14/1 MUMETAL INPUT TRANSFORMERS **£2/17/6.**

Enquiries:—

**V. F. Harris**

19 KNOCKLAYDE STREET, ASHFIELD, N.S.W.

Printed and Published by Associated Newspapers Ltd. (successors to Sun Newspapers Ltd.), at the registered office of the Company, 60-70 Elizabeth-street, Sydney.

**TOMMY DORSEY AND HIS ORCHESTRA.**—"At Sundown" and "Born to be Blue." EA.3554.

**FREDDY MARTIN AND HIS ORCHESTRA**—"Serenade to Love" and "When Am I Going to Kiss You Good Morn'g?" EA.3552, and—"Managua, Nicaragua" and "Speaking of Angels." EA.3555.

**GLENN MILLER AND HIS ORCHESTRA.**—"Prairie Land Lullaby" and "The Gaucho Serenade." EA.3556.

**BRUNA CASTAGNA**, Contralto with Victor Symphony Orchestra—"Carmen"—Gypsy Song, Act II (Bizet) and "Mignon"—Gavotte, Act II (Thomas) (In French). EC.160.

**THE BBC SYMPHONY ORCHESTRA** Conducted by Sir Adrian Boult—"The Planets Suite, Op. 32 (Holst). 1. Mars, The Bringer of War (2 parts). ED.503. 2. Venus, The Bringer of Peace (2 parts). ED.504. 3. Mercury, The Winged Messenger (1 part). ED.505. 4. Jupiter, The Bringer of Jollity (2 parts). ED.506. 5. Saturn, The Bringer of Old Age (2 parts). ED.507. 6. Uranus, The Magician (2 parts). ED.508. 7. Neptune, The Mystic (2 parts). ED.509.

**RICHARD CROOKS**, Tenor with Piano Accompaniment—"Serenade" and "A Dream." EC.161.

**ALEXANDER KIPNIS**, Bass (With Bala-lalka Orchestra)—"Soldier's Song" and "The Recruit's Farewell (In Russian). EC.162.

**DAVID ROSE AND HIS ORCHESTRA.**—"Humoreske" and "One Love." EA.3528.

**ROYAL CANADIAN AIR FORCE BAND** (Overseas)—"The Harmonious Blacksmith" and "The Three Solitaires." EA.3529.

**REGINALD FOORT**, Concert Organ.—Rose Marie Selection—Intro.: Introduction: "Why Shouldn't We?" "Door of My Dreams," "Indian Love Call," "March of the Mounties," "Totem Tom Tom," "Rose Marie."

### COLUMBIA

**FRANKIE CARLE AND HIS ORCHESTRA.**—"No Baby, Nobody but You" and "They Can't Convince Me." DO.3046.

**METRONOME ALL STARS WITH FRANK SINATRA.**—"Sweet Lorraine" and "Nat Meet June." DO.3047.

**DINAH SHORE WITH ORCHESTRA.**—"What can I say" After I say I'm Sorry" and "When Am I going to Kiss You Good Morning?" DO.3045.

**FRANKIE CARLE AND HIS ORCHESTRA.**—"Unless It Can Happen With You" and "You are There." DO.3042.

**VICTOR SILVESTER & HIS BALLROOM ORCHESTRA.**—"Canadian Capers" and "Jazz Me Blues." DO.3043.

**FRANK SINATRA WITH ORCHESTRA.**—"All of Me" and "I Concentrate on You." DO.3044.

**LOU PRAEGER AND HIS ORCHESTRA.**—"May I Call You Sweetheart" and "How Lucky You Are." DO.3051.

**VICTOR SILVESTER AND HIS BALLROOM ORCHESTRA.**—"I Can't Believe It Was All Make-believe" and "I Was Waiting for a Dream." DO.3052.

**FRANK SINATRA WITH ORCHESTRA.**—"Poinciana" and "I'm Sorry I Made You Cry." DO.3053.

**ALBERT SANDLER TRIO.**—"Chanson Hindoue (Song of India) and "A Raindrop Kissed a Rose." DO.3019.

**CLEMENT Q. WILLIAMS**, Baritone Accompanied by Alfred Shaw's Strings—"My Love Song to a Tree" and "Sighs." DO.3020.

### PARLOPHONE

**GERALDO AND HIS ORCHESTRA.**—"Don't Fall in Love" and "The Old Apple Tree Will Bloom Again." A.7593.

**BIX BEIDERBECKE AND HIS ORCHESTRA.** Hot Jazz Classic, No. 25—"Wa-Da-Da (Ev'body's Doin' It Now), Bix Beiderbecke (Cnt.); Bill Rank (Tmb.); Izzy Friedman (Cnt.); Min Leibbrook (Bass Sax.); Lennie Hayton (Pno.); Harry Gale (Dms.); (Recorded 7th July, 1928), and "Imagination," Miff Mole (Tmb.); Fud Livingstone (Cnt.); Arthur Schutt Nichols, Phil Napoleon (Tpts.); Arthur Schutt (Pno.); Eddie Lang (Gtr.); Dick McDonough (Bjo.); Adrian Rollini (Bass Sax.); Vic Berton (Dms.); (Recorded 1927). A.7618.

**JOE DANIELS AND HIS HOTSHOTS IN "DRUMNASTICS."**—"Bugle Boy Blues" and "Drum Kit." A.7619.

**THE ORGAN, THE DANCE BAND AND ME.**—"The Stars Will Remember (So Will I)" and "The Anniversary Song." A.7617.

**THE ORGAN, THE DANCE BAND AND ME.**—"The Mission of the Rose" and "How Did I know?" A.7621.

**DOROTHY SQUIRES WITH ORCHESTRA.**—"When China Boy Meets China Girl" and "The Old Apple Tree Will Bloom Again." A.7622.

# MULLENS'

## TECHNICAL BOOKS

### RECENT BOOKS

	Price	Postage
Philips—"Manual of Radio Practice" . . . . .	22/6	1/0½
Moore—"Electronics" . . . . .	19/3	4½d
"Technical Topics Radio Handbook" . . . . .	7/6	4½d
"Amateur Radio Station Log" . . . . .	3/6	3½d
Hubbell—"Television" . . . . .	23/9	6½d
"The Radio Handbook," 10th Edition . . . . .	21/-	10½d
Rigby—"Short Wave Radio Handbook" . . . . .	3/2	2½d
Bulgin—"Radio Service Manual" . . . . .	4/-	2½d
Ghirardi—"Modern Radio Servicing" . . . . .	40/-	1/2
"Everybody's Radio Manual" by Staff of Popular Science Monthly . . . . .	7/6	5d
Emery—"Ultra-High Frequency Radio Engineering" . . . . .	20/3	6d
Chute—"Electronics in Industry" . . . . .	35/-	8d
Fink—"Principles of Television Engineering" . . . . .	38/6	10d
Hudson—"Introduction to Electronics" . . . . .	21/9	6d
Henney—"The Radio Engineering Handbook" . . . . .	35/-	11d
"Audel's Radioman's Guide" . . . . .	28/-	9d
"Radio Reference Handbook" . . . . .	19/6	6d
Ghirardi—"Radio Physics Course" . . . . .	40/-	1/2
Norris—"Radio Engineering" . . . . .	12/-	7d
Nilson & Hornung—"Radio Operating Questions and Answers" . . . . .	24/6	7d
Ghirardi—"Radio Troubleshooter's Handbook" . . . . .	40/-	1/4
Nilson & Hornung—"Practical Radio Communications" . . . . .	45/6	1/2
Slurzberg & Ostfeld—"Electrical Essentials of Radio" . . . . .	31/6	9d
Stranger—"The Outline of Wireless" . . . . .	17/6	9d
Hund—"High Frequency Measurements" . . . . .	35/-	10d
Harvey—"High Frequency Thermionic Tubes" . . . . .	28/6	6d
"Radio for the Millions" by Staff of Popular Science Monthly . . . . .	10/6	6d
Tucker—"Introduction to Practical Radio" . . . . .	18/9	6d
Denton—"Short Wave Radio Handbook" . . . . .	8/-	4d
HOW TO MAKE IT, by Jim Gordon. Step by step directions on boat building, garden furniture, household furniture, paint and french polishing..		
TOYMAKING SIMPLIFIED, by Jim Gordon.	1/6	1½d
Illustrations and instructions for making fifty toys ..	1/6	1½d

Technical Department,  
**ROBERTSON & MULLENS LTD.,**  
107-113 Elizabeth St.,  
MELBOURNE, C.1.



# ANSWERS TO CORRESPONDENTS

UNDER THE PERSONAL SUPERVISION OF THE TECHNICAL EDITOR

M.S. (Mt. Henry, WA) reports having built up the "Little Jim" receiver with excellent results.

A. Many thanks for your report on the set and we are glad that it has proved so successful. The explanation for the condenser breakdown is probably that you did not provide for sufficient bleed, current to prevent high peak voltage on the first filter, with the inevitable result that it failed. We take it from your later remarks that you now have a single input choke and following filter condenser which would be a better arrangement. Glad to note that you like the "Serviceman Who Tells" feature.

R.B. (Jeparit, Vic.) has built up the "All Wave Battery Three" but complains of poor tone, harsh reaction and whistling effect.

A. It is very evident from your letter that the set is suffering from some form of audio instability, although the exact reason for this is not clear. Make sure that you have not inadvertently connected the 10 mfd condenser the wrong way around and that the 8 mfd condenser is in circuit and in good order. Put shields over the first two valves and shield the two "hot" leads to the volume control. As the tuning coil is unshielded, we suggest that you make sure that it is well clear of the output wiring and that the leads to it are as short as possible. You will probably find that elimination of the instability will clear up all your complaints about howling and poor tone. The dynamic microphone may just give enough output into the pickup terminals of this set but you will very likely have to connect it between the grid of the detector and earth. The tone will be very high pitched and severe howling will naturally result from any attempt to operate the microphone and loudspeaker in the same room.

R.A.W. (Portsea, Vic.) is anxiously awaiting an article on an auto radio and suggests that we should describe a few aerial systems for use at UHF.

A. We have not been able as yet to tackle the design of another auto set as there are so many other projects to be dealt with in very limited time. We agree that articles on aerial systems would interest quite a few readers but, once again, time and space is our problem. Thanks for your encouraging remarks.

K.M. (Barmera, SA) sends in his subscription and comments favorably on "Radio & Hobbies."

A. We are pleased to note that you have been able to learn so much from reading our magazine. Glad to note, also, the results from the "Little Jim's Mate" and we will bear in mind your suggestions for other articles.

M.S. (Sth. Perth, WA) asks whether it would be possible to replace one of the valves in the "1K5-Four" with a type 30.

A. You could replace the 1K5-G detector with your 30 valve, provided the latter is not unduly microphonic. Simply omit the two components which supply the screen potential. The resultant reduction in gain could be offset by remitting the 1-meg feedback resistor between the plates of the last two valves.

E.M.C.O. (Broken Hill, NSW) wants to know the operating voltages of the EF50 pentode valve.

A. We are publishing full information of this type of valve in this issue.

D.D. (Casino, NSW) renews his subscription and expresses his appreciation of the information contained in "R. & H." He also suggests that a few hints on home-wound loop aerials would be appreciated by many readers.

A. Many thanks for your subscription. We have described the loop aerial on one or two small receivers but, when it comes to winding the loop to track with the oscillator coil, we feel that it is better to rely on the commercial types.

B.H. (Pine Creek, Qld.) writes to tell of his experience and gives his ideas about model flying clubs.

A. Many thanks for your letter which we read with considerable interest. We agree that shortage of materials and cost of motors is a disadvantage, but the position should gradually improve.

N.G. (Marriickville, NSW) says he has built up an autodyne superhet. to an old "R. & H." circuit but finds that he has difficulty in tuning of all the desired stations.

## HOW TO SUBMIT YOUR QUERY

1. Queries will be answered in rotation through the columns of our magazine if not accompanied by a fee for a postal reply.
2. Queries, neatly and concisely set out, will be answered by mail as quickly as possible if accompanied by 1/- in postal notes or postage stamps. Endorse envelope "Query."
3. Back numbers are rarely available but reprints of most circuits, wiring diagrams, and parts lists will be supplied for 6d each, minimum charge 1/-. Thus a circuit, layout, and parts list will cost 1/6 in stamps or a postal note. Endorse envelope "Circuit."
4. Blueprints of exact size chassis layouts with all essential holes and cut-outs will be supplied if available for 2/6. Endorse envelope "Blueprint."

Address your letters to the Technical Editor, "Radio & Hobbies," Box 2728C, GPO, Sydney.

A. It would seem from what you say that the trouble is due to unsuitable tuning condensers. Apparently your .0005 condenser has a very high minimum capacitance which is preventing it from tuning the high frequency stations. There seems to be some confusion about the values of capacitance

quoted, but there is no other obvious reason for the trouble. We suggest you use a two-gang condenser of reasonably modern design and there should be no more trouble with it. As for the wind screen motor, we have no idea whether or not it would be applicable for driving a turntable. The prob-

## How To Increase Your Height!



IN your own home it is now possible to increase your height by a Simple, Natural Method. There are no drugs, nothing to get out of order; there is no risk; everything is simple and straightforward. This wonderful new Method should add to your stature, improve your health and appearance, or no cost!

### 500 TREATISES-FREE!

THIS remarkable literature will amaze you—it will show you the short cut to a tall, commanding personality. Through reading this wonderful literature, hundreds have already increased their height, hundreds are doing so at this moment. For a short while you can get one of these Treatises Free—if you SEND AT ONCE.

### READ THIS ASTOUNDING PROOF!

"Without your help I would never have been able to join the Air Force. My height is now five foot seven inches, a gain of three inches in two months."

—D.B., West Wallsend.

"I have now completed two weeks' training and have already gained one inch in height."

—K.N., Sth. Toowoomba.

### SEND NO MONEY!

SYDNEY PHYSICAL INSTITUTE,  
DEPT. R.R., WAYNE HOUSE,  
28 CLARENCE ST., SYDNEY, N.S.W.

### £1,000 GUARANTEE

The above sum will be paid to any person who can prove that any one of these testimonials appearing in this announcement are other than genuine extracts from actual letters in our possession.

(Enclose 2½d. in stamps.)

R. & H. Oct.



## ANSWERS TO CORRESPONDENTS

Item is more likely to be a matter of obtaining adequate power than anything to do with interference due to sparking.

J.H. (Banksia, NSW) is interested in the latest version of the "Little General" and asks whether a "Reinartz" coil can be used in place of the aerial coil.

A. Provided the Reinartz coil is of modern design, it will probably track with a new oscillator coil of the same brand and type. The reaction winding will naturally be left unconnected.

K.J.S. (Five Dock, NSW) asks whether it is necessary to have a permit to purchase ex-army type transmitting equipment.

A. No, the regulations governing the acquisition of this equipment have long since expired and you can buy it without restriction. However, it is important to realise that the transmitting circuits must not be put into operation unless one has the necessary AOCIP to cover amateur operation. For information on courses of study, we suggest that you get in touch with the Marconi School of Wireless and the Australian Radio College, both of which advertise in this magazine. The Wireless Institute also run classes on occasions and the PMG Dept. can supply copies of the examination syllabus and relevant literature for a small charge.

B.T.R. (Ringwood East, Vic.) says he gets excellent results from the Two Valve Set For Headphones, except that there is a continuous hissing noise behind the signals.

A. It is possible that the trouble is caused by a noisy resistor in the plate or screen circuit of the 1K5-G or the plate load of the 1J6-G. Try other resistors in these positions, and also try substituting for the various bypass and coupling condensers. A run-down B-battery can also cause noisy operation. Your one valve circuit is quite a standard arrangement and should give good results. However, you may find it necessary to connect a .00025 mfd. bypass condenser between earth and the side of the RF choke remote from the plate of the valve.

J.C. (Coogee, NSW) reports having built up our electric clock and soldering pencil, both with successful results. He also has a version of the "Springtime Portable" and says the output is distorted at high volume.

A. Many thanks for your letter and the photographs of the finished articles, which certainly have a very nice appearance. The power output available from any of these small portable sets is very limited, due to the small valves used, the low B-battery voltage and the comparative inefficiency of midge loudspeakers. One can expect only enough output for the sound to be heard a few feet away in the open air, or at moderate volume in a room. Any attempt to increase the volume beyond this level only results in overloading of the audio system and severe distortion.

R.M. (North Bondi, NSW) takes us to task for using plug-in coils in one or two of our recent short-wave receivers, and suggests that the system is old fashioned.

A. We have no serious quarrel with your remarks, R.M. and agree that plug-in coils are old fashioned. But, for all that, they are far easier to get into operation, especially if trimmed manually for amateur band-work. Any number of additional sets of coils can be wound up at leisure without rendering the set inoperative during the course of one's experiments. The idea of all-band operation with switched coils is very convenient and was adopted for the "Communications Nine" receiver. But you can take it from us that there is quite a lot of work to wind and adjust a dozen superhet. coils and to install them around a switch without running into trouble from losses or absorption effects. There are plenty of readers who will not just tackle the task. As for all-band commercial units, we know of none on the market at the moment. Even manufacturers are not keen on producing these units commercially because limited demand, high price and assembly difficulties make them a poor proposition financially and in respect to labor problems.

R.B. (Blakehurst) says he has built "Little Jim II" and has had great success with it.

A. Many thanks for your report on the set, R.B. The 1J6 draws the same filament current as the 1J6-G and should be no heavier on batteries. However, it is poor economy to use a small cell with this filament, which is rated to draw 0.24 amp. at 2.0 volts. You would be well advised to use the accumulator which you apparently have available.

L. G. McK. (Dennington, Vic.) asks whether an EF50 could be used in the RF stage of the "Communications Nine" receiver and whether any alterations would be necessary.

A. Yes, and EF50 is quite satisfactory for this service. Provided care is taken with the bypassing and layout there should be no particular difficulty with instability. The screen can operate from the full high tension voltage, while the bias can be adjusted for the best balance between gain and stability.

## MAXWELL COMMUNICATIONS

# 1300 hrs saved..


### by MAXWELL TELEPHONES

If 20 persons in your organisation wasted 15 minutes per day due to faulty communications, you would lose 1300 hours or 162 working days per year.

Eliminate inefficient communications . . . save time and increase efficiency by installing MAXWELL, the ever dependable and readily serviced telephone. Maxwell 5, 10 or 20 line Telephones are ideal for organisations requiring from 2 to 21 points of communication!



20-LINE TABLE MODEL.

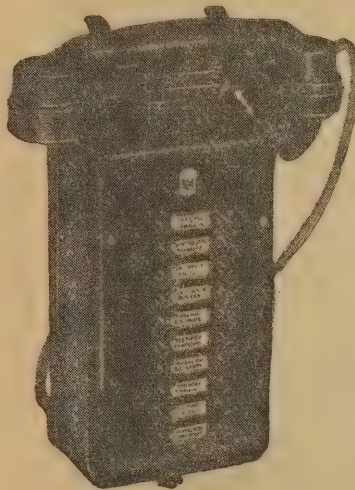

20-LINE WALL MODEL.

Whatever your communication problems may be, Maxwell engineers can solve them for you, and, when installing a sound or telephone system may we suggest you purchase your equipment outright, because it then becomes a CAPITAL INVESTMENT . . . YOUR PROPERTY . . . and IT IS 75% CHEAPER than RENTAL!

Just drop us a line on your business letterhead, and our representative will be pleased to call and discuss your particular problem with you.

# MAXWELL

## Communications

(Inc. William Blogg)

25 McLACHLAN AVENUE, RUSHCUTTERS BAY, SYDNEY. FA1274.

VICTORIA—Speakeasy Telephones, 43 Clarence St. East Malvern, Melbourne. UL6272.  
WEST AUSTRALIA—Atkins (W.A.) Ltd., 894 Hay Street, Perth — — — — — B3151.

## MAXWELL COMMUNICATIONS



## SWITCHING B & C BATTERIES

A reader from St Peters, NSW, asks the following question: "Can you inform me through the columns of your magazine whether it is necessary to have an off-on switch on the B and C batteries of a battery set?"

**T**HE answer to this question depends entirely on the circuit arrangement of the receiver. In the majority of cases it is sufficient to switch off the valve filaments, leaving the B and C batteries permanently connected. With the filaments off, the valves cannot pass current and no load is imposed on the high tension supply.

The high tension voltage is naturally present in the circuits and across the various bypass condensers but, if these are in order, the leakage through them will be to all intents and purposes zero. There is therefore little point in providing a switch on the bias or high tension supply.

However, there are circuits in which gain or reaction control is achieved by means of a potentiometer connected


across the high tension and used to vary the screen or plate voltage of one or more valves. The value of the potentiometer is usually such that the current through it is very small—probably just a fraction of a milliamp. This is of no consequence while the set is in operation, but it represents an unnecessary and harmful drain on the B batteries during the normal rest period, while the set is not in use.

The remarks, naturally, do not apply where a potentiometer is used purely as a series resistor, with no connection to chassis.


However, if the normal potentiometer circuit is used, it is essential to provide a switch to break the circuit through the B batteries and the potentiometer. Insertion of a switch at either point A

or point B in the sketch will have the desired effect. In the normal way, the operation can be performed by an extra pole on the filament switch, using one section for the filaments and the other for the high tension circuit.

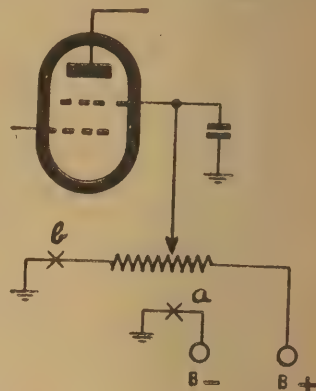It should be emphasised that both circuits cannot be broken with a single pole switch, and the arrangement in figure 2 is both unsatisfactory and dangerous. It is unsatisfactory because it does



(1)

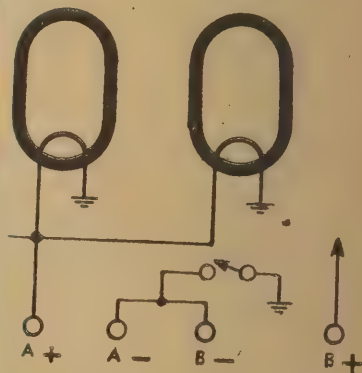

(2)

not open the high tension circuit to chassis, even though B-minus lead is broken. Actually, B-minus still goes to chassis via the A battery and the valve filaments, so that any drain imposed by the potentiometer remains.

What is no less important, the A and B batteries are connected in series when the switch is in the open position, being connected to chassis via the filaments. An accidental short between B-plus and chassis, or a breakdown in the high tension bypass condenser connects the total voltage across the filaments, with a very sad and inevitable result. If you want to break the A-minus and B-minus leads, do it with a double pole switch.



### FEATURES THAT GIVE YOU SOMETHING TO TALK ABOUT!

- ★ 5 valve Dual Wave; 1.4 volt battery operated mantel operated receiver.
- ★ Exceptional daytime range.
- ★ High gain tuned radio frequency stage.
- ★ Low current consumption.
- ★ New type "plug-in" batteries.
- ★ Dial illumination separately controlled by pressing tuning knob—saves current!
- ★ Piano finish walnut veneer cabinet.

★ Address all trade enquiries to Zenith Radio Company Pty. Ltd., 131-133 Palmer Street (off William St.), EAST SYDNEY. FA 2157-8.

**Zenith**  
RADIO COMPANY PTY. LTD.

### FREE CATALOGUE

Radio Parts, Etc.  
Send for yours today.  
Include 3d. for postage.  
**ARBEE SUPPLY CO. PTY. LTD.,**  
Bacchus Marsh.



# 'HANDIE-TALKIE'

(Continued from Page 75)

as high up as possible on the side of the cabinet and you will find that the lugs clear the chassis assembly quite nicely. The grid and AVC connections must be made to the receiver with short lengths of hook-up, while the aerial and earth connections can be terminated in pin jacks on the side of the cabinet.

The signal pickup from a small loop is naturally restricted and, once out of the immediate vicinity of local stations, it is desirable to supplement the signal pickup by using an external aerial and earth connection. There is no need to worry about this for the ordinary suburban beach picnic, but for more remote operation take along a couple of lengths of wire. However, we are getting ahead of ourselves.

The A-battery is best held in a spring clip attached to the rear lid. We bent one up from a scrap of duralumin, while the spring brass clip for the positive connection came from a cycle battery. You will find that the A-battery will need changing after a few hours operation, and the idea of soldering wires to it is quite impractical.

## FILAMENT BATTERY

We suggest that you follow our lead and provide for the type of cell used in the ordinary cycle lamp battery. Simply break the battery in halves, clip one cell into place and pop the other one into your pocket for future use.

Before you switch the set on, double check the wiring and, if possible, measure the filament voltage on all sockets with the receiver connected to the batteries and to the loop aerial. Valves are scarce, expensive and easily ruined by overload. Plug the valves in and, if everything is OK, the set should tune in a strong station.

We found that the IF transformers used in the original were a long way off optimum setting, and quite a lot of adjustment was necessary to bring them into line. A problem if you have no oscillator, but that's the way it is—or was.

## ADJUSTING CORES

We had to manufacture a small tool to grip the core slugs. Get a scrap of 18 gauge wire, bend the tip around sharply with the pliers, allowing just enough clearance to slip over the flat portion of the screws. Solder the tip to hold the bend rigid and bend the rest of the wire at right angles to form a handle.

The alignment then follows normal procedure, as described for other superhets. If the receiver tends to be unstable, increase the value of the screen dropping resistor. Conversely, you may be able to reduce it slightly without encountering trouble. But, if you find that you can operate the screen from the full high tension voltage it is almost certain that the IF transformers are not peaked properly or that the connections are the wrong way round.

That, then, is the story of our 1947 "Handie Talkie," the first of our really midget portables.

## BOOK REVIEWS

In compiling this book, the author has elected to devote the first three chapters, amounting to almost 100 pages, to a survey of radio theory and circuits. This will be good reading, therefore, for those whose technical ideas and conceptions need setting in order.

"RADIO RECEIVER SERVICE AND MAINTENANCE," by E. J. G. Lewis, M. (Brit.), IRE. Price 12/6 (approx.), plus 6d postage. Hard cover, 324 pages.

Chapters 4 to 6 take up the servicing angle, with a discussion of servicing equipment, testing components for faults, and fault-finding procedure in a receiver. Then follow general chapters on superheterodynes, all-wave receivers, aerial systems and interference, press button tuning, loudspeakers and pickups. The book ends with a discussion of radio gramophone combinations, ac/dc receivers and an appendix giving sundry color codes and data.

The book is written mainly around English equipment but the Australian reader will nevertheless find much useful information between its covers. (Our copy from Angus and Robertson.)

"APPLIED PRACTICAL RADIO," by the Technical Staff of the Coyne Electrical and Radio School. Three volumes, Australian price (approx.), £4/7/9.

For those who can afford the purchase price, these three volumes represent an excellent course of home study in radio theory and practice. They are well written and illustrated and appear to contain all that is necessary to lead the student from complete ignorance of the subject to a quite solid theoretical foundation.

Volume 1 deals with the elements of electricity, electron flow, conductors, insulators, switching and control, capacitance, inductance and the other subjects common to elementary textbooks.

In Volume 2, the reader is introduced to alternating currents and ac circuits, resonance, tuning coils, transformers and circuit coupling and finally to several extensive chapters on radio valves.

In the third volume this theory forms the basis for an introduction to receivers, amplifiers, power supplies, aerial systems and so on. There are chapters on auto radio, PA systems, frequency modulation, television and other subjects of immediate interest. In short, an excellent set of volumes for the student who is capable of following a planned course of home study.

(Our copy from Associated Trade Journals Coy.)

## RADIO DEALERS

We specialise in Radio Parts and stock all reliable accessories, including

**Coils — Dials — Transformers — Speakers — Tubular Condensers — Resistors — Electrical Accessories. Valves — Wires — Flex — Meters — Multimeter — Testing Equipment. Radio Manuals — Radio Designers' Handbook.**

If it is available—we have it!

## DAVIS RADIO CO.

Wholesale Radio Distributors.  
1st Floor — Wembley House,  
841 George St., Sydney.  
Phone M3917.

## BOYT'S

Radio & Electrical  
Distributors

## FS6 Transceivers

Brand New Complete.

Consisting of 8-Valve Transceiver complete with Meter, Valves, 6-Volt Vibrator, Pack including Vibrator, Morse Key and Connecting Leads.

£12/-/-

3 BARLOW STREET,  
SYDNEY. MA2323.

... for all Meter and instrument Repairs call on the

## METER REPAIR SPECIALISTS

FOR PROMPT  
EFFICIENT  
SERVICE

**ZENITH RADIO CO. Pty. Ltd.**

131-133 Palmer St., (Off William St.) Sydney

**MODELS** Technical Engineering Supplies, Castings and Blue Prints. Send 1/- for Catalogue. O. BOLTON, Room 1, 70 KING ST., SYDNEY.

**HOOVER**  
The World's Best  
**CLEANER**



# WANTED TO BUY, SELL OR EXCHANGE

**EXCHANGE:** D.C. multimeter, 5ma movement, ranges 3, 30, 300v; ohms 6, 30, 300, 3000mas., for K12 speaker or similar field 1000-1500 ohms, 1938 model or later. Sell R. & H., Feb., '43-Aug., '45, and Jan., '46-June, '47. McLeod, 6 Palmerston-grove, Oakleigh, Vic.

**FOR SALE:** A one-valve receiver (1Q5GT), new batteries, less phones, size 8" x 4" x 3 1/2". £5/15/- or offer. D. H. Walker, Box 17, P.O., Inglewood, Victoria.

**FOR SALE:** Large number of radio parts and radio magazines, details on application to H. J. Simmons, 29 Carlisle-street, St. Kilda, Melbourne.

**FOR SALE:** Battery charger, 4v. accumulator, B. & C. eliminator, old 5v. battery set, £3 the lot. Also 12" Rola 2500 F.C. and 10" Rola 1500 P.C. speakers, as new. Best 10" Rola 1500 F.C. speakers, as new. Best offer. Woodbridge, 24 Frederick-ave., Beverly Hills.

**FOR SALE:** A quantity of radio parts at bargain prices, incl. valves, transformers, chokes, condensers, resistors, potentiometers, knobs, etc. Must sell. Write for list. R. Dovatt, Anzac-street, Temora, N.S.W.

**FOR SALE:** 50-75 watt phone—C.W. 28 meg transmitter. Assorted gear. All copies R. & H., No. 1 to date, first five vols. bound. Q.S.T. for 1938. Amateur Radio, 46-47. Best reasonable offers. VK5JJ, J. C. Jennison, 4 Ross-street, Black Forest, S.A. L6287.

**FOR SALE:** Microphone, amplifier, seven speakers, all Phillips. Best offer. JA6259.

**FOR SALE:** Electric steel guitar and amplifier, 2 6J7G's, 2 6V6G's, 5Y3G, £25. Also two walkie talkies, operate on 22 m/cs. to 25 m/cs., £8. H. Thompson, 35 Ocean-street, Kogarah, N.S.W.

**FOR SALE:** Battery radio, 2-3valve; 30, 1J6G. plug in b'cast, s'wave coils. With phones, less batteries, £3/10/-. Letter only. J. Gillard, 3 Leichhardt-street, Glebe Pt.

**FOR SALE:** Midget portable, using latest midget parts, new, £18/10/-; also R.H. 46 Advance 5 V.D.W. in table model cabinet, powerful, new, £18/10/-, guaranteed. J. Wood, 7 Central-street, Naremburn, Sydney.

**FOR SALE:** "Transpro" multimeter and valve tester, complete, unused, condition as new. Receipts to show purchased £37. Sell for £30, or nearest offer. N. Allan, Post Office, Cooran, Qld.

**FOR SALE:** About 300 radio magazines, Aust. and overseas; also radio textbooks. Absolute gift. Also Stanley drill and 5v dual wave mantel, cheap. B. Abbott, 24 Fifth-avenue, Campsie, N.S.W.

**FOR SALE:** Kit of parts for 1946 Pentagrid, four valves and speaker extra. Worth £8/10/-, sell for £7. Details, C. Knight, East Gresford, N.S.W.

**FOR SALE:** Palec VTC-V model multi-tester, brand new, £25; 5-valve vibrator mantel model, brand new vibrator, vibrator transformer, and 6in. permag speaker; set not operating, £10; 1943 Super Six d/w receiver, all parts brand new, including 12in. Magnavox speaker; set not working, £17/10/-; 4-valve Fisk Radiolette, £5; Radio World, full set, August, 1937, to date; Radio and Hobbies, 61 copies, not consecutive; 33 copies Radio and Television; number technical books; second-hand parts. J. O'Connor, 27 Paxton-street, North Ward, Townsville.

**FOR SALE:** Set, ED447/51 Harold in Italy—Berlioz, 37/-; Set ED209/12 Picture at an Exhibition—Moussorgsky, 30/-; Postage 2/6 extra. A. G. Loveday, Elimbah, Qld.

**MUST SELL:** Leaving State, Lot 1, Vox, amp, with pre. amp—6J7, 6C6, 6V6, 5Y3, no cab., with 12" spkr., Ellipsoid mike with 6ft. floor stand. Port. gram. fit with Atom P.4. Lot for £10/10/-. Lot 2, Little Gen. rec., complete, and playing with 8" Rola, also USL44 dial, no cab., also parcel of parts, incl. 60 mica cond., 75 paper cond., 150 resistors, EBF2, 1T4, 1S5, 1R5, drill, elect. iron and host of other parts. Lot for £10/10/-. Apply F. Hall, c/o Regent West, Post Office, Victoria.

**SALE:** University S.O.A. test oscillator, 150 kcs—32 mcs. good condition; internally new, £7/10/-. F.O.R.E., Ipswich, Q. Cpl. Cameron, K. J., 82 Wing, R.A.A.F., Amberley, Qld.

**SALE:** 10 volumes "Applied Electricity," never been used. Cost £17/17/-; Accept £12/10/-, or best offer. Apply, "Cairns," Lido-avenue, Narrabeen.

**SALE:** 10w. 6V6G P.P. amplifier, with latest Rola 12/42 P.M. speaker, including pick-up, excellent tone, four months old, £18. Write or call, 81 Glyndon-road, Camberwell, Vic.

**SALE:** 2 crystal sets, 25/-; 1-valve set, £2/10/-; all with 2000 ohms earphones. T. Francis, 8 College-street, Hamilton, Vic.

**SELL:** Cathode ray tube, 5". Sell, exchange for parts, meters, offers to Stephenson, 152 Fullerton-street, Stockton, Newcastle.

**SALE:** Navy receivers, new, No. P29, with valves and fractional h.p. 240v. motor, and No. M361 (no valves), £4 each. G. Payne, 61 High-street, North Sydney.

**SALE:** B.38 H.F. communications receiver, 3 bands, 10-20, 20-40, 40-60, m/cs. 110.240 A.C. and 6-volt operation. Built like a battleship for Royal Navy. Perfect reception. Sell or exchange for twin lens reflex camera. 50 Streatham-road, Bellevue Hill.

**SALE:** Folded horn (PMG type), beautiful veneered timber, compete with speaker, also H.M.V. pick-up and motor in cabinet to match. What offers? Phone FU5304.

**SALE:** "Monty" 2-valve A.C., complete with cabinet, phones new, £8 or offer. N. Ellason, 295 Wardell-road, West Marrickville.

**SALE:** M-meter (1000 ohms), £3; tester, £5; crystal parts, gangs, some valves. 116 Norton-street, Leichhardt, Sydney. LM2233.

**SALE:** New valves, equivalent 5Y3G, 6B6G, 6U7G, 6F6G, 8/6 ea. Blueprints of oscilloscope circuit using 5BP1, 3/- ea. R. Naughton, 7 Elizabeth-street, Kingsgrove, N.S.W.

**SELL** 1 2000 ohms headphone, 15/-; 1 130 ohms headphone, 6/-; 3 1-gang tuning condensers, 3/6 each; 1 1J6-G valve, once used, 12/6; other radio parts, cheap. G. F. Learmonth, c/o Mrs. Ross, Lyon-st., Warwick, Qld.

Readers wishing to buy, sell or exchange goods are invited to insert an advertisement on this page. The cost is 9d per line; minimum charge 2/3. Approximately 6 words to a line. Advertisements for the next issue must reach our office by **WEDNESDAY, OCTOBER 8.** Dealers' advertisements not accepted.

**SELL:** Hammerlund Super-Por chassis, engraved panel, both venier dials and circuits. Suit ham building own receiver, 30/-; Also cables for No. 19 transceiver, 6/-; L. Hearn, 80 Munro-street, Coburg, Victoria.

**SELL:** Porcelain nine-pin silver-plated sockets for EF50 series, new, 4/9. 23 Doom-ben-avenue, Eastwood. WL1186.

**SELL:** New Jap 4-valve transceiver, 1000k/c crystal, spare valves, £10, or offer. What offers for separate copies of R. & H. from 1940-47? Jones, 6 Russell-avenue, Lindfield, N.S.W.

**SELL** Calstan, VCT, AC and DC model 223A, extra leads, etc., as new, £25 or offer. A. Williams, 85 Cabramatta-road, Mosman.

**SELL:** New, two 832, two 808, one 809. Offers? Mail only, please. Alexander, 3 Byrnes-avenue, Neutral Bay, N.S.W.

**SELL:** Three 1.4 volt valves, 1D8GT type. One lot. Used, but all quite serviceable. 30/- lot, posted. A. F. Tucker, Traynor's Lagoon, via St. Arnold, Vic.

**SELL:** 2 only 210's with ceramic sockets, dw coil kit w/s.w. osc. rf. aer. cutting head, 8 chokes, crystal, velocity mikes, 3-gang .00014, 3 meters, breeze plugs. Line trans., 200/80000, 30-15kc. £14 lot, or separate. Write E. Englander, 44 Toorak-road, South Yarra, Vic.

**SELL:** R. & H. from Oct., 1942. Also old copies of QST from 1927. What offers? Box 49, P.O., Merredin, W.A.

**SELL:** Paton VCT £15, University job; osc. £8/10/-, both good order. F. Hall, c/o Regent West Post Office, Victoria.

**WANTED:** Gauge "0" electric locomotive, any make, price, and particulars to J. Nevill, Post Office, Toowong, Qld.

**WANTED:** R. & H. for year 1946, also Listener in Handbook, No. 14. Pars. to W. Downer, 1267 Burke-road, East Kew, Vic.

**WANTED:** New or SH, power tranny, 230v. input, 385v. CT 385v; at 125ma., 5v at 3 amp; and 6.3 or 2.5 windings. Price to Paton, Seymour, Victoria.

**WANTED** urgently by ex-Army sig. studying for amateur licence: One complete set connectors for Army No. 11 set, comprising 1 10-pin, 1 4-pin, 1 3-pin. D. Dalcesse, Myrtleford, Victoria.

**WANTED—Radio and DX enthusiasts** Don't miss this chance to form a club in the Parramatta to Liverpool district. For particulars write or call, Ern Bentlin, 36 Mountford Avenue, Guildford, NSW.

**STAMPS**—100 all different super quality stamps, including many large pictorials, only 2/- Post Free. G. A. LAKER, Postage Stamp Merchant, 115 Queen Street, Brisbane, Queensland.

**ALBUMS.** Globe Junior (illustrated) 1/9 each, Globe Loose Leaf (illustrated) 7/6 each. Price List Stamps Free. MAYFAIR STAMPS, A.P.T.A., 7 Gleeson Avenue, St. Peters, N.S.W.

**STAMPS**—25 Br. Empire, 9d; 50, 1/6; 25 World, 6d; 50, 1/-; 25 Indian States, 1/6; 25 S. American, 1/3; 25 Switzerland, 1/- Send stamp for Price Lists. ATLAS STAMP CO., Box 1, Roseville, N.S.W.

## Stamps on Approval

Approval sheets are my SPECIALITY, good clean stamps at attractive prices sent on 14 days approval. Now is the time to send for a selection. N. Cleary, 12 Ryan Street, Northcote, N.16, Victoria

## —STAMPS—

6 New Guinea 2/- or 12 5/6; 10 Papua 4/6 or 20 10/-; 7 Spanish-Morocco, views, 1/-; 13 2/-; 10 San-Marino 9d or 30 3/-; 8 Tonga 2/6. List Free. Commonwealth Catalogue, 1/2 posted. Hinges, 2/6 per 1000. Postage Extra under 5/-.  
W. ACKLAND,  
82 Elizabeth St., Melbourne, C.I.

You get maximum performance from all

"R. and H." Circuits by using

## "RWS" TRANSFORMERS

Plate Supply, Filament Modulation, C.R.O., etc., for Power Supply Components for the New 100w. RIG. Consult.

## RADIO WINDING SERVICE,

32 CULWILLA-ST., HURSTVILLE.

## MAKE MONEY AT HOME



Special Postal Courses in modern money-making arts and crafts will teach you how to turn spare time to profit. For a Home Business or a Profitable Hobby, send stamp today for FREE BOOKLET. Dept. B, Le Bon College (Regd.), Box 279, Haymarket P.O., Sydney.

## HOBBYISTS

Beat the Shortages. Save Money. Make It Yourself. Any Formula and Method 2/6. E.g.:—Paints, Enamels, Lacquers, Varnishes, Dyes, Inks, Colours, Cosmetics, Cements, Adhesives, Glues, Soaps, Stain Removers, Plating Solutions, Soldering Fluxes, Invisible Inks, Luminous Paints. LUX RESEARCH AND INFORMATION BUREAU, Box 36, Stn. Yarra, Victoria.

Printed and Published by Associated Newspapers Ltd. (successors to Sun Newspapers Ltd.), at the registered office of the Company, 60-70 Elizabeth-street, Sydney.



**"Cracajac" Air Rifle** — possesses tremendous power and accurate sighting, very strongly made—perfectly safe, 35/- and 2/- posting.

**"DIKTA" Donkey Engine**—brass piston and boiler — beautifully made, ideal for working models, etc. Absolutely safe for children. Complete with whistle, funnel, etc., 39/6. Add 1/6 postage.

**"Cosmocord" English Crystal Pick-up Cartridges**, 37/6, or 38/-posted.

**Hand, carbon microphone**. Gives splendid reproduction. Fine offer, 7/6 complete with transformer, battery, jack lead, 27/6, or 28/6 posted.

**Army Morse Code Sets**. Beautifully made, 10/6. Add 1/6 postage. Battery 5/- extra. Suitable headphones 10/-. Add 1/- postage.

**BUG MORSE CODE KEY**. Beautifully made, for amateurs and professionals, 57/11. Carrying Case 15/- extra. Postage 2/6 extra.

**Handy size, reliable Torch**. Chrome finished, very attractive, complete 5/5 or 6/- posted.

**English miniature crystal sets**—fitted with "Perikon" crystal detector. Approx. average range 10-15 metres. Tuning range, 200-500 metres. 24/6. Add 1/- postage.

**2 Cell Standard Torches**, metal case, 4/6. Fitted with 2 batteries. Add 1/- postage. Special price to Trade.

**Box of Four English JEWELLERS' SCREW DRIVERS**. Assorted sizes. Special Wooden Box, 9/8 or 10/3 posted.

**"WAKOUWA"**  
The world's greatest novelty. It's a scream. It's a wonder! Great fun for young and old. Just press the base and he will perform. 7/9 or 8/2 posted.

**Magnetic "LOVE PUPS."** Screamingly Funny Little Novelties. Fun! and what Fun. They do the most unusual, unheard things. 3/6 or 4/- posted. The pair could fit in a Safety Match Box.

**NOVELTY WATER PISTOLS**  
Simple action, 3/3, or 3/9 packed and posted.

**"Durable" English Unbreakable Black Enamelled High Grade Fountain Pens**. Inoxydable Nib, pocket clip. Push bottom filler. 25/-, or 25/6 posted.

**"BIRO" Ball Point Pen**, 55/-.  
"Burnham" 14ct. nib, 20/9, 7/8. "Mentmore Autoflow", 23/9. "Unique", 16/9. "Platinum", 6/9. Add 6d postage to each.

**English de luxe table tennis sets**, sturdy, attractive, with 4 balls, 2/6 or 22/6 posted.

**"C O LIBRI" Lighter**—just arrived from England—Single action—automatic. You will be proud to own one. 33/3 posted.

**Stromberg Carlsson**  
2000 ohms. Wonderful value at 21/- Add 1/6 postage. These phones are brand new!!



**MINIATURE TELESCOPES**  
Just arrived from England. 3 x 4 Section Optically precision ground and polished lenses. 9/11. or 10/6 posted.

**English Microscopes**. Beautifully made, just the thing for budding young scientists. Magnification 100. Complete with slides, tweezers, etc., in polished lock-up Cabinet. £5/5/-. Add 2/6 postage.



**"Percy"**

**The WALKING PENGUIN**



The best novelty yet — children will adore him — non-mechanical, yet walks on a slight down grade. 5/2, or 5/8 posted.




**Plated Metal-cased Tobacco Case and Cigarette Maker**. Complete. Very Simple. 7/6, or 8/3 posted. Shut to make Cigarette on front.




**English Crystal "Cosmocord" Pick-Up**. Wonderful clarity and sensitivity. £3/6/-. Add 1/6 postage. Chromed Cantilever Pick-Up with Cosmocord Crystal, £3/19/6. Plus 1/6 postage. English "Goldring" Pick-Up. Wonderful value, 53/9, plus 1/6 postage.

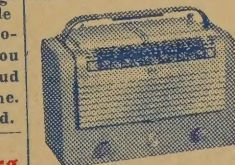**English Parker Flints**, long, hard, 2/9 per doz. posted.



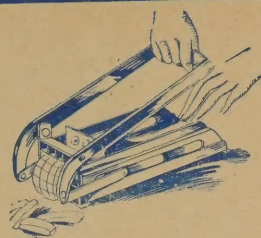**"CADET" 5-valve Portable**. Ultra smart Cabinet, wonderful tone, clarity, and fidelity. £29/6/-. Add freight. Weight packed, 35lb.



**All Metal British Potato Chipper**, 14/3. Posted and packed, 1/6 extra. Easy, Strong, Safe. One stroke makes a dozen chips.



**SPECIAL OFFER**

**English Polo Lighter** — Swift action, beautifully finished. Usual retail price, 15/-. Now 9/6, or 10/- posted.



**JEEP English Pedal Car** scale model. Complete with headlights, water carrier, spare wheel, etc. Size, 16"x20"x36". £14/12/6. Add freight. Weight crated approx. 65lb. Add 15/- for crate.



The "Lucas" Pedal Car as supplied to H.R.H. Prince William of Gloucester, solidly made, 3 feet pedals and adjustable seat. 48"x19"x12". Remarkable value at £11/15/-. Add freight. Weight crated, 75lb. Add 15/- for crate.




**Tumbling Block and Coin Trick**. Amuses, amazes and mystifies. Anyone can do it. 3/7, or 4/- posted.



**Modern Radio Servicing**. U.S.A. £2, plus 1/- postage.

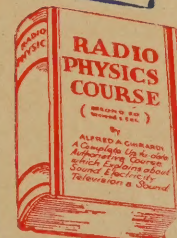A giant size book for radio amateurs and professionals.



**Radio Physics Course**, £2, plus 1/- postage.

Another giant size U.S.A. Book chock full of diagrams, drawings, circuits, etc.

**LEVENSON'S RADIO**

226 PITT STREET, SYDNEY.

Games, Hobbies, Novelties, and Slot Machine Specialists. Everything from A to Z in Radio at Same Profit Prices. Phone M2525 and M2526-7. Goods forwarded C.O.D. Post or Rail over 10/- (C.O.D. Rail within N.S.W. only; not interstate.)



# WANT MORE MONEY IN YOUR WALLET?



then . . .

## Learn **RADIO** in your spare time!

Get into Radio—today's fastest moving profession. You can earn good money in Radio. Let us take you in hand and train you for a splendid Radio career. Today is an electronic age with Frequency Modulation already here and Television just around the corner. More miracles of Radio are on the way.

### EARN GOOD MONEY WHILST LEARNING

You don't have to wait a year, or even six months, before you are ready to begin "cashing in". We will show you how to earn extra money almost from the word "go". Many students make £4 and up to £8 per week in their spare time whilst studying.

### PREVIOUS KNOWLEDGE UNNECESSARY

You don't need a knowledge of Radio or Electricity—we'll give you all you need of both, in a simple, practical manner, that makes learning easy. presented, too, in such a way that you remember what you're taught and how to put that knowledge to practical use

### COSTS LITTLE

Think of this—for a few pence per day—actually less than many fellows spend on tobacco—you can prepare yourself for a man-sized job in Radio NOW

### TRAIN AT HOME, OR AT OUR BENCHES

A.R.C offers ambitious men a sound, proven course in Radio Engineering. Sound because it is the result of many years' successful operation, proven because hundreds of ex-students owe their present success to the College.

You can learn with equal facility at home (by means of our correspondence course).

### NOW IS THE TIME TO ACT

Send in today for the free book, "Careers in Radio and Television." It's a book no man can afford to miss. It shows you the steps you can take to get into Radio immediately!

## AUSTRALIAN RADIO COLLEGE PTY. LTD.,

Cnr. Broadway and City Road, Sydney.

Phones: M6391, M6392.

★ ★ CUT THIS COUPON FOR FREE BOOK ★ ★	
<p>To Mr. L. B. GRAHAM, Principal, Australian Radio College, Pty. Ltd. Broadway, Sydney. Phone M 6391-2.</p> <p>Dear Sir—I am interested in Radio. Please send me, without obligation on my part, the free book, "Careers in Radio and Television."</p> <p>Name .....</p> <p>Address .....</p>	<p><b>GET THIS FREE BOOK NOW!</b></p>